

Resistor Network Answers

1. (a) pd = 3.6 V (1) 1
 Example of answer;
 p.d. = 0.24 A × 15 Ω = 3.6 V
- (b) Calculation of pd across the resistor (1)
 [6.0 – 3.6 = 2.4 V]
 Recall V = I_R (1)
 I₁ calculated from their pd / 4Ω (1)
 [correct answer is 0.60 A. Common ecf is 6V/4Ω gives 1.5 A] 3
 Example of answer:
 I₁ = 2.4 V / 4.0 Ω = 0.6 A
- (c) Calculation of I₂ from I₁ – 0.24 [0.36 A] (1)
 [allow ecf of their I₁. common value = 1.26 A]
 Substitution V = 3.6 V (1)
 R = 10 Ω (1) 3

[7]

2. (a) p.d. across 4 Ω resistor
 1.5 (A) × 4 (Ω)
 = 6 V (1) 1
- (b) Resistance R₂
 Current through R₂ = 0.5 A (1)

$$R_2 = \frac{6(V)}{0.5(A)}$$
 R₂ = 12 Ω (1) 2
 [allow ecf their pd across 4 Ω]
- (c) Resistance R₁
 p.d. across R₁ = 12 – 6 – 4
 = 2 V (1)
 Current through R₁ = 2 A (1)

$$R_1 = \frac{2(V)}{2(A)} = 1\Omega (1)$$
 [allow ecf of pd from (a) if less than 12 V]
 Alternative method
 Parallel combination = 3Ω (1)
 Circuit resistance = 12(V)/2 (A) = 6Ω (1)
 R₁ = 6 – (3 + 2) = 1 Ω (1) 3
 [allow ecf of pd from (a) and R from (b)]

[6]

3. Charge

Charge is the current \times time (1) 1

Potential difference

Work done per unit charge [flowing] (1) 1


Energy

9 V \times 20 C (1)

= 180 J (1) 2

[4]

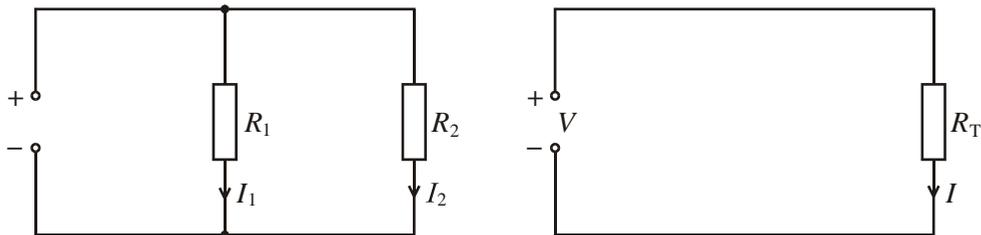4. The power supplies in the two circuits shown below are identical.



Write down the relationship between I_1 , I_2 and I which must hold if the combined resistance of the parallel pair, R_1 , and R_2 , is to equal R_T .

$$I = I_1 + I_2$$

(1 mark)

Hence derive the formula for the equivalent resistance of two resistors connected in parallel.

From Ohm's law:

$$I = V/R_T \quad I_1 = V/R_1 \quad I_2 = V/R_2 \quad (1)$$

$$\therefore V/R_T = V/R_1 + V/R_2 \quad (1)$$

$$\text{and } 1/R_T = 1/R_1 + 1/R_2 \quad (1)$$

(3 marks)

Use your formula to show that the resistance between the terminals of a low-resistance component is hardly changed when a high-resistance voltmeter is connected in parallel with it.

$$\text{If } R_V \gg R_{\text{low}} \text{ then } 1/R_V \gg 1/R_{\text{low}} \quad (1)$$

$$\text{and } R_T \approx R_{\text{low}} \quad (1)$$

Allow method based on numerical example

(2 marks)

[Total 6 marks]

5. Resistance calculations

Evidence of 20 Ω for one arm (1)

$$\frac{1}{R} = \frac{1}{20} + \frac{1}{20} \quad (1)$$

$$R = 10 \Omega \quad (1)$$

3

Comment

This combination used instead of a single 10 Ω resistor [or same value as before] (1)

because a smaller current flows through each resistor/reduce heating in any one resistor/average out errors in individual resistors (1)

2

[5]

6. Circuit

Ammeters and two resistors in series (1)

1

[1 mark circuit penalty for line through cell or resistor]

Cell e.m.f

$$E = 150 \times 10^{-6} \text{ (A)} \times 40 \times 10^3 \text{ (}\Omega\text{) total } R \quad (1)$$

Powers of 10 (1)

2

$$E = 6.0 \text{ (V)}$$

New circuit

Voltmeter in parallel with 25 (kΩ) resistor (1)

1

Resistance of voltmeter

$$\text{(Total resistance)} = \frac{6\text{(V)}}{170 \times 10^{-6} \text{ (A)}}$$

$$= (35.3 \text{ k}\Omega) \quad (1)$$

$$\text{(Resistance of II combination)} = 35 - 15 \text{ k}\Omega$$

$$= (20 \Omega) \text{ [e.c.f. their total resistance]} \quad (1)$$

$$\frac{1}{20} = \frac{1}{25} + \frac{1}{R_V}$$

$$\frac{1}{R_V} = \frac{5 - 4}{100}$$

$$R_V = 100 \text{ k}\Omega \text{ [108 k}\Omega \text{ if } R_T \text{ calculated correctly]} \quad (1)$$

Alternative route 1:

3

$$\text{p.d. across } 15 \text{ k}\Omega = 2.55 \text{ V} \quad (1)$$

$$(\therefore \text{p.d. across II combination} = 3.45 \text{ V})$$

$$\text{resistance combination} = 20 \text{ k}\Omega$$

$$\rightarrow R_V = 100 \text{ k}\Omega \quad (1)$$

$$(1)$$

Alternative route 2:

3

$$\text{p.d. across parallel combination} = 3.45 \text{ V} \quad (1)$$


$$I \text{ through } 25 \text{ k}\Omega = 138 \mu\text{A} \quad (1)$$

$$\rightarrow R_V = 100 \text{ k}\Omega \quad (1)$$

$$(1)$$

[7]

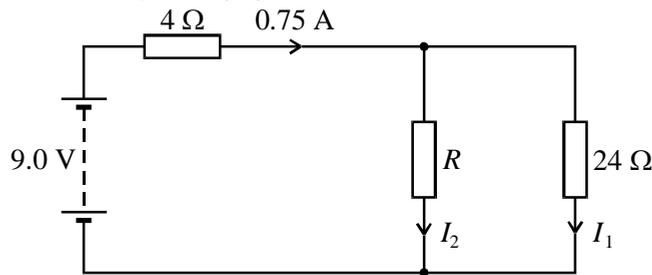7. The circuit shows a battery of negligible internal resistance connected to three resistors.



Calculate current I_1 .

Voltage drop across 4Ω resistor = $3V$ (1)

$$I_2 = \frac{(9V - 3V)}{24\Omega} \quad (1)$$

$$I_1 = 0.25A \quad (1)$$

(3 marks)

Calculate resistance R

$$I_2 = 0.75A - 0.25A = 0.50A \quad (1)$$

$$R = 6V / 0.50A = 12\Omega \quad (1)$$

$$R = 12\Omega$$

(2 marks)

[Total 5 marks]


8. Diagram of torch circuit:

The lamp will light

Correct circuit

2

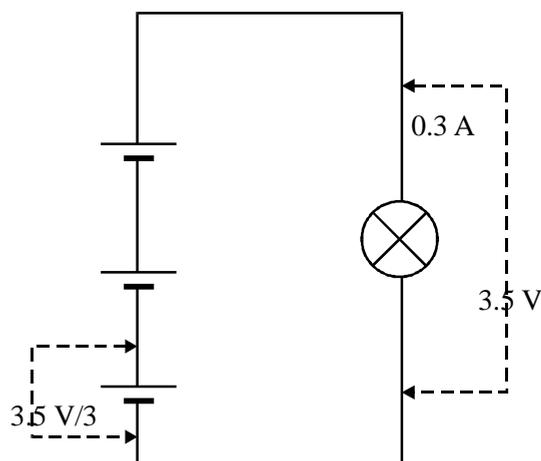[Circuit showing one cell only is allowed one mark only unless the cell is labelled 4.5 V. If a resistor is included, allow first mark only unless it is clearly labelled in some way as an internal resistance.]



Voltage across each circuit component and current in lamp:

Either 3.5 V/3 shown across the terminals of one cell or 3.5 V across all three cells

3.5 V shown to be across the lamp

0.3 A flowing in the lamp [i.e. an isolated 0.3 A near the lamp does not score]

Calculation of internal resistance of one of the cells:

3

$$\text{Lost volts} = 4.5 \text{ V} - 3.5 \text{ V} \text{ or } 1.5 \text{ V} - \frac{3.5\text{V}}{3}$$

$$\text{or total resistance} = (4.5 \text{ V})/(0.3 \text{ A}) = 15 \text{ K}\Omega$$

$$\text{Internal resistance of one cell} = [(1.0 \text{ V})/(0.3 \text{ A})] \div 3$$

$$\text{or } [(0.33 \text{ V}) (0.3 \text{ A})] \text{ or lamp resistance} = (3.5 \text{ V}) / (0.3 \text{ A}) 11.7 \Omega$$

$$= 1.1 \Omega \text{ or } = (3.3\Omega)/3 = 1.1 \Omega \quad 3$$

[Some of these latter marks can be read from the diagram if it is so labelled]

[8]

9. Proof:

$$V = V_1 + V_2 \quad V = V_1 + V_2 \quad (1)$$

$$V = IR \quad V_1 = IR_1 \quad V_2 = IR_2 \quad \div I \quad (1)$$

$$\text{Substitute and cancel } I \quad \text{Sub using } R = \quad (1)$$

3

Explanation of why it is a good approximation:

Resistance of connecting lead is (very) small (1)

So $I \times R_{(\text{very}) \text{ small}} = (\text{very}) \text{ small p.d.}/e^{-1}$ s do little work so p.d. small/r small (1)

compared with rest of the circuit so p.d. small

2

Circumstances where approximation might break down:

If current is large **OR** resistance of rest of circuit is small (1)

[**Not** high voltage/long lead/thin lead/high resistivity lead/hot lead]

1

Calculation:

$$\text{Use of } R = \frac{\rho l}{A} \text{ with } A \text{ attempted } \times \text{ sectional area} \quad (1)$$

$$\text{Correct use of } 16 \quad (1)$$

$$\text{Use of } V = IR \quad (1)$$

$$0.036 \text{ V} \quad (1)$$

4

[10]

10. No, because V is not proportional to I OR not straight line through origin / (1)
only conducts above 0.5 V / resistance changes 1


Use of $R = 0.74$ / current from graph (1)

= 9.25 Ω [9.0 – 9.5 Ω] [Minimum 2 significant figures] (1) 2

Calculation of p.d. across R [8.26]	Calculation of total resistance [109 – 115]	Ratio R : ratio V	$E = \Sigma IR$ (1)
$\div I$	– diode resistance [9]	Correct substitutions	Correct substitutions (1)
103 Ω [100 – 106] (1)			

3

[If not vertical line, 0/2]

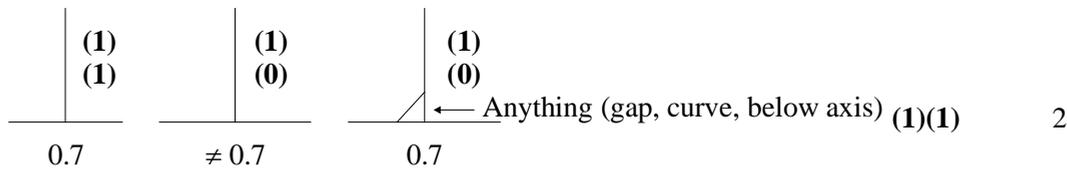

[Otherwise 0 0]

[8]

11. Circuit diagram

Resistor with another variable resistor/potential divider/variable power pack (1)

Ammeter reading current through resistor (1)

Voltmeter in parallel with resistor (1) 3

Graph labels

Straight line – resistor } Both labelled (1) 1
Curve – lamp }

Potential difference

At 0.5 A p.d. = 3.5 V / 3.4 V + 7.8 V / idea of adding p.d. [for same current] (1)

= 11.2 V / 11.3 V (1) 2

[Accept 11.0 – 11.5 V]

Resistance of lamp

$\frac{3.5 \text{ V}}{0.5 \text{ A}}$ [OR their value of p.d. across lamp \div 0.5 A] (1)

= 7.0 Ω (1) 2

[e.c.f. their value]

[8]

12. Show that

[In diagram or text]

- states p.d. same across each resistor (1)
- use of $I = I_1 + I_2 + I_3$ [symbols or words] (1)

• $\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$ (1) 3

[$I = V / R$ stated somewhere gains one mark]

Networks

- First network: 2.5(Ω) (1)
Second network: 25 (Ω) (1)
Third network: 10 (Ω) (1) 3

Meter readings

- Ammeter: 25 (mA) (1)
Voltmeter V_1 : 25×10 OR 50×5 [ignore powers of 10] (1)
= 0.25 V (1)
Voltmeter V_2 : 50×25 [ignore powers of 10] (1)
= 1.25 V (1) 5

[Allow full e.c.f. for their resistance for 2nd network OR their V_1 answer]

[11]

13. Readings on voltmeter

Use of any resistor ratio OR attempt to find current in *either* circuit (1)

At 950 kΩ

$$V = \frac{10 \text{ k}\Omega \times 6 \text{ V}}{960 \text{ k}\Omega} = 0.063 \text{ V (1)}$$

At 1.0 kΩ

$$V = \left(\frac{10 \text{ k}\Omega \times 6 \text{ V}}{11 \text{ k}\Omega} \right) = 5.45 \text{ V (1)} 3$$

Use of circuit as lightmeter

Maximum resistance corresponds to low light intensity/resistance down as light intensity up (1)

∴ lightmeter or voltmeter reading will increase as light intensity increases [or reverse] (1) 2

[Can ecf for 2nd mark if resistance/light intensity incorrect and/or p.d. calculation wrong]

[5]