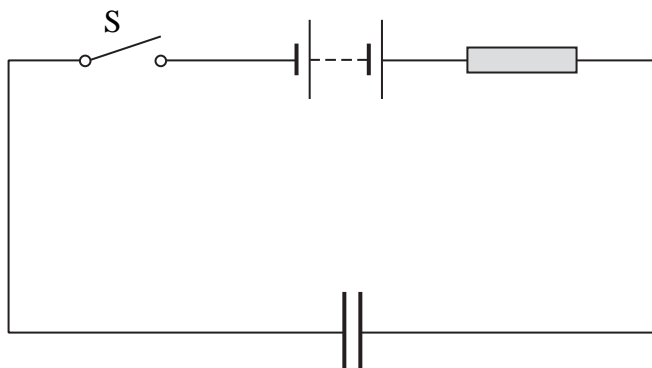


1 An uncharged capacitor is connected into a circuit as shown.



(a) Describe what happens to the capacitor when the switch S is closed.

(2)

.....

.....

.....

.....

(b) A student models the behaviour of the circuit using a spreadsheet. The student uses a $100\ \mu\text{F}$ capacitor, a $3.00\ \text{k}\Omega$ resistor and $5.00\ \text{V}$ power supply. The switch is closed at time $t = 0\ \text{s}$.

	A	B	C	D	E
1	t / s	I / mA	$\Delta Q / \mu\text{C}$	$Q / \mu\text{C}$	p.d. across capacitor/V
2	0	1.67	167	167	1.67
3	0.1	1.11	111	278	2.78
4	0.2	0.74	74	352	3.52
5	0.3	0.49	49	401	4.01
6	0.4	0.33	33	434	4.34
7	0.5	0.22	22	456	4.56
8	0.6	0.15	15	471	4.71
9	0.7	0.10	10	480	4.80
10	0.8	0.07	7	487	4.87

(i) Explain how the value in cell C4 is calculated.

(2)

(ii) Explain how the value in cell E3 is calculated.


(2)

.....

.....

.....

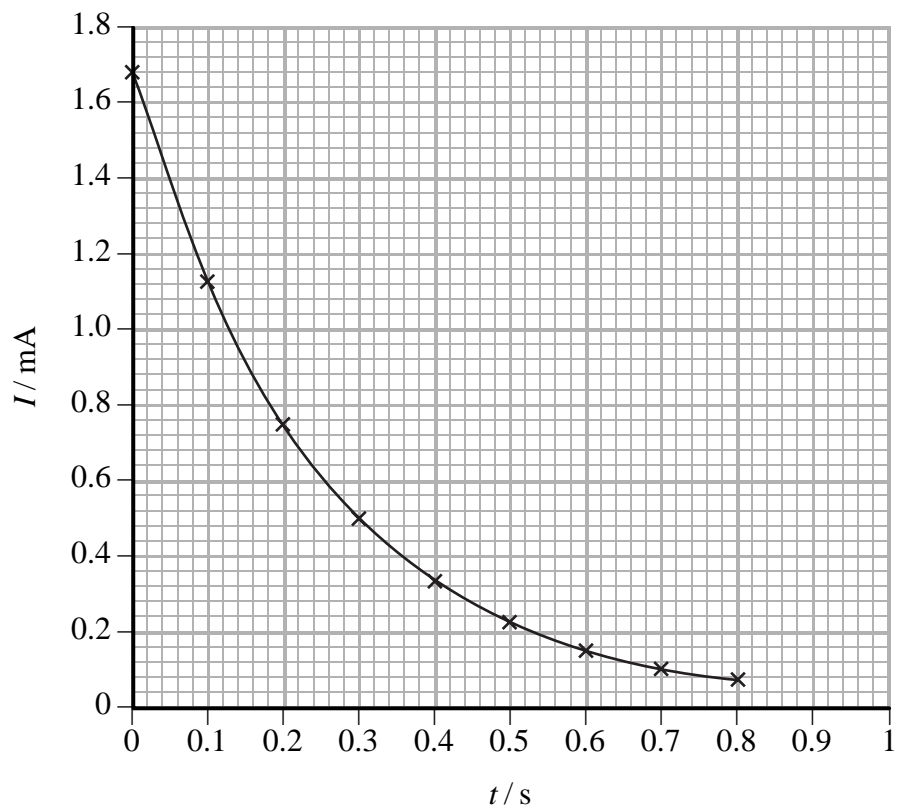(c) The graph shows how the spreadsheet current varies with time.



(i) Use the graph to show that the time constant is approximately consistent with the component values.

(4)

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

(ii) The student thinks that the graph is an exponential curve. How would you use another graph to confirm this?

(3)

.....

.....

.....

.....


.....

.....

.....

(Total for Question = 13 marks)

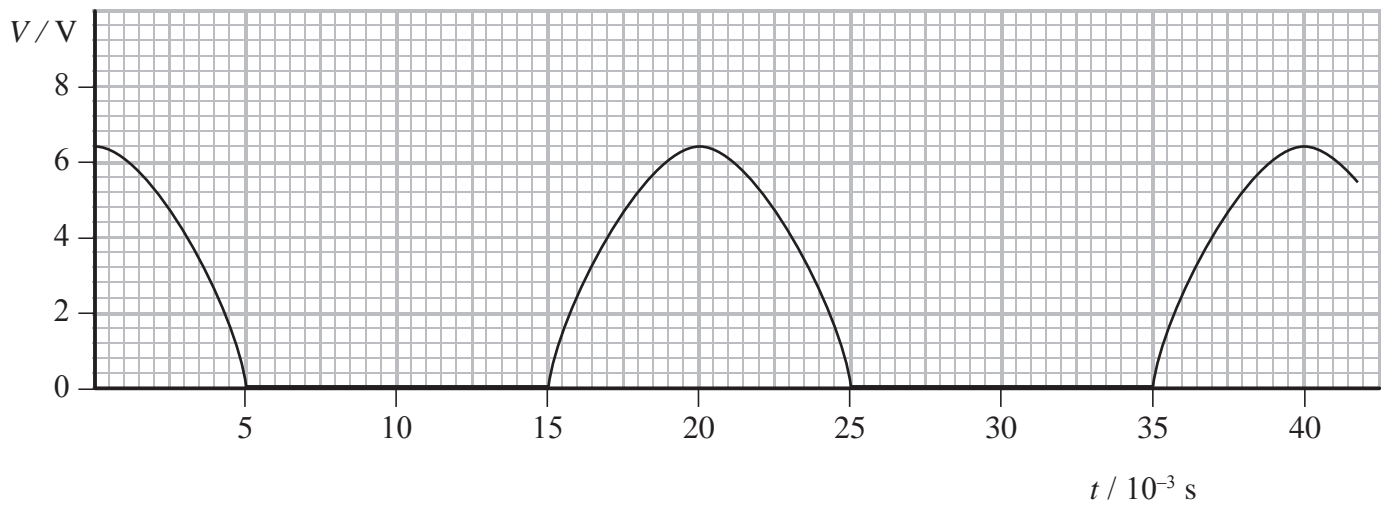- 2 The graph shows how the output V from the terminals of a power supply labelled d.c. (direct current) varies with time t . This type of supply will not allow current to flow backwards through it.




- (a) A student connects a capacitor across the terminals of this power supply in order to try to produce a constant voltage.


Suggest how this produces a constant voltage.

(2)

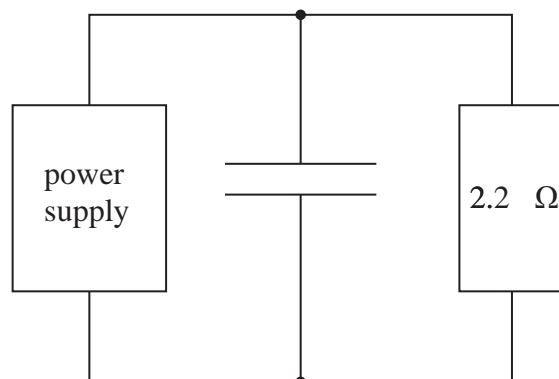- (b) The student then connects a resistor across the capacitor as shown.



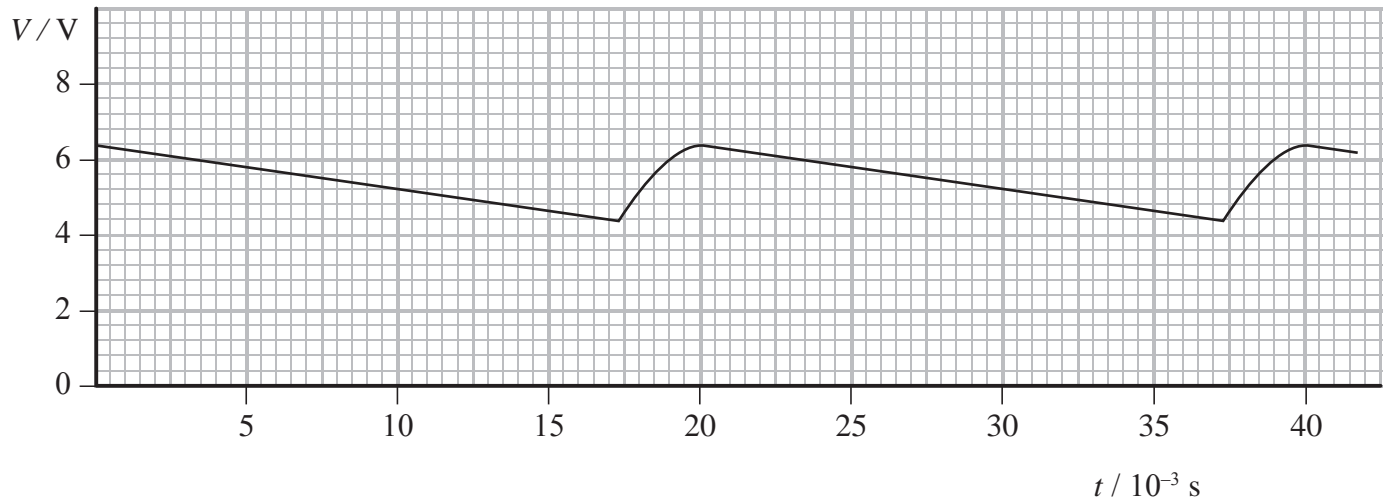The graph shows the variation of the potential difference V across the resistor with time t .



(i) Estimate the average potential difference across the resistor.

(1)

Average potential difference =

(ii) Calculate the average current in the resistor.

(2)

Average current =

(iii) Determine the time in each cycle for which the capacitor discharges through the resistor.

(1)

Discharge time =

(iv) Calculate the charge passing through the resistor during one discharge of the capacitor and hence determine the capacitance of the capacitor.

(4)

Charge =

Capacitance =

(c) The student wants to produce a potential difference across the same resistor that has less variation in magnitude.

State, with a reason, what the student could do to achieve this.

(2)

(Total for Question = 12 marks)


3 A particular experiment requires a very large current to be provided for a short time.

(a) An average current of 2.0×10^3 A is to be supplied to a coil of wire for a time of 1.4×10^{-3} s. The resistance of the coil is 0.50Ω .

(i) Show that the charge that flows through the coil during this time is about 3 C.

(2)

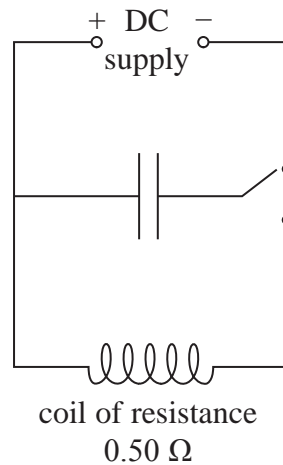(ii) The circuit shows how a capacitor could be charged and then discharged through the coil to provide the current.



The circuit contains a capacitor of capacitance $600 \mu\text{F}$. This capacitor is suitable to provide the current for 1.4×10^{-3} s.

Explain why the capacitor is suitable.

(3)

(b) It can be assumed that the $600 \mu\text{F}$ capacitor completely discharges in $1.4 \times 10^{-3} \text{ s}$.

(i) Calculate the potential difference of the power supply.

(2)

Potential difference =

(ii) Calculate the average power delivered to the coil in this time.

(3)

Average power =

(Total for Question = 10 marks)