

Question			Expected Answers	Marks	Additional Guidance
1	(a)	(i)	$I = V/R = 8.0/200$ $I = 0.040$ (A)	C1 A1	
		(ii)	$V = 24 - 8 = 16$ (V)	B1	
		(iii)	$R = 16/0.04$ giving $R = 400$ (Ω)	C1 A1	accept ratio of p.d.s to ratio of Rs ecf from (i) & (ii) ie (a)(ii)/(a)(i)
		(iv)	$P = VI = I^2R = V^2/R$ $P = 0.640$ (W)	C1 A1	ecf from (i) & (ii) accept 640 mW
(b)	(i)	the thermistor has heated up/ its temperature has increased so its resistance has dropped so the ratio of the voltages across the potential divider changes/AW	B1 M1 A1	accept so the current increases accept so IR of fixed resistor increases	
	(ii)	voltages are equal so resistances are equal	B1		
(c)	(ii)	straight line through origin labelled R passing through 0.06,12	B1 B1	allow correct lines with no labels	
	(ii)	upward curve below straight line through origin labelled T passing through 0.06,12	B1 B1		
			Total question 3	15	

Question			Answer	Marks	Guidance
2	(a)	(i)	energy transferred from source/changed from some form to electrical energy; per unit charge (to drive charge round a complete circuit)	M1 A1	allow chemical
		(ii)	(some) energy is transferred into thermal energy /lost as heat in (driving charge through) the battery. It behaves as if it has an (internal) resistance/AW or there is a voltage drop across/decrease in voltage from the battery when a current is drawn from it/AW	B1	allow any description which uses $E = V + Ir$ with symbols defined but not just the formula alone or e.g. statement about 'lost volts'/current
	(b)	(i)	correct substitution into resistors in parallel formula $R = 90 \Omega$	C1 A1	$1/R = 1/90$ or 0.011 correct answer
		(ii)	using $V_{out} = R_2/(R_1 + R_2) V_{in}$: alt: $16 = I \times 120$ $V_{out} = 90/(30 + 90) 16$ so $I = 0.133 \text{ A}$ $V_{out} = 12 \text{ V}$ $V_{out} = 0.13 \times 90 = 12 \text{ V}$	C1 C1 A1	ecf (b)(i) accept $V_{out} = (90/120) \times 16 = 12 \text{ V}$ for full marks N.B. beware of false ratios, e.g. $360/(120 + 360)$ giving correct answer; give first marking point only
A A A		(iii)	resistance (of thermistor) decreases (with temperature increase) current <u>in circuit</u> increases or as <u>total</u> resistance is less so current in thermistor increases voltage ratio between 30Ω and combination changes so voltage across thermistor falls	B1 M1 A1 M1 A1	max 4 marks QWC mark is either of the M marks
	(c)	(i)	$Q = It = 1.2 \times 8 \times 60 \times 60$ $Q = 34560 \text{ (C)}$ correct unit,	C1 A1 B1	accept 3.5 or 3.46×10^4 allow 1 mark for answer of 9.6 or 576 allow C, kC, A s; N.B. 9.6 A h or 576 A min score 3/3
		(ii)	energy = $34560 \times 16 = 552960 \text{ J}$ or $I = 1.4/16 = 0.0875 \text{ A}$ time = $552960/1.4 = 394970 \text{ s}$ then $t = 34560/I$ time = $394970/3600 = (109.7 \text{ h}) = 110 \text{ h}$	C1 C1 A1	ecf (c)(i) allow full marks for $1.2 \times 8 \times 16/1.4 = 110 \text{ h}$ allow 111 h when using $3.5 \times 10^4 \text{ C}$
Total				18	

			Answer	Marks	Guidance
3	(a)		360 (Ω)	B1	
		(i)2	Curr	B1	not symbol only; not unit only
		(ii)1	$1/10 + 1/20 + 1/40 = 1/R$ $R = 5.7 (\Omega)$	C1 A1	$1/R = 0.175$ accept 40/7
		(ii)2	potential difference	B1	accept p.d. or voltage not e.m.f.; not symbol only; not unit only
	(b)	(p.d./voltage must be proportional to curre as long as temperature and/or (other) physical conditions remain constant R line is straight and <u>through the origin</u>	M1 A1 B1	symbols may be used but must be defined
		(ii)1	(same current so) at 0.6 A have $4.5 \text{ V} + 4.5 \text{ V} (=9.0 \text{ V})$	B1 B1	accept resistors in series (so V's add); i.e recognise that at 0.6 A each component has 4.5 V across it.
		(ii)2	add currents so at 3.0 V have $0.2 \text{ A} + 0.4 \text{ A} = 0.6 \text{ A}$	B1 B1	accept attempt to add currents for 1 mark (i.e. method mark)
		(iii)	thermistor heats up/temperature increases resistance (of thermistor/circuit) decreases (so current rises) temperature/resistance becomes constant (after 2 s) because thermal equilibrium reached	B1 B1 B1 B1	max 3 marks accept thermal energy frees more charge carriers/AW accept energy/power/heat in/generated = energy/power/heat out/lost
Total				15	