

M1. (a) current that is always in the same direction 1

(b) total resistance = 30 (Ω) 1

$V = 0.4 \times 30$ 1

12 (V) 1

*allow 12 (V) with no working shown for 3 marks
an answer of 8 (V) or 4 (V) gains 2 marks only*

(c) $P = 0.4 \times 12 = 4.8$ 1

5 (W) 1

*allow 5 (W) with no working shown for 2 marks
allow 4.8 (W) with no working shown for 1 mark*

[6]

M2. (a) (i) 15 1

(ii) 4.5 or their (a)(i) x 0.3 correctly calculated
*allow 1 mark for correct substitution, ie 0.3 x 15/their (a)(i),
provided no subsequent step* 2

(ii) decrease 1

(b) **Y**
*accept any correct indication
reason only scores if Y is chosen
accept voltage for p.d.* 1

(only one that) shows a direct current / p.d.
or
a battery / cell gives a direct current
accept both X and Z are a.c.

or
a battery/cell gives a constant current/p.d.
*accept it's a constant current/p.d.
it is not changing is insufficient* 1

[6]

M3. (a) (i) 50 (Hz) 1

(ii) 2760 (W) 1

(b) 12

allow 1 mark for correct substitution, ie 2400/200

or

allow 1 mark for 2760/230 provided no subsequent step shown

2

amps

1

(c) the charge is directly proportional to the time switched on for
accept for 1 mark the longer time (to boil), the greater amount of charge
or positive correlation
or they are proportional

2

[7]

M4. (a) $25(\Omega)$

1

(b) (i) $2(\text{V})$

allow 1 mark for showing a correct method, ie 6 / 3


2

(ii) equal to

1

[4]

M5.(a)

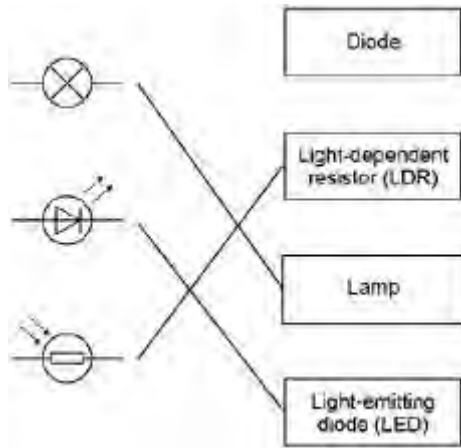

allow 1 mark for each correct line if more than one line is drawn from any symbol then all of those lines are wrong

3

(b) (i) half

1

(ii) 3(V)

1

(iii) V_1

1

(c) (i) potential difference / voltage of the power supply
accept the power supply
accept the voltage / volts
accept number of cells / batteries
accept (same) cells / batteries
do not accept same ammeter / switch / wires

1

(ii) bar drawn – height 1.00A
ignore width of bar
allow 1 mark for bar shorter than 3rd bar

2

(iii) as the number of resistors increases the current decreases

1

[10]

M6.(a)	battery, lamp and ammeter connected in series with variable resistor	1
	voltmeter in parallel with (filament) lamp	1
(b)	<p>Level 2 (3–4 marks): A detailed and coherent description of a plan covering all the major steps is provided. The steps are set out in a logical manner that could be followed by another person to obtain valid results.</p> <p>Level 1 (1–2 marks): Simple statements relating to relevant apparatus or steps are made but they may not be in a logical order. The plan would not allow another person to obtain valid results.</p> <p>0 marks: No relevant content</p> <p>Indicative content</p> <ul style="list-style-type: none"> • ammeter used to measure current • voltmeter used to measure potential difference • resistance of variable resistor altered to change current in circuit or change potential difference (across filament lamp) • resistance (of filament lamp) calculated or $R=V / I$ statement • resistance calculated for a large enough range of different currents that would allow a valid conclusion about the relationship to be made 	4
(c)	(as current increases) resistance increases (at an increasing rate)	1
(d)	any value between 6.3 and 6.9 (Ω)	1
(e)	A: Filament lamp	1
	B: Resistor at constant temperature	

1

C: Diode

1

[11]

M7.(a) (i) any **six** from:

- switch on
- read both ammeter and voltmeter
allow read the meters
- adjust variable resistor to change the current
- take further readings
- draw graph
- (of) V against I
allow take mean
- $R = V / I$
allow take the gradient of the graph

6

(ii) resistor would get hot if current left on

1

so its resistance would increase

1

(iii) 12 (V)

0.75 × 16 gains 1 mark

2

(iv) 15 (Ω)

1

16 is nearer to that value than any other

1

(b) if current is above 5 A / value of fuse

1

fuse melts

allow blows / breaks

*do **not** accept exploded*

1

breaks circuit

1
[15]