

## A Level Physics A

**H556/02** Exploring physics

**Question Set 8** 

1(a)	A capacitor of capacitance 7.2 pF consists of two parallel metal plates separated by
	an insulator of thickness 1.2 mm. The area of overlap between the plates is $4.0 \times 10^{-4}$ m <sup>2</sup> .
	Calculate the permittivity of the insulator between the capacitor plates.

(b) Fig. 21 shows a circuit.

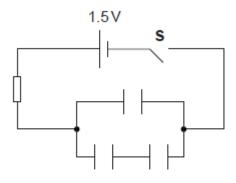


Fig. 21

The capacitance of each capacitor is  $1000\,\mu\text{F}$ . The resistance of the resistor is  $10\,k\Omega$ . The cell has e.m.f. 1.5V and negligible internal resistance.

(i) Calculate the total capacitance C in the circuit.

(ii) The switch **S** is closed at time t = 0. There is zero potential difference across the capacitors at t = 0.

Calculate the potential difference V across the resistor at time t = 12 s.

## **Total Marks for Question Set 8: 6**



OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department

For queries or further information please contact The OCR Copyright Team, The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

opportunity.

of the University of Cambridge