

A level Physics B

H557/01 Fundamentals of physics

Question Set 8

A student makes an iterative model for the decay of charge on a capacitor. The time constant of the circuit is RC = 10 s.

time lapsed /s	charge Q on capacitor /C	charge $\triangle Q$ leaving capacitor in time interval $\Delta t = 1 \text{ s}$ /C	charge Q remaining after time interval Δt
t	Q	$\Delta \mathbf{Q} \approx \frac{\mathbf{Q} \Delta t}{\mathbf{RC}}$	/C Q = (Q − ∆Q)
0	5	$\frac{5\times1}{10}=0.5$	5-0.5 = 4.5
1	4.5		

Complete the numerical values in the two blank cells in the table.

Explain the physics behind the approximation in the third column of the table (b) (i)

$$\Delta \mathbf{Q} \approx \frac{\mathbf{Q} \Delta t}{\mathbf{RC}}.$$
[2]

(ii) State the assumption made in using this approximation and explain how its effect can be made insignificant.

[2]

[2]

Total Marks for Question Set: 6



Copyright Information

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact The OCR Copyright Team, The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge