

## A level Physics B

**H557/02** Scientific literacy in physics

## **Question Set 2**

1 This question is about charging a capacitor in a circuit with two resistors in series.

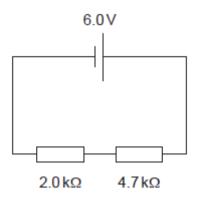


Fig. 1.1

Show that the p.d. across the 4.7 k $\Omega$  resistor in the circuit in **Fig. 1.1** is about 4 V, assuming that the cell has zero internal resistance.

(b) A student changes the circuit as shown in Fig. 1.2

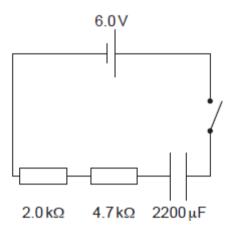


Fig. 1.2

Show that the time constant of the circuit is about 15 s.


[2]

[2]

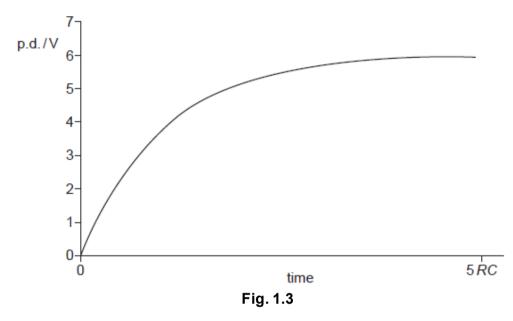(c) The graph in **Fig. 1.3** shows how the p.d. across the capacitor varies with time up to 5 *RC*.

Add a line to the graph that shows how the p.d. across the **4.7** k $\Omega$  **resistor** varies $\Omega$  with time.

Add another line to show how the p.d. across the **2.0** k $\Omega$  **resistor** varies $\Omega$  with time. Label the lines.



(d) Calculate the time it takes from the start of the charging for the p.d across the capacitor to reach 5.0 V.

time =..... s [4]

[2]

**Total Marks for Question Set 2: 10** 



work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible

For queries or further information please contact The OCR Copyright Team, The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge