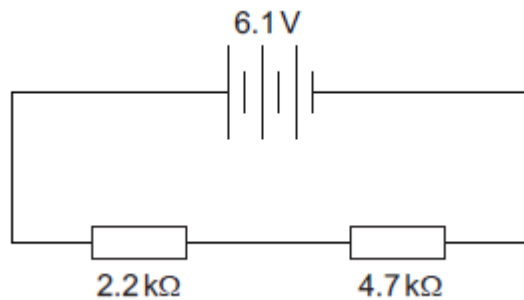


## **A level Physics B**

**H557/02** Scientific literacy in physics

### **Question Set 14**

- 1 (a) **Fig. 1.1** shows a potential divider circuit using cells with very low internal resistance.



**Fig. 1.1**

Show that the potential difference across the 4.7 kΩ resistor is 4.2 V to 2 significant figures.


[1]

- (b) An analogue voltmeter connected across the 4.7 kΩ resistor reads 3.2 V.

Show that the resistance of the voltmeter is about 5 kΩ.

[3]

- (c) A cell is made by inserting a zinc strip and a copper strip into a potato. When the same analogue voltmeter is connected to the cell as shown in **Fig. 1.2**, it registers a potential difference of 0.50 V.

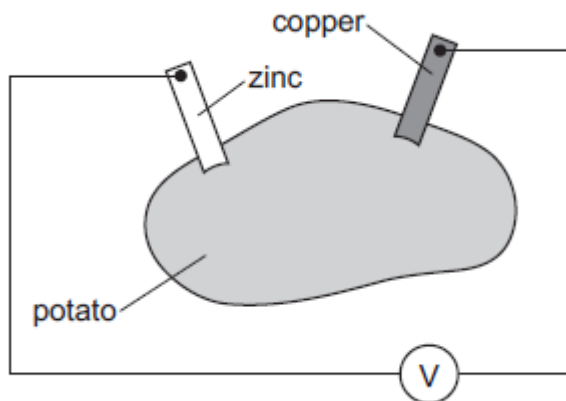

**Fig. 1.2**

- (i) Using your answer to (b), calculate the current in the circuit.

current = ..... A [1]

- (c) (ii) When a digital voltmeter of resistance 1.0 MΩ replaces the analogue voltmeter in **Fig. 1.2**, it registers a potential difference of 0.93 V. Use the readings from the two meters to calculate an estimate for the internal resistance of the potato, stating any assumptions you make.

internal resistance = ..... Ω [3]

**Total Marks for Question Set 14: 8**

---

# OCR

Oxford Cambridge and RSA

## **Copyright Information**

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website ([www.ocr.org.uk](http://www.ocr.org.uk)) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact The OCR Copyright Team, The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge