

## A level Physics B

H557/03 Practical skills in physics

## **Question Set 1**

This question is about using a thermistor in a temperature sensing circuit. The graph, **Fig. 1.1**, shows how the resistance *R* of a thermistor varies with temperature *T*.

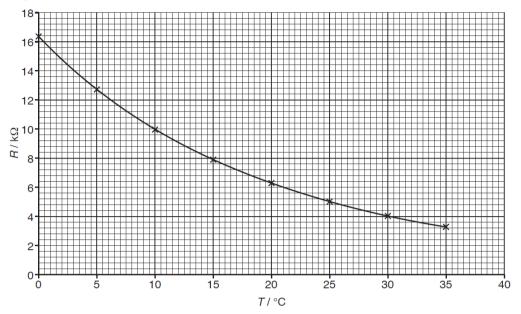


Fig. 1.1

The resistance of the thermistor can be measured with a multimeter on the resistance range. Suggest how you might vary and measure the temperature of the thermistor so that the data for **Fig. 1.1**, could be collected.

[2]

(b) The thermistor is used in the potential divider shown in Fig. 1.2.

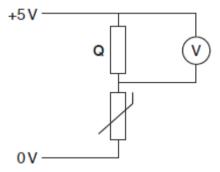


Fig. 1.2

Suggest why the voltmeter is connected across the fixed resistor  ${\bf Q}$  rather than the thermistorin this temperature sensing circuit.

[1]

(c) Readings of voltage  $V_{\rm out}$  against temperature T are recorded using an analogue voltmeter. The uncertainty in the voltmeter readings is  $\pm$  0.1 V and the uncertainty in the temperature readings is  $\pm$  1 °C. The data is shown in **Fig. 1.3** in the form of a graph.

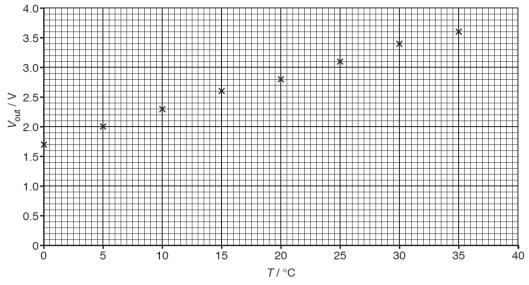


Fig. 1.3

It is suggested that  $V_{\text{out}}$  varies linearly with T.

(i) By adding uncertainty bars to **Fig. 1.3**, use the graph to show that this is true over the temperature range tested. State your reasoning.

[3]

(ii) Explain how you could calibrate the analogue voltmeter scale to read temperature directly.

[2]

[6]

(d)\* Discuss the effect of changing the fixed resistor **Q** to a higher **and** a lower value on the performance of the temperature sensing circuit over the range of temperatures 0 – 35 °C. Use data from **Fig. 1.1** and **Fig. 1.3** to perform calculations to support your ideas.

Total Marks for Question Set 1: 14



work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible

For queries or further information please contact The OCR Copyright Team, The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge