

## AS Level Physics A

H156/02 Depth in physics

**Question Set 4** 

Some houses are heated by "night storage heaters" which use cheap electricity between the hours of midnight and 7.00 am.

Fig. 4.1 shows a circuit diagram of three identical 230 V, 3.5 kW storage heaters connected to a 230 V mains power supply of negligible internal resistance.



- (a) (i) Show that the resistance of each heating element is about  $15\Omega$  when the heater is operating at 230 V.
  - (ii) The heating element is constructed from a metallic wire of resistivity  $1.6 \times 10^{-6}$   $\Omega$ m. The radius of the wire is 0.55 mm.

Determine the length L of the metallic wire in one heating element.

*L* = ...... m [3]

[1]

[2]

(iii) State and explain whether the heater obeys Ohm's law.

(b) The cost of 1 kW h of energy is 7.6 pence.

Calculate the cost of using the three storage heaters between midnight and 7.00am every night for one week.

(c) A student monitors the temperature in a room by using a potential divider circuit containing a negative temperature coefficient (NTC) thermistor. The student sets up the circuit shown in Fig. 4.2.



The battery has an e.m.f. of 6.0 V and negligible internal resistance.

(i) When the temperature of the thermistor is 12 °C the thermistor has a resistance of  $6.8 \,k\Omega$ . The resistance of the variable resistor is set to a value of  $1.4 \,k\Omega$ . Calculate the reading V on the voltmeter.

V = ...... V

- [2]
- (ii) Explain how the reading on the voltmeter will change when the temperature of the thermistor increases.

## **Total Marks for Question Set 4: 14**

[4]



## **Copyright Information**

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact The OCR Copyright Team, The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge