

GCSE Physics A (Gateway)





J249/01 Physics A P1-P4 and P9 (Foundation Tier)

Question Set 27

Multiple Choice Questions

P3: Electricity


1 Which symbol is used to show an LDR?

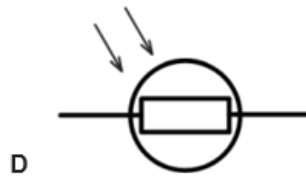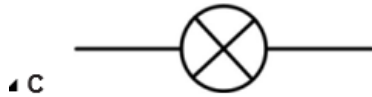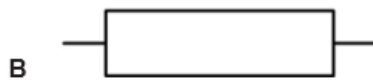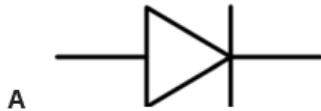

Your answer

[1]

2 Look at the circuit diagram.

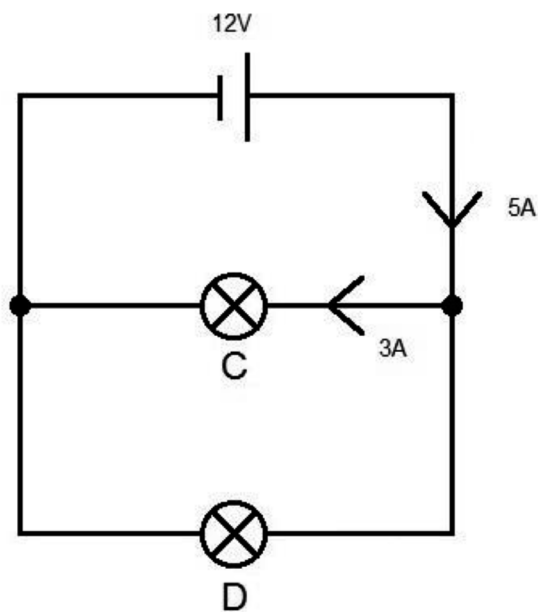

resistance = potential difference \div current

Calculate the resistance of bulb D.

A 2 Ω

B 4 Ω

C 6 Ω

D 8 Ω

Your answer


[1]

- 3 Which voltage is the maximum voltage made when **four** 1.5V cells are connected in **series**?
- A 0V
 - B 1.5V
 - C 3.0V
 - D 6.0V

Your answer

[1]

- 4 This is a circuit.




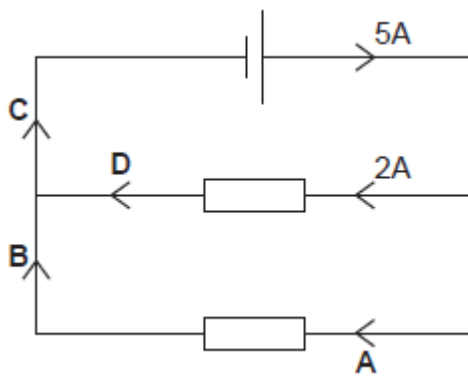


Which letter **A**, **B**, **C** or **D** shows the part of the circuit that carries a current of 2A?

Your answer

[1]

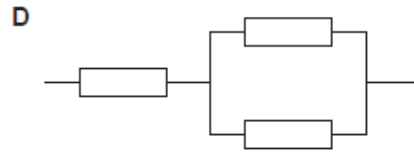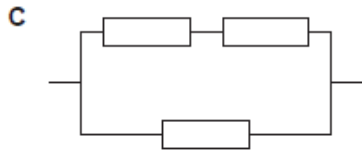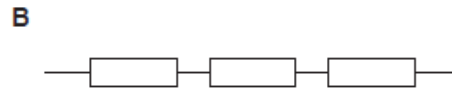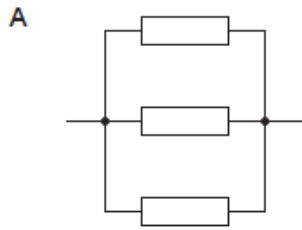5 A student has 3 identical resistors. She arranges them in four different ways.



Which arrangement has the **most** resistance?

Your answer

[1]

6 Static electricity can be produced when two materials are rubbed together.

Which two types of material could cause static electricity to be produced?





- A Two insulators
- B Two conductors
- C One insulator and one conductor
- D A metal and a non-metal

Your answer

[1]

7 A student investigates how current and potential difference vary in different components.

Look at the graphs of her results.

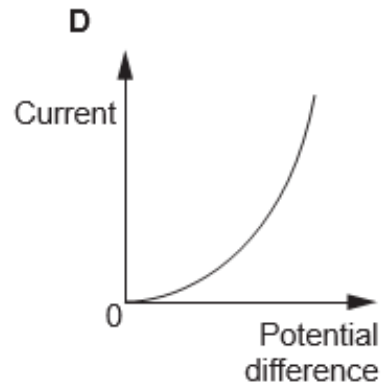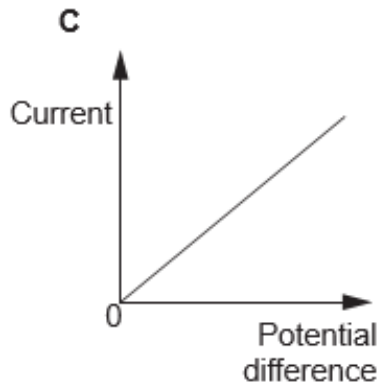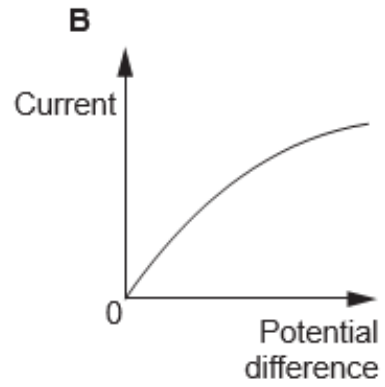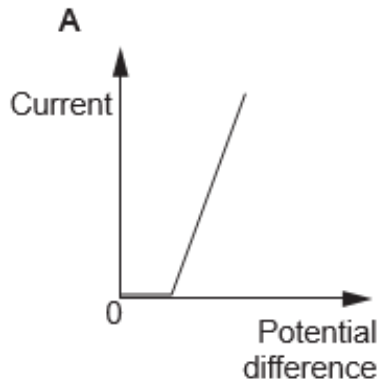

Which graph shows a filament lamp?


Your answer

[1]


8 A student sets up four different circuits. He uses identical lamps and the same cell.

Look at the diagrams of his circuits.


A

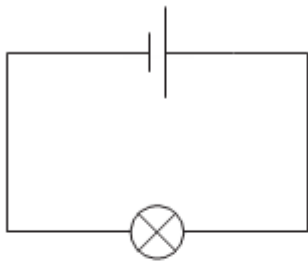


B

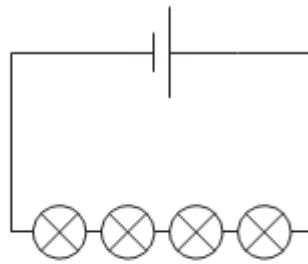

C

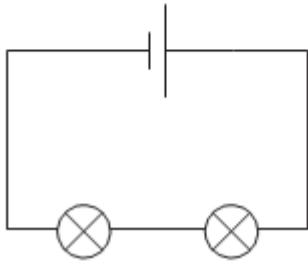

D

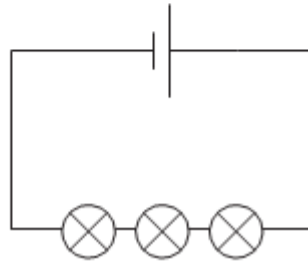

Which circuit has the brightest lamp(s)?

Your answer

[1]

9 What conditions are needed for charge to flow?

- A A source of potential difference and two lamps.
- B A complete circuit and two lamps.
- C A complete circuit and a source of potential difference.
- D A complete circuit and a source of resistance.

Your answer

[1]

Total Marks for Question Set 27: 9

Equations in physics

$$(\text{final velocity})^2 - (\text{initial velocity})^2 = 2 \times \text{acceleration} \times \text{distance}$$

$$\text{change in thermal energy} = \text{mass} \times \text{specific heat capacity} \times \text{change in temperature}$$

$$\text{thermal energy for a change in state} = \text{mass} \times \text{specific latent heat}$$

$$\text{energy transferred in stretching} = 0.5 \times \text{spring constant} \times (\text{extension})^2$$

$$\text{potential difference across primary coil} \times \text{current in primary coil} = \text{potential difference across secondary coil} \times \text{current in secondary coil}$$

OCR

Oxford Cambridge and RSA

Copyright Information

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact The OCR Copyright Team, The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge