

Gateway Science Physics A J249/01 Physics A P1-P4 and P9 (Foundation Tier)

Question Set 22

22		A student finds a resistor which has no markings on it.			
		The student uses a voltmeter, an ammeter and a cell to find the resistance of the resistor.			
	(a)	Draw a circuit diagram to show how the student could set up this apparatus to find the resistance of the resistor.			
			[3]		
	(b)	In the experiment the current is 0.15 A and the potential difference is 2.0 V.	L-J		
		potential difference = current × resistance			
		potential difference = current × resistance Calculate the resistance of the unknown resistor.			
		Calculate the resistance of the unknown resistor.			
		Calculate the resistance of the unknown resistor. Show your working.			
		Calculate the resistance of the unknown resistor. Show your working.			
		Calculate the resistance of the unknown resistor. Show your working.			
		Calculate the resistance of the unknown resistor. Show your working. Record your answer to 3 significant figures.	[3]		
		Calculate the resistance of the unknown resistor. Show your working. Record your answer to 3 significant figures.	[3]		

(c) The student repeats the experiment with different potential differences and currents.

Look at the results.

Potential difference (V)	Current (A) (Attempt 1)	Current (A) (Attempt 2)	Current (A) (Attempt 3)	Mean current (A)
2.0	0.15	0.14	0.16	0.15
4.0	0.31	0.31	0.31	0.31
6.0	0.44	0.44	0.38	0.44
8.0	0.60	0.62	0.58	0.60
10.0	0.74	0.75	0.73	0.74

There is an anomaly in the results.

(i) Write down the anomaly from the table.

(ii) How did the student deal with the anomaly?

[1]

[1]

Total Marks for Question Set 22: 8



OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department

For queries or further information please contact The OCR Copyright Team, The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

opportunity.

of the University of Cambridge