

GCSE Physics B (Twenty First Century Science)

J259/01 Breadth in Physics (Foundation Tier)

Question Set 15

Multiple Choice Questions



(a)

Which **two** parts of the circuit **must** be present for a current to flow? Tick (\checkmark) **two** boxes.

The ammeters, to measure the current

The cell, to provide a potential difference

The lamp, to provide resistance

The wires, to make a complete circuit

\checkmark	
\checkmark	

(b) Amaya measured the current in the lamp as 1.5A. The potential difference across the lamp is 3.3 V.

Calculate the resistance of the lamp.

Use the equation: resistance = potential difference ÷ current

$$R = \frac{\sqrt{2}}{2} = \frac{3 \cdot 3}{1 \cdot 5} = 2 \cdot 2 \cdot 2 \quad [2]$$

Resistance = $\frac{2}{2} \cdot 2 \cdot 2 \quad [2]$

(c) Amaya and Li compare their results. The table shows the readings on the ammeters **P** and **Q**.

	Reading on ammeter P (A)	Reading on ammeter Q (A)
Amaya	1.5	1.5
Li	1.4	1.5

(i) Who got the expected results?

Amaya	\checkmark
Li	

Explain your answer.

[2]

[1]

[1]

Current should be the same everywhere in a series circuit

(ii) Amaya thinks her results are different to Li's because something is wrong with the ammeters.

Suggest how Amaya could check if there is something wrong with the ammeters.

Use different ammeters and see if you get the same results

Total Marks for Question Set 15: 6



Copyright Information

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact The OCR Copyright Team, The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge