


GCSE Physics B (Twenty First Century Science)

J259/04 Depth in physics (Higher Tier)

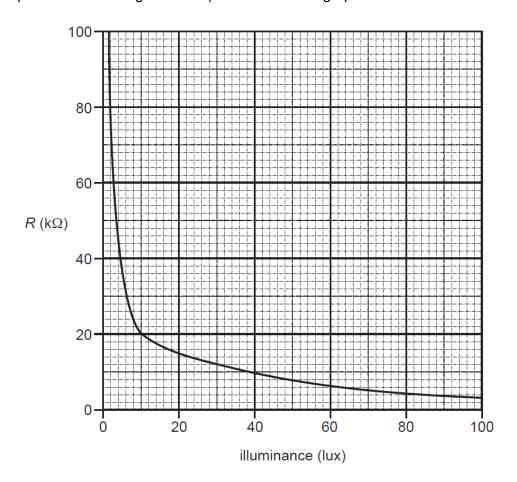Question Set 1

Multiple Choice Questions

- **1** This question is about using an LDR (light-dependent resistor) to measure light intensity.
 - (a) The resistance *R* of an LDR varies with illuminance (the amount of light energy per unit area hitting a surface) as shown in the graph.



(i) Which of the following statements correctly describes this variation?Tick (✓) one box.

The resistance is directly proportional to the illuminance.

The resistance and the illuminance have a positive correlation.

As the illuminance increases, the change in resistance becomes less and less.

The resistance is greater at 80 lux than at 20 lux.


(ii) Use the graph to estimate the change in resistance of the LDR when the illuminance increases from 10 lux to 70 lux.

Change in resistance = $k\Omega$ [2]

[1]

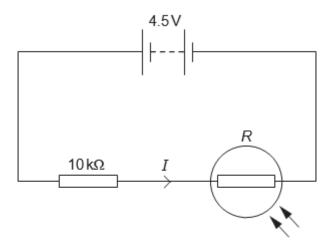(b) The LDR is connected in series with a fixed resistor of resistance $10\,k\Omega$ and a 4.5 V battery.

The **total** resistance at 30 lux is 22000Ω .



(i) Calculate the current in the circuit.

	Current = A	[3]
(ii)	Calculate the potential difference across the fixed $10k\Omega$ resistor when the	

illuminance is 30 lux.

Total Marks for Question Set 1: 12



OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department

For queries or further information please contact The OCR Copyright Team, The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

opportunity.

of the University of Cambridge