

# OCR Computer Science AS Level

## 1.4.3 Boolean Algebra

### Concise Notes



**Specification:**

**1.4.3 a)**

- Define problems using Boolean logic

**1.4.3 b)**

- Manipulate Boolean expressions
  - Karnaugh maps to simplify Boolean expressions





**1.4.3 c)**

- Use logic gate diagrams and truth tables



## Logic Gate Diagrams and Truth Tables

- Problems can be defined using [Boolean logic](#) in [Boolean equations](#)
- A Boolean equation can equate to either True or False
- Four operations are used:

Operation	Conjunction	Disjunction	Negation	Exclusive Disjunction
Logic gate				
	AND	OR	NOT	XOR
Symbol	$\wedge$	$\vee$	$\neg$	$\underline{\vee}$

### Truth tables

- A table showing [every possible permutation](#) of inputs to a logic gate and the corresponding output
- Inputs are usually labeled A, B, C etc
- 1 represents True, 0 represents False

### Conjunction (AND)

- Applied to two [literals](#) (or inputs) to produce a single output
- Can be thought of as applying [multiplication](#) to its inputs
- Truth table shows  $A \wedge B = Y$

AND

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

### Disjunction (OR)

- Operates on two literals and produces a single output
- Can be thought of as applying [addition](#) to its inputs
- As long as one input is True then the output is True
- Truth table shows  $A \vee B = Y$

OR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1



### Negation (NOT)

- Only applied to **one literal**
- Reverses the truth value of the input
- Truth table shows  $\neg A = Y$

#### NOT

A	Y
0	1
1	0

### Exclusive Disjunction (XOR)

- Also known as **exclusive OR**
- Similar to disjunction but differs when both inputs are True
- Only outputs True when **exactly** one input is True
- Otherwise output is False
- Truth table shows  $A \vee B = Y$

#### XOR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

### Combining Boolean Operations

- Boolean equations are made by combining Boolean operators
- This is done in the same way that standard mathematical operators are combined
- Every boolean equation can be represented with a truth table

### Manipulating Boolean Expressions

- Sometimes a long Boolean expression has the **same truth table** as another, shorter expression
- It tends to be **desirable to use the shorter versions**
- There are a variety of methods which can be used to simplify expressions



## Karnaugh Maps

- Can be used to simplify Boolean expressions
- The tables are filled in corresponding to the expression's truth table
- Can be used for a truth table with **two**, **three** or **four variables**
- It's important that the values in the columns and rows are written using **Gray code**
- Columns and rows only ever differ by **one bit**, including wraparound
- To simplify a Boolean expression:
  - First write your truth table as a Karnaugh map
  - Then highlight all of the 1s in the map with a rectangle
  - The larger the rectangle you can highlight at once the better
  - Only groups of 1s with edges equal to **a power of 2** (1, 2 or 4 in a row) can be highlighted, wraparound is included
  - Remove variables which change within these rectangles from the expression
  - Keep variables which do not change, but negate to become True if required

