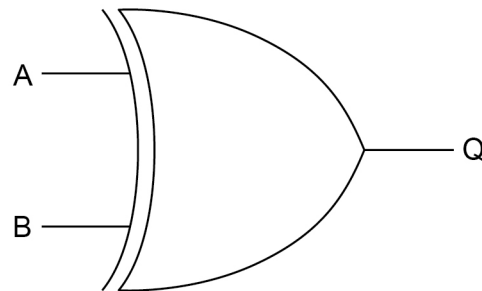


0 1 . 1 **Figure 1** shows a logic gate symbol.

Write the name of the logic gate underneath the figure.

[1 mark]


Figure 1



Answer: _____

0 1 . 2 **Figure 2** shows a logic gate symbol.

Figure 2

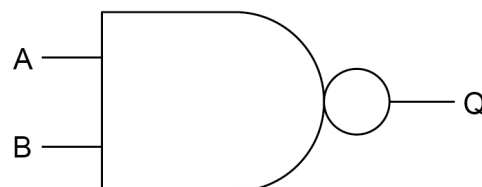

Complete the truth table below for the logic gate shown in **Figure 2**.


[1 mark]

A	B	Q
0	0	
0	1	
1	0	
1	1	

0	1	3
---	---	---

Represent the Boolean equation $\bar{A} + \bar{B} \cdot C$ as a logic circuit by drawing a diagram of it in the space below.

[3 marks]

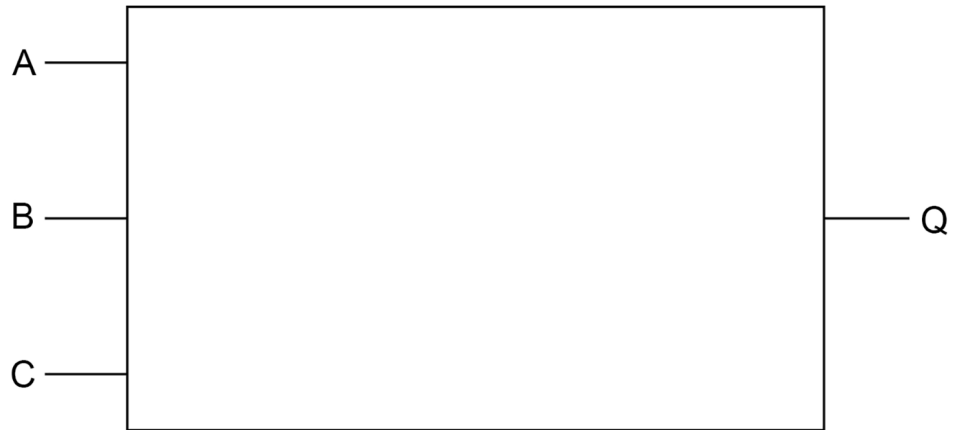

0 2 . 1

State the name of the logic gate represented by the truth table shown in **Figure 1**.
[1 mark]

Figure 1

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

Answer: _____

0 2 . 2

A factory has a machine for filling bottles on a conveyor belt.

- Q represents the signal to move the conveyor belt on. When Q is set to true the belt will move on.
- A is a sensor which outputs true if a bottle is present.
- B is a sensor which outputs true if a bottle is full.
- C is a sensor which outputs true if a bottle is correctly positioned.
- D is a sensor which outputs true if the next section has a bottle in it.

The conveyor belt is able to move if both of these conditions are true:

- a bottle is full and correctly positioned or there is no bottle present
- there is no bottle in the next section.

In the box below, draw a logic circuit for the machine.

[3 marks]



0	2
---	---

 .

3

De Morgan's laws can be applied to enable a combination of logic gates to be replaced by a single gate that produces the same output.

What single gate could replace the combination of gates in the expression $\overline{\overline{A} \cdot \overline{B}}$?

[1 mark]

0 **3** **1** Complete the truth table for A NAND B.


[1 mark]

A	B	A NAND B
0	0	
0	1	
1	0	
1	1	

0 3 . 2 A XOR B can be implemented as a logic circuit without using an XOR gate.

Using **only** AND, OR and NOT gates draw a circuit that will produce an output **Q** which is logically equivalent to **A XOR B**.


[3 marks]

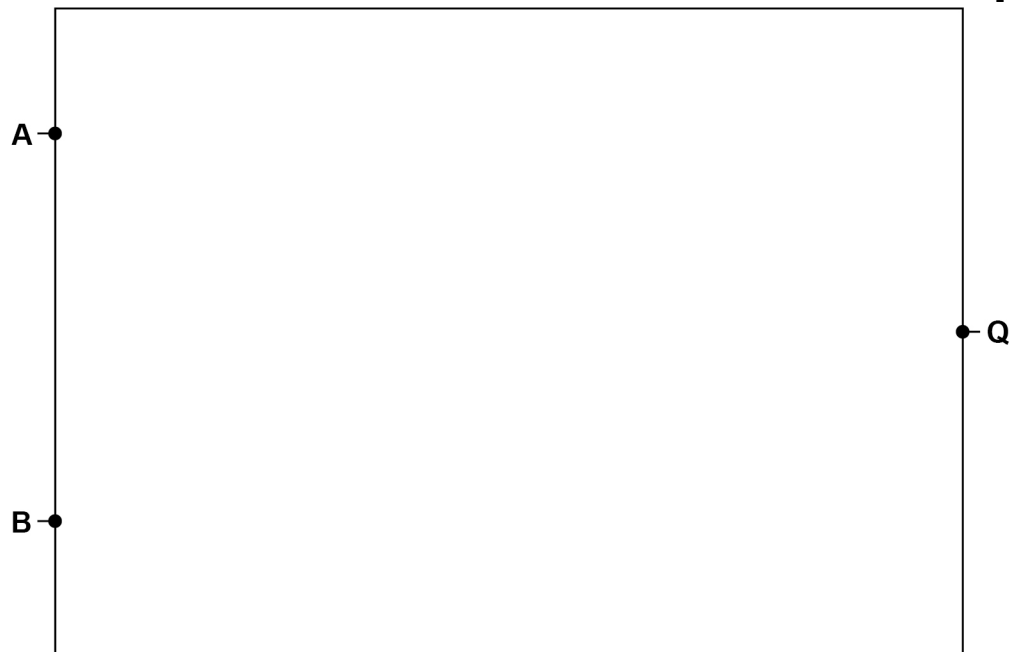

0 4 . 1State which logic gate has the truth table shown in **Figure 4**.**[1 mark]****Figure 4**

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

Answer _____

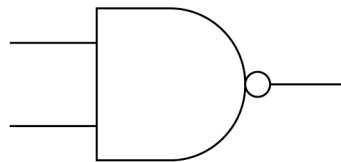0 4 . 2State the logic gate that is represented by the symbol shown in **Figure 5**.**[1 mark]****Figure 5**


Answer _____

0 4 . 3

Draw the logic circuit for the following Boolean expression.

$$Q = \overline{\overline{A} \cdot \overline{B}} + C$$

[2 marks]

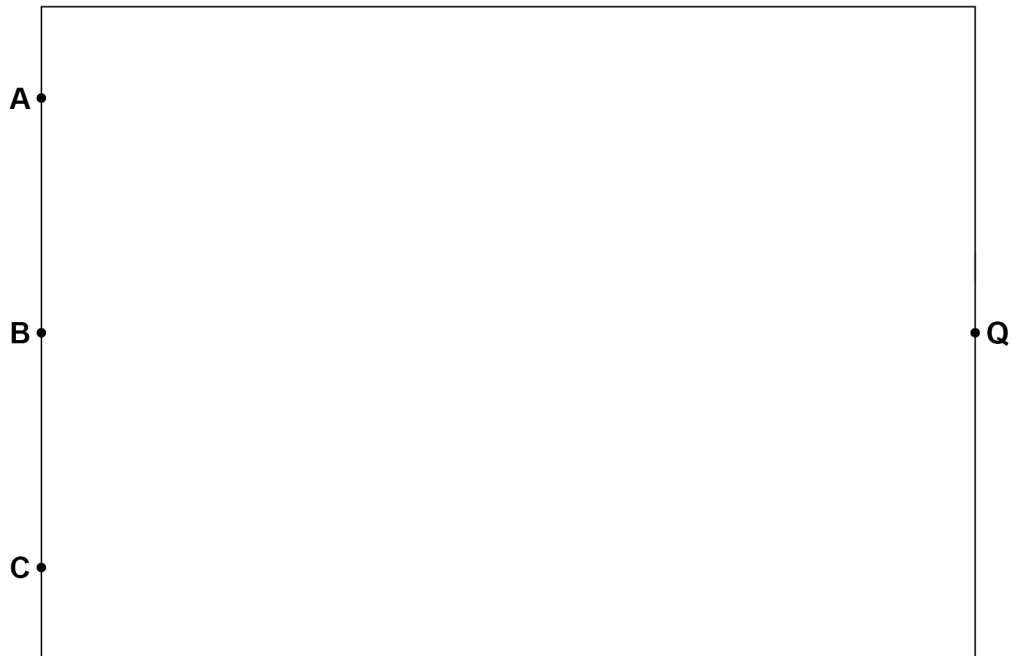

0 4 . 4

Complete the truth table below.

A	B	\bar{B}	$(A + \bar{B})$	$(A + \bar{B}) \cdot B$
0	0			
0	1			
1	0			
1	1			

Using the final column, give a simplified Boolean expression for

$$(A + \bar{B}) \cdot B$$


[3 marks]

Answer _____

05.1

Figure 3 shows a circuit diagram.

Figure 3

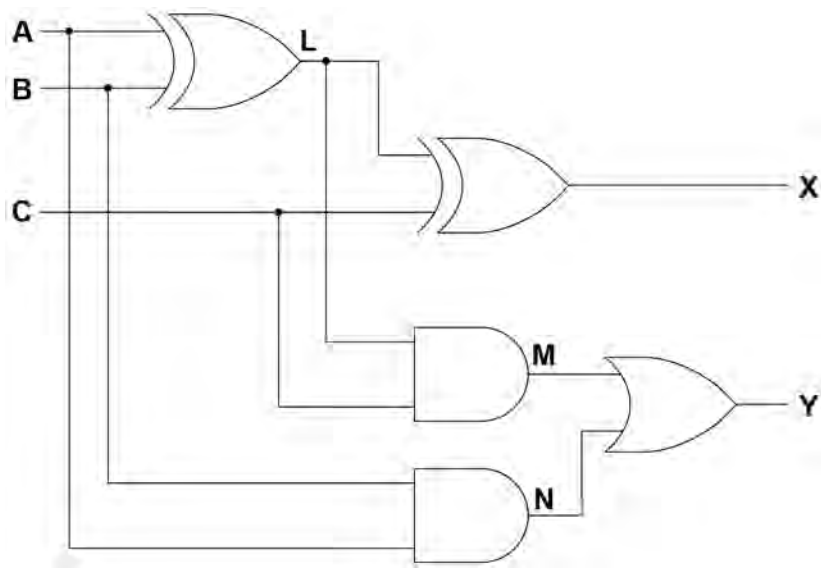

Complete the truth table below for the circuit shown in **Figure 3**.

[3 marks]

A	B	C	L	M	N	X	Y
0	0	0		0		0	
0	0	1		0		1	
0	1	0		0		1	
0	1	1		1		0	
1	0	0		0		1	
1	0	1		1		0	
1	1	0		0		0	
1	1	1		0		1	

0	5	.	2
---	---	---	---


 Using **Figure 3**, write a Boolean expression for output **Y** in terms of inputs **A**, **B** and **C**.
[2 marks]

Y = _____

06.1

Figure 2 shows the symbol for a logic gate.

Figure 2

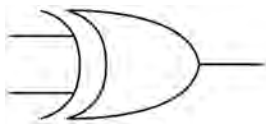


State the name of the logic gate shown in **Figure 2**. [1 mark]

06.2


Figure 3 shows a logic circuit.

Figure 3

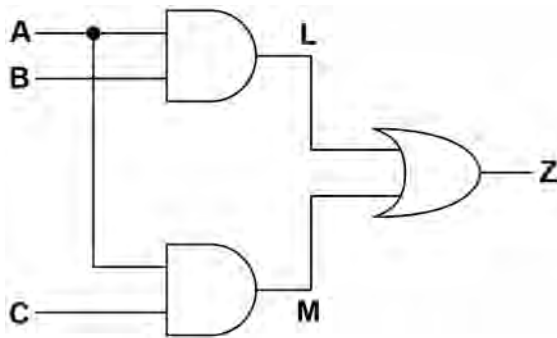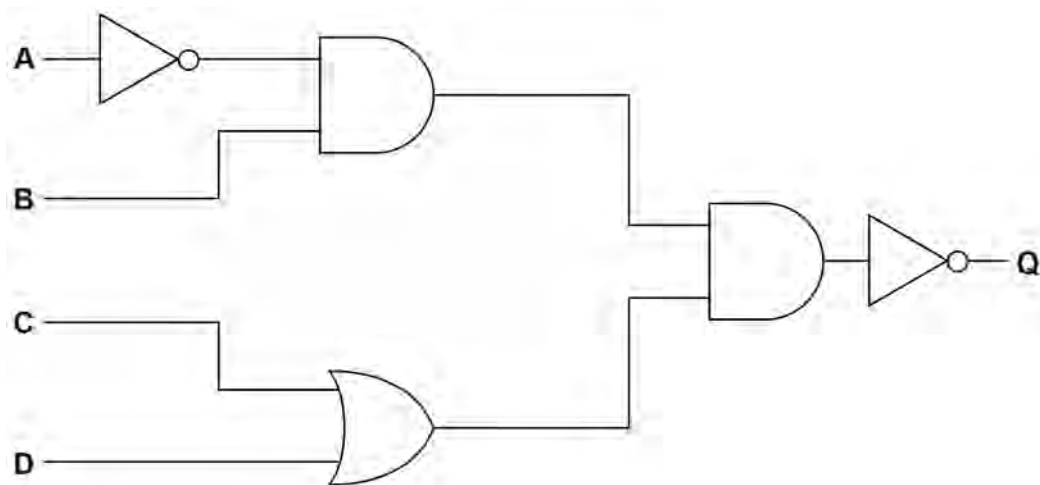

Complete the truth table for the logic circuit in **Figure 3**. [2 marks]

A	B	C	L	M	Z
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

0 6 . 3**Figure 4** shows a logic circuit.**Figure 4**Write a Boolean expression for **Q**.**[3 marks]**

Using the rules of Boolean algebra, simplify the following expression.

You **must** show your working.

[illegible]

Final answer