

# **CAIE Computer Science IGCSE**

## **10 - Boolean logic**

### **Advanced Notes**

This work by [PMT Education](https://www.pmt.education) is licensed under [CC BY-NC-ND 4.0](https://creativecommons.org/licenses/by-nc-nd/4.0/)





**AND**

The AND gate has two inputs, labelled A and B in the truth table below. The AND gate only outputs TRUE (1) when both inputs are TRUE, otherwise it outputs FALSE.

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

**OR**

OR only outputs FALSE when both inputs are FALSE. When one or more of the gate's inputs are TRUE, the logic gate outputs TRUE.

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1




## XOR (EOR)

The XOR gate's full name is exclusive or, hence, it's sometimes called EOR instead of XOR. It **outputs TRUE when exactly one of its inputs is TRUE**. The gate's truth table is the same as the OR gate with the exception of the last line in which FALSE is output with two TRUE inputs.

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0
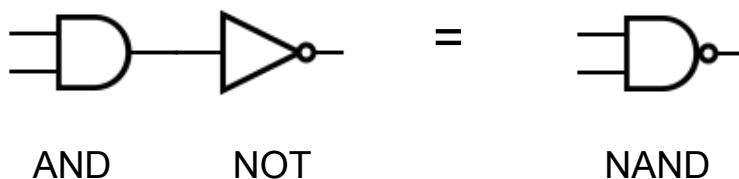
## NAND

NAND is short for **NOT AND**. The NAND gate is actually a **combination of two gates** which we've already covered, the NOT gate and the AND gate.




The NAND gate's truth table is the same as the AND gate's truth table, but the output is **reversed**. This leads to a logic gate that outputs true as long as at least one of its inputs isn't true.

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0


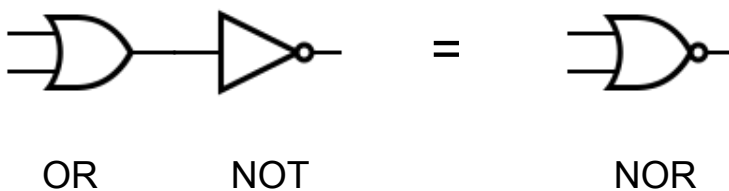
## NOR

NOR, short for **NOT OR**, is a **combination** of the two logic gates NOT and OR.




Therefore, the NOR gate's truth table is the same as the OR gate's table, just with the output **reversed**. This leads to a logic gate that outputs true if neither of its inputs are true, but false otherwise.

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0


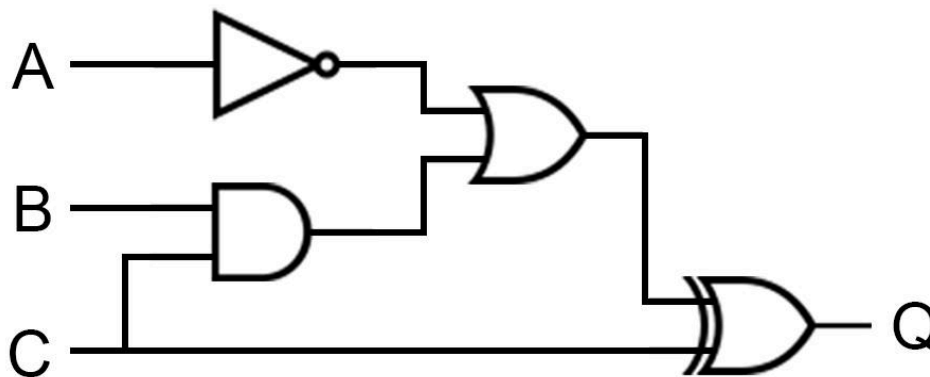
## Combining Logic Gates

Within a processor, logic gates are **combined** to form **logic circuits**. These can perform **more complex operations** like binary addition. In exam questions, logic circuits will be limited to a maximum of three inputs and one output.



The logic circuit above combines **four logic gates** and can be represented using the following logic statement:

$$Q = (C \text{ XOR } ((\text{NOT } A) \text{ OR } (B \text{ AND } C)))$$

In order to create a truth table for this circuit, we first need to fill in **all the possible permutations of inputs** like so:

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1



Next, we **add columns for each of the elements** that make up the logical expression such as (**B AND C**). This will make it easier for us to **combine them** to form the final expression.

<i>A</i>	<i>B</i>	<i>C</i>	<b>B AND C</b>	NOT <b>A</b>	((NOT <b>A</b> ) OR ( <b>B AND C</b> ))	( <b>C XOR ((NOT A) OR (B AND C))</b> )
0	0	0	0	1	1	1
0	0	1	0	1	1	0
0	1	0	0	1	1	1
0	1	1	1	1	1	0
1	0	0	0	0	0	0
1	0	1	0	0	0	1
1	1	0	0	0	0	0
1	1	1	1	0	1	0

Once the column in the truth table for the **finished expression** is complete, the columns used for working **can be removed** and the final column (representing the output) **renamed Q**.

<i>A</i>	<i>B</i>	<i>C</i>	<i>Q</i>
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

