

# OCR Computer Science GCSE

## 2.4 – Boolean logic

### Advanced Notes

This work by [PMT Education](https://www.pmt.education) is licensed under [CC BY-NC-ND 4.0](https://creativecommons.org/licenses/by-nc-nd/4.0/)



## 2.4.1 Boolean logic

### What is Boolean logic?

Boolean logic is a form of algebra where all values are either TRUE (1) or FALSE (0). It is used in computers to control [decision-making](#) and [logical operations](#).

Computers use Boolean logic in:

- Programming conditions
- Logic gates and circuits
- Searching and filtering

### Truth tables

A truth table is used to show the [output](#) of Boolean expressions for [all possible input combinations](#). This means that they are useful for [debugging](#) and understanding logic conditions.

### Logic gates

A computer's processor is made up of [billions of logic gates](#), components which apply [logical operations](#) to one or more [Boolean inputs](#) in order to produce a [single output](#).

Within a processor, logic gates are [combined](#) to form [logic circuits](#). These can perform [more complex operations](#) like binary addition.

### AND

- Returns **TRUE** only if **both inputs** are TRUE
- Symbol:  $A \text{ AND } B$ ,  $A \wedge B$

A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1



## OR

- Returns **TRUE** if **either** input is TRUE
- Symbol:  $A \text{ OR } B$ ,  $A \vee B$

A	B	A OR B
0	0	0
0	1	1
1	0	1
1	1	1

## NOT

- Reverses the input
- Symbol:  $\text{NOT } A$ ,  $\neg A$

A	NOT A
0	1
1	0



## Combining operators

You can combine logic gates and build expressions like:

$A \text{ AND } (B \text{ OR NOT } C), A \wedge (B \vee \neg C)$

## Order of precedence

Algebraic operations have an [order of precedence](#), meaning that some operations must be [applied before others](#). You may have met BODMAS in Mathematics, this is the same idea.

Operator	Precedence
Brackets	Highest
NOT	.
AND	.
OR	Lowest

For example, the expression  $B \text{ OR NOT } C \text{ AND } A$  would actually be carried out in the order  $B \text{ OR } ((\text{NOT } C) \text{ AND } A)$ .

## Logic circuit symbols

Each of the three required logic gates has an [internationally recognised](#) symbol which you should learn. The symbols have inputs on the left and outputs on the right.



NOT



AND



OR


These symbols can be combined to form [logic circuit diagrams](#).



## Logic circuit diagrams

Logic gates can be **combined** to form **more complex** circuits. You may be asked to draw or interpret a logic circuit involving **multiple logic gates**.

### Example 1 - combining two AND gates

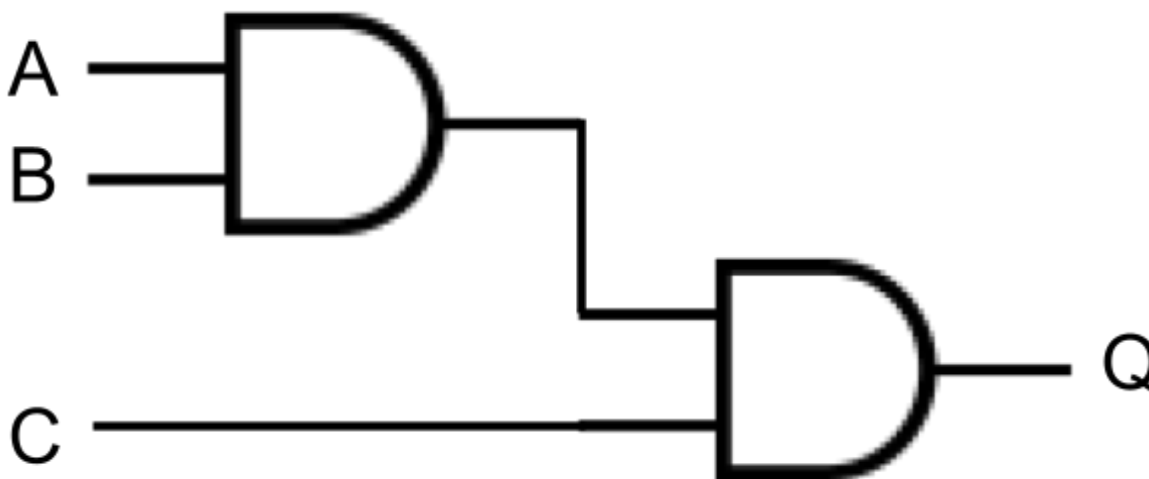

In this example, the output Q is TRUE only if A, B AND C are all TRUE.


The Boolean expression from this logic circuit is A AND B AND C.

You are also expected to be able to fill out truth tables for logic gate diagrams, the following table represents the diagram above:

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


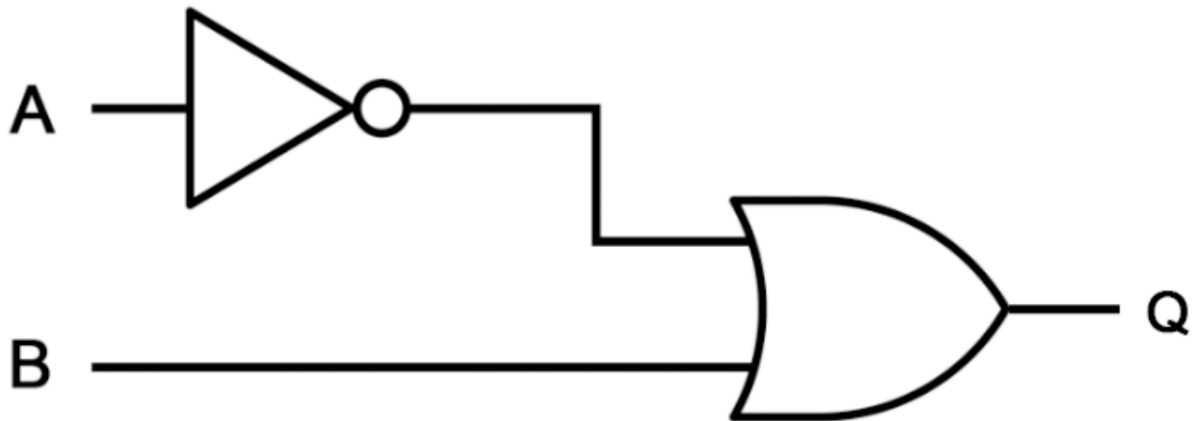
### Example 2 - combining NOT and OR gates



In this example, the output Q is TRUE when either A is FALSE, B is TRUE, or both, in one instance.

You can visualise this in the truth table below:

A	B	Q
0	0	1
0	1	1
1	0	0
1	1	1

