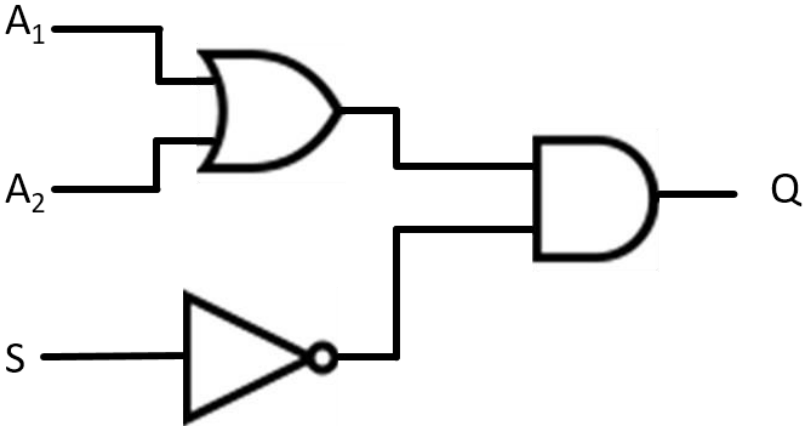
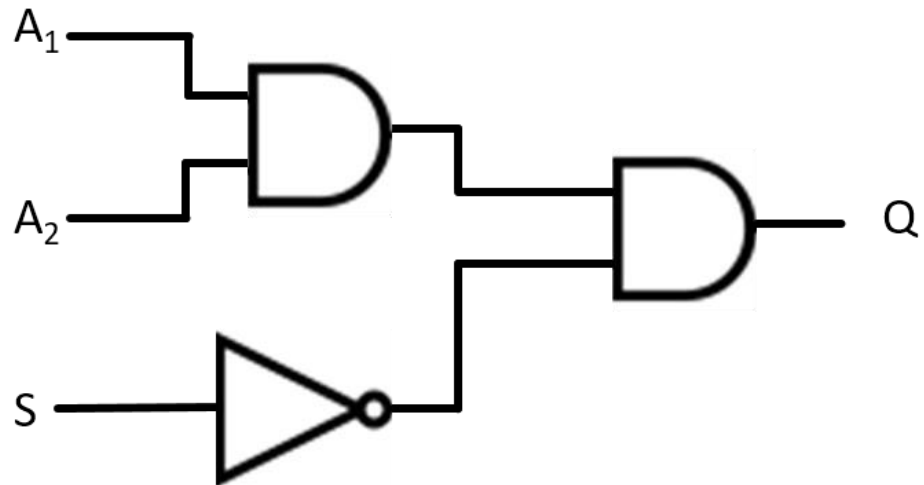
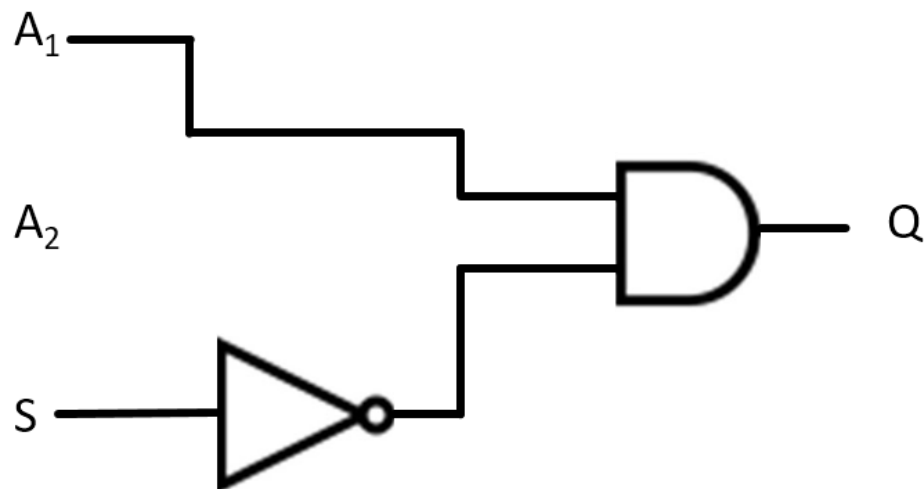
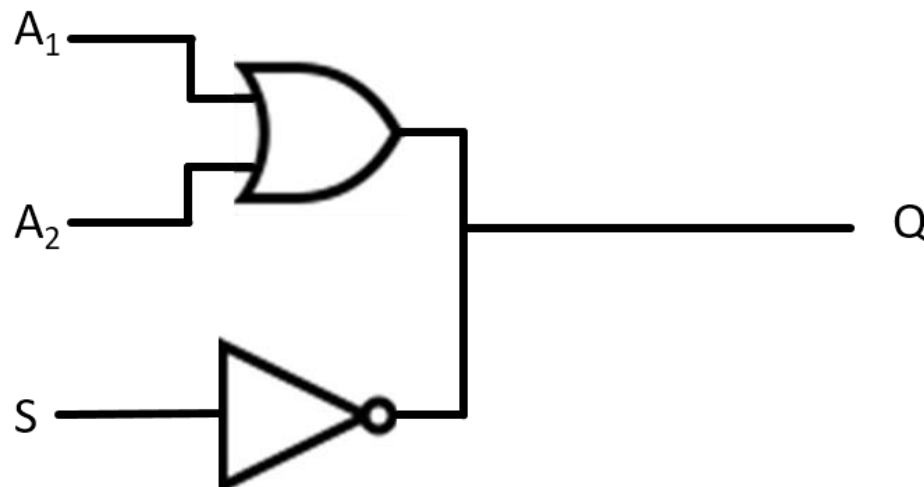


01	1	<p><b>Mark is for AO1 (understanding)</b></p> <p>Only reward if column <b>A AND B</b> is completely correct;</p> <table><tr><th>A</th><th>B</th><th>A AND B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> <p><b>A.</b> F,F,F,T//false, false, false, true//off, off, off, on <b>I.</b> Case and minor spelling mistakes</p>	A	B	A AND B	0	0	0	0	1	0	1	0	0	1	1	1	1
A	B	A AND B																
0	0	0																
0	1	0																
1	0	0																
1	1	1																


Question	Part	Marking guidance	Total marks
----------	------	------------------	-------------


01	2	<p><b>3 marks for AO2 (apply)</b></p> <p>Max 2 marks if not fully correct (the fully correct answer is given in example 1).</p> <p>Mark A if <math>A_1</math> and <math>A_2</math> are the inputs to an OR gate; Mark B if S is the only input into a NOT gate; Mark C if Q has a single output connection from an AND gate;</p> <p><b>Example 1 (Fully correct answer)</b></p>  <p>R. Incorrect symbols</p> <p><b>See next page for partially correct answers</b></p>	3
----	---	---	---

**Example 2 (Marks B and C)****Example 3 (Marks B and C)****Example 4 (Marks A and B)**

Question	Part	Marking guidance	Total marks
02	1	<b>Mark is for AO2 (apply)</b>  NOT;	1

02	2	<b>Mark is for AO2 (apply)</b>  AND;	1
----	---	--	---

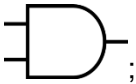02	3	<b>Mark is for AO2 (apply)</b>   ;  I. all labels	1
----	---	--	---

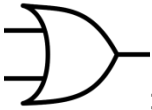02	4	<b>Mark is for AO2 (apply)</b>   ;  I. all labels	1
----	---	--	---

02	5	<p><b>3 marks for AO2 (apply)</b></p> <p>1 mark for correct column <b>X AND Y</b>; 1 mark for correct column <b>NOT X</b>; 1 mark for correct <b>OR</b> of the answers given in the column <b>X AND Y</b> and the column <b>NOT X</b> even if the answers for <b>X AND Y</b> and <b>NOT X</b> are incorrect;</p> <p>The correctly completed table is:</p> <table><tr><th>X</th><th>Y</th><th>X AND Y</th><th>NOT X</th><th>(X AND Y) OR (NOT X)</th></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td></tr></table> <p><b>A.</b> follow through from previous columns</p>	X	Y	X AND Y	NOT X	(X AND Y) OR (NOT X)	0	0	0	1	1	0	1	0	1	1	1	0	0	0	0	1	1	1	0	1	3
X	Y	X AND Y	NOT X	(X AND Y) OR (NOT X)																								
0	0	0	1	1																								
0	1	0	1	1																								
1	0	0	0	0																								
1	1	1	0	1																								

02	6	<b>Mark is for AO2 (apply)</b>  <b>D</b> A1 AND A3; <b>If more than one lozenge shaded then mark is not awarded</b>	1
----	---	--	---

Qu	Part	Marking guidance	Total marks										
03	1	<b>Mark is for AO1 (recall)</b>  AND;	1										
03	2	<b>3 marks for AO2 (apply)</b>  1 mark for one correct label; 2 marks for two correct labels; 3 marks for all correct labels; <table><tr><th>Label</th><th>Logic Gate</th></tr><tr><td>L1</td><td>NOT</td></tr><tr><td>L2</td><td>AND</td></tr><tr><td>L3</td><td>AND</td></tr><tr><td>L4</td><td>OR</td></tr></table>	Label	Logic Gate	L1	NOT	L2	AND	L3	AND	L4	OR	3
Label	Logic Gate												
L1	NOT												
L2	AND												
L3	AND												
L4	OR												

04	1	<b>Mark is for AO1 (recall)</b>  AND (gate);	1
----	---	--	---

04	2	<b>Mark is for AO1 (recall)</b>  OR (gate) ;	1
----	---	--	---

04	3	<b>Mark is for AO1 (recall)</b>  1 mark for any of the following: <ul style="list-style-type: none"> <li>• A NOT gate is used to flip/invert/switch an input</li> <li>• The output will be the opposite of the input</li> <li>• 0s become 1 <b>and</b> 1's become 0s;</li> </ul>	1
----	---	--	---

04

4

3 marks for AO2 (apply)

3

INPUTS			A AND B	C OR D	D OR E
A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	0	0
0	1	1	0	1	1
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	1	1
1	1	1	1	1	1


1 mark for column D correct  
1 mark for column E correct  
1 mark for column F correct

A. Follow through for column F based on incorrect but complete columns D or E

05

3 marks for AO2 (apply)

3

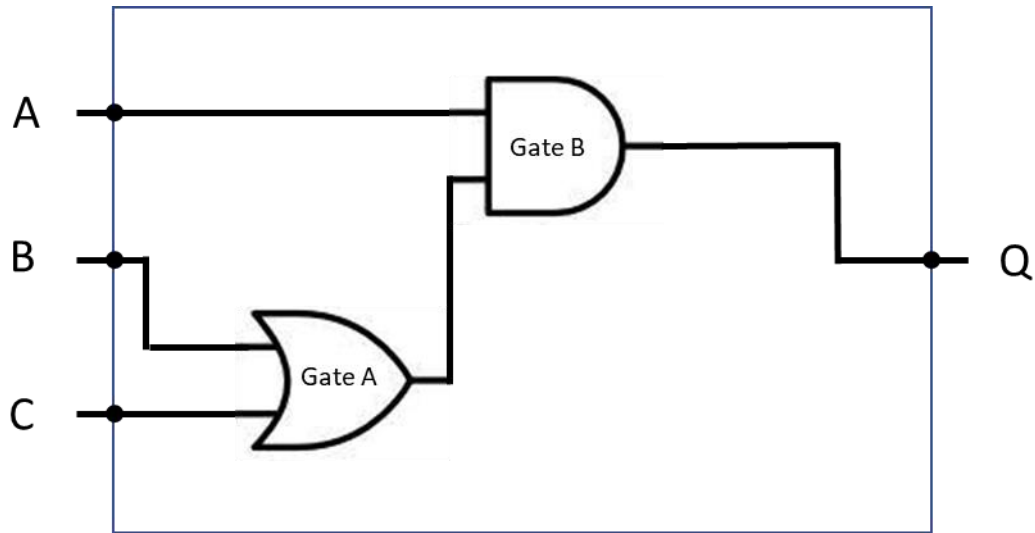

- **OR Gate**, with correct symbol used, with **TWO inputs** from B and C;
- **AND Gate**, with correct symbol used, with **TWO inputs** from A and Gate A (even if Gate A is an incorrect gate);
- Output from Gate B is the only connection to Q (even if Gate B is an incorrect gate);

Qu	Part	Marking guidance	Total marks															
06	1	<p>Mark is for AO1 (understanding)</p> <table><tr><th>A</th><th>B</th><th>A XOR B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> <p>1 mark for correct column <b>A XOR B</b>;</p> <p>A. F / FALSE / False / Off instead of 0 A. T / TRUE / True / On instead of 1 R. if correct outputs but mix of styles given eg F, T, T, 0.</p>	A	B	A XOR B	0	0	0	0	1	1	1	0	1	1	1	0	1
A	B	A XOR B																
0	0	0																
0	1	1																
1	0	1																
1	1	0																

Qu	Part	Marking guidance	Total marks
06	2	<div><div>3 marks for AO2 (apply)</div><div>Maximum of <b>two</b> marks (if not fully correct) from:</div><div><ul style="list-style-type: none"><li>• <b>D</b> is always the only input to a NOT gate with correct symbol used;</li><li>• AND gate with two correct inputs with correct symbol used;</li><li>• <b>R</b> is always the only output from a second AND gate with correct symbol used;</li></ul></div></div>	3

		<div><div>Example 1</div><div><pre>graph LR; D((D)) --&gt; NOT1[NOT]; L((L)) --&gt; AND1[AND]; W((W)) --&gt; AND1; NOT1 --&gt; AND2[AND]; AND1 --&gt; AND2; AND2 --&gt; R((R))</pre></div></div>	
--	--	--	--



Example 2

```
graph LR; D((D)) --> NOT1[NOT]; NOT1 --> C1(( )); L((L)) --> AND1[AND]; C1 --> AND1; AND1 --> AND2[AND]; W((W)) --> AND2; AND2 --> R((R));
```

Example 3

```
graph LR; D((D)) --> NOT1[NOT]; NOT1 --> C1(( )); L((L)) --> AND1[AND]; C1 --> AND1; AND1 --> AND2[AND]; W((W)) --> AND2; AND2 --> R((R));
```

R. incorrect symbols

Qu	Part	Marking guidance	Total marks
06	3	<p><b>Mark is for AO2 (apply)</b></p> <p><b>C</b> <math>(W \cdot D) + (D \cdot L) + (W \cdot L)</math> ;</p> <p><b>R.</b> if more than <b>one</b> lozenge shaded</p>	1

Qu	Part	Marking guidance	Total marks
06	4	<p><b>3 marks for AO2 (apply)</b></p> <p><math>\bar{D}.\bar{L}.W \quad // \quad W.(\bar{D} + \bar{L}) \quad // \quad (\bar{D}.W).(\bar{L}.W) \quad ;;;</math></p> <p><b>2 marks</b> if fully correct but using different notation, eg  NOT D AND NOT L AND W;;  W AND NOT (D OR L);;  (NOT D AND W) AND (NOT L AND W);;</p> <p>Maximum of <b>two</b> marks (if not fully correct) from:</p> <ul style="list-style-type: none"> <li>• <b>1 mark</b> for using Boolean operator symbols throughout the expression; (<b>for this year only</b>)</li> <li>• <b>1 mark</b> for <math>W + (\bar{D}.\bar{L})</math>;</li> <li>• <b>1 mark</b> for <math>\bar{D} + \bar{L} + W</math>;</li> <li>• <b>1 mark</b> for <math>(\bar{D} + W) + (\bar{L} + W)</math>;</li> </ul>	3


Qu	Part	Marking guidance	Total marks															
07	1	<p>Mark is for AO1 (recall)</p> <table><tr><th>A</th><th>B</th><th>A XOR B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> <p>Mark as follows:</p> <p>1 mark if column A XOR B is correctly completed;</p> <p>A. F / FALSE / False / Off instead of 0 A. T / TRUE / True / On instead of 1</p>	A	B	A XOR B	0	0	0	0	1	1	1	0	1	1	1	0	1
A	B	A XOR B																
0	0	0																
0	1	1																
1	0	1																
1	1	0																




Qu	Part	Marking guidance	Total marks
07	2	<p><b>Mark is for AO1 (understanding)</b></p> <p>AND (gate);</p> <p>I. case</p>	1

Qu	Part	Marking guidance	Total marks
07	3	<p><b>2 marks for AO2 (apply)</b></p> <p><math>A.B + C // C + A.B;;</math></p> <p><b>Mark as follows:</b></p> <p>1 mark for A.B or B.A; 1 mark for + C or C +;</p> <p>Examples of responses worth 1 mark:</p> <p>A.B.C      mark is for A.B A + B + C      mark is for + C (A.B).C      mark is for A.B (A+B) + C      mark is for + C</p> <p><b>I.</b> brackets that don't change the value of the expression <b>I.</b> Case <b>A.</b> other commonly recognised symbols such as <math>\neg \wedge \vee \sim</math></p> <p><b>R.</b> if words used (eg AND, OR, NOT etc)</p> <p><b>Max 1</b> if any errors.</p>	2

Qu	Part	Marking guidance	Total marks
----	------	------------------	-------------

08	1	<div>Mark is for AO1 (understanding)</div> <div>Only reward if column <b>A AND B</b> is completely correct;</div> <table><tr><th>A</th><th>B</th><th>A AND B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	A AND B	0	0	0	0	1	0	1	0	0	1	1	1	1
A	B	A AND B																
0	0	0																
0	1	0																
1	0	0																
1	1	1																

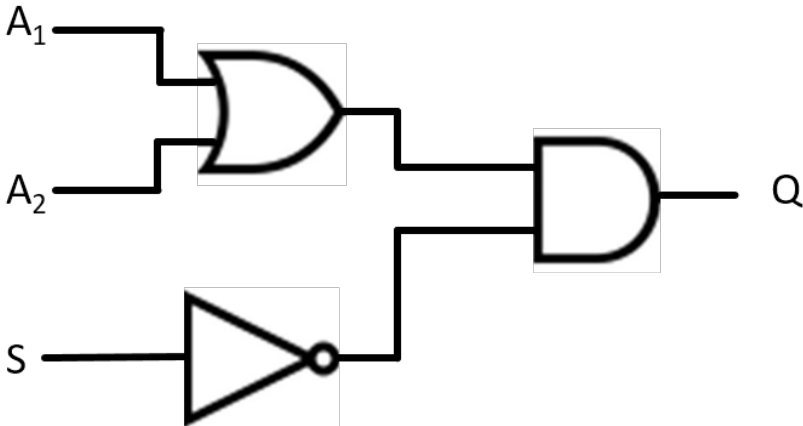08	2	<p><b>3 marks for AO2 (apply)</b></p> <p>Max 2 marks if not fully correct (the fully correct answer is given in example 1).</p> <p>Mark A if A<sub>1</sub> and A<sub>2</sub> are the inputs to an OR gate; Mark B if S is the input to a NOT gate; Mark C if the output from an AND gate is Q;</p> <p><b>Example 1 (Fully correct answer)</b></p>  <p>See next page for partially correct answers</p>	3
----	---	--	---

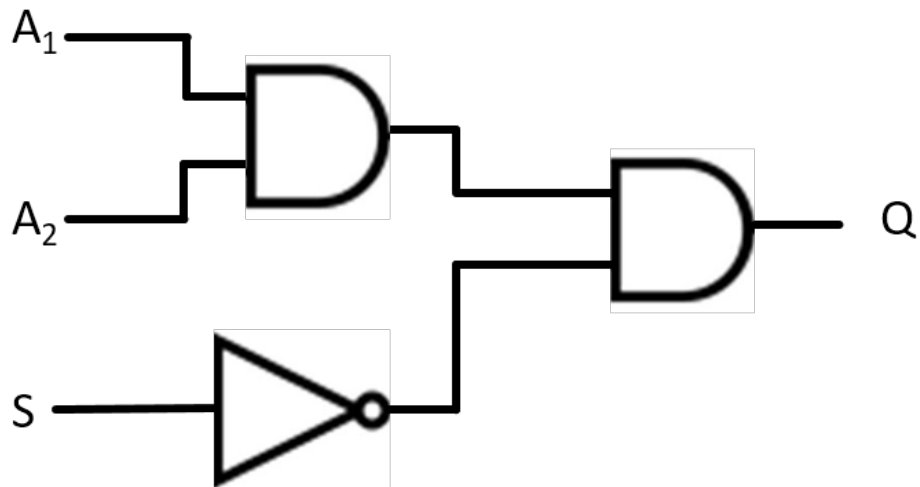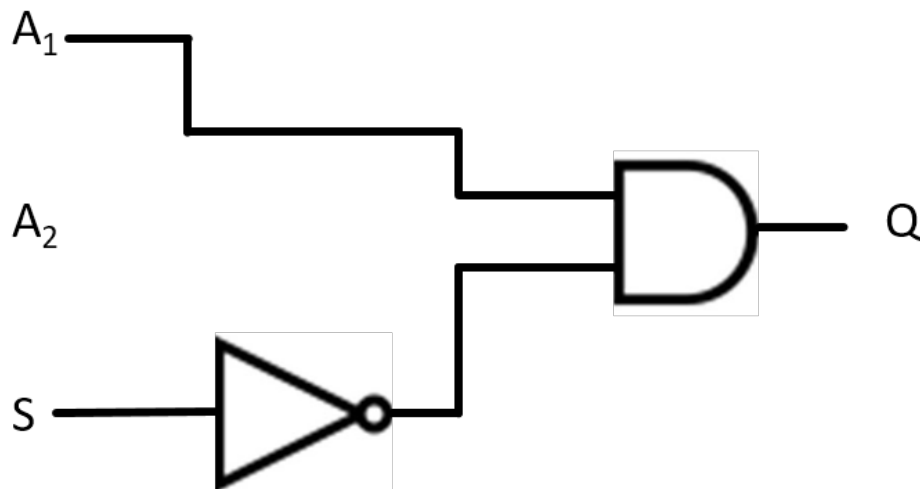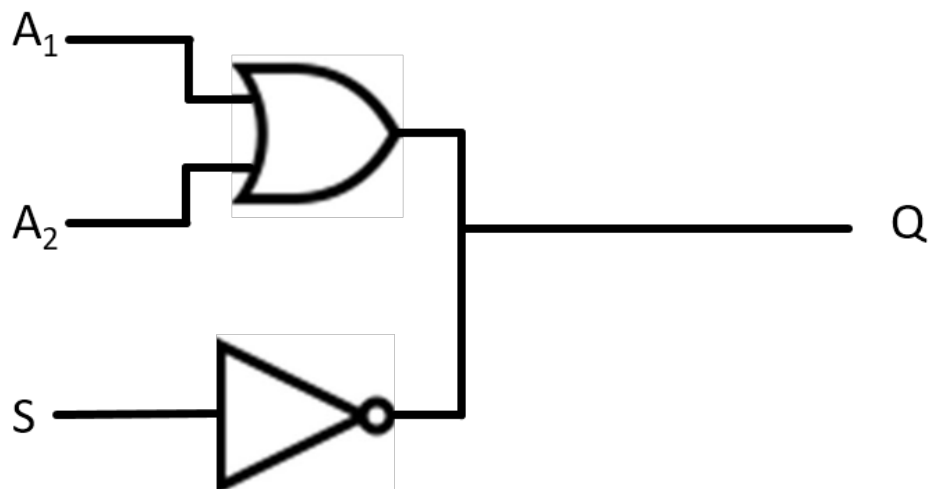**Example 2 (Marks B and C)****Example 3 (Marks B and C)****Example 4 (Marks A and B)**

Question	Part	Marking guidance	Total marks															
09	1	<p>Mark is for AO2 (apply)</p> <div><div>C<table><tr><th>A</th><th>B</th><th>Q</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table></div><p>R. If more than one lozenge shaded</p></div>	A	B	Q	0	0	0	0	1	1	1	0	1	1	1	1	1
A	B	Q																
0	0	0																
0	1	1																
1	0	1																
1	1	1																

Question	Part	Marking guidance	Total marks
09	2	<div>3 marks for AO2 (apply)</div> <div>1 mark for each correct logic gate name in the correct box</div> <div><div><div>A</div><div>B</div><div>C</div><div><div>AND;<div>X</div></div><div><div>XOR;<div>Y</div></div><div><div>NOT;<div>Z</div></div></div></div></div></div><div>A. if the name is not inside the box, but it is clear which box the name refers to</div><div>R. if logic gate symbols used instead of names</div></div> <div></div> <div></div>	3

Question	Part	Marking guidance	Total marks
09	3	<p><b>3 marks for AO2 (apply)</b></p> <p><b>Note to examiners:</b> any alternative notations <b>must</b> be referred to a senior examiner.</p> <p><math>\bar{A} + B.C ;;;</math></p> <p>If equation is not correct then award a <b>maximum of 2 marks</b> from the following:</p> <ul style="list-style-type: none"> <li>• Using the AND symbol . in between inputs <b>B</b> and <b>C</b>;</li> <li>• Using the OR symbol + in between input <b>A</b> and another gate;</li> <li>• Using the NOT symbol <math>\bar{\quad}</math> above input <b>A</b>;</li> </ul> <p><b>I.</b> Parentheses unless they change the order of precedence eg <math>(\bar{A} + B).C</math> is incorrect</p>	3