

Computer Science

10. Boolean Logic

Marking Scheme

Q1)

(a)

A	B	C	Working	X
0	0	0		1
0	0	1		0
0	1	0		0
0	1	1		0
1	0	0		0
1	0	1		1
1	1	0		1
1	1	1		1

1 mark


1 mark

1 mark

1 mark

[4]

(b) 1 mark per dotted section

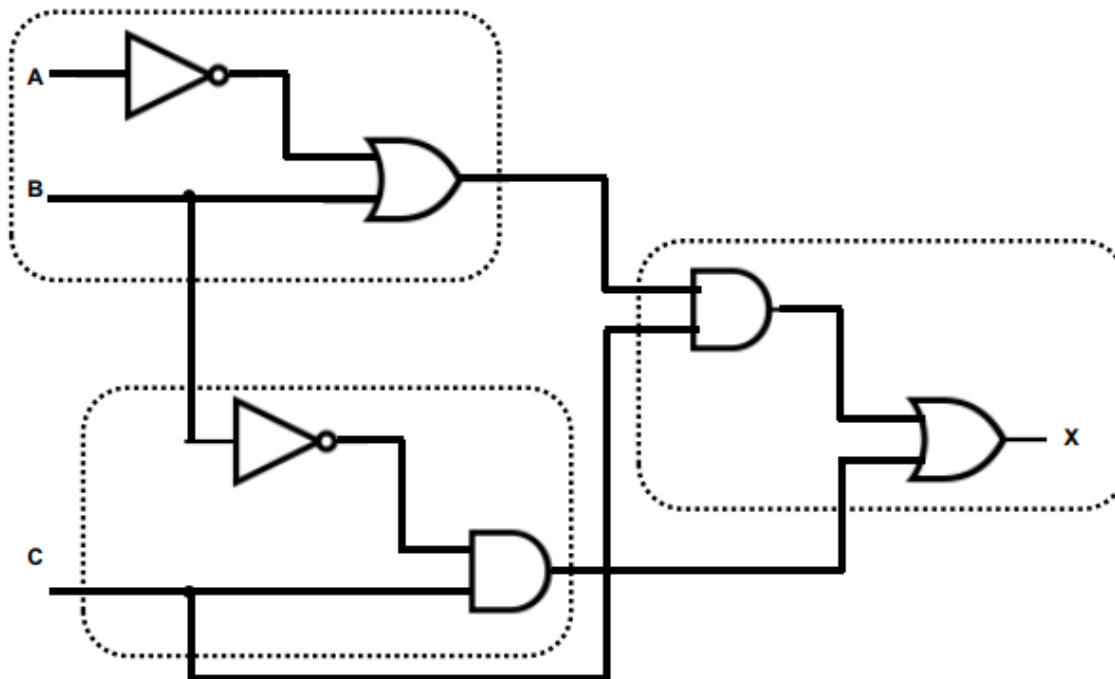

[3]

(c) X is 1 if:

(A is 1 OR B is 1)

(1 mark)

AND

(1 mark)

(B is 1 OR C is NOT 1)

(1 mark)

accept equivalent ways of writing this:

e.g. $(A \text{ OR } B = 1) \text{ AND } (B \text{ OR NOT } C = 1)$


e.g. $(A \text{ OR } B) \text{ AND } (B \text{ OR NOT } C)$

e.g. $(A + B) (B + \bar{C})$

[3]

Q2)

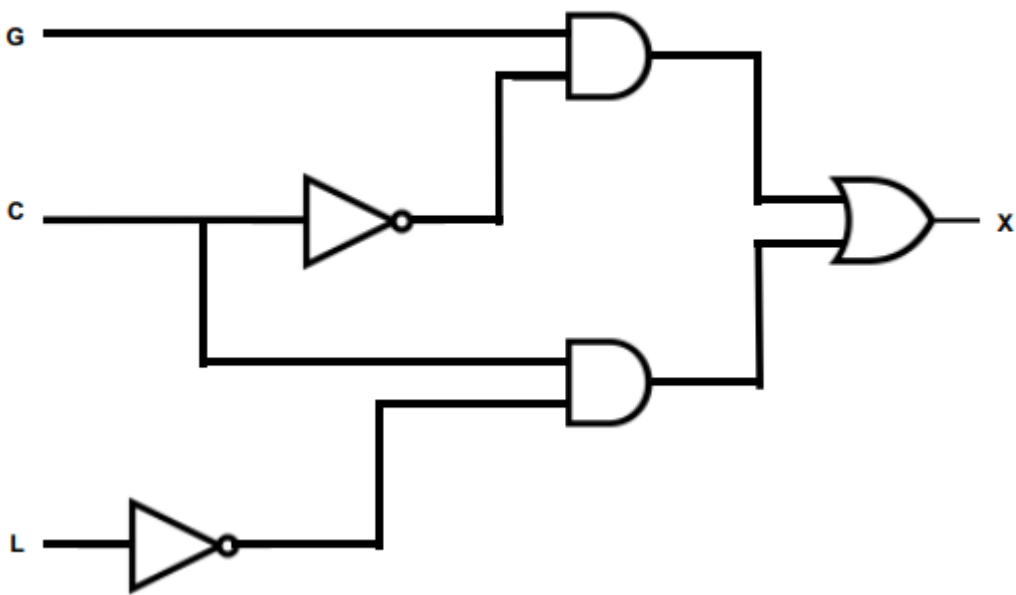(a) 1 mark per correct logic gate, correctly connected



[5]

(b)

G	C	L	Workspace	X
0	0	0		0
0	0	1		0
0	1	0		1
0	1	1		0
1	0	0		1
1	0	1		1
1	1	0		1
1	1	1		0

1 mark

1 mark

1 mark

1 mark

[4]


(c) 1 mark for correctly completed truth table

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

[1]

Q3)

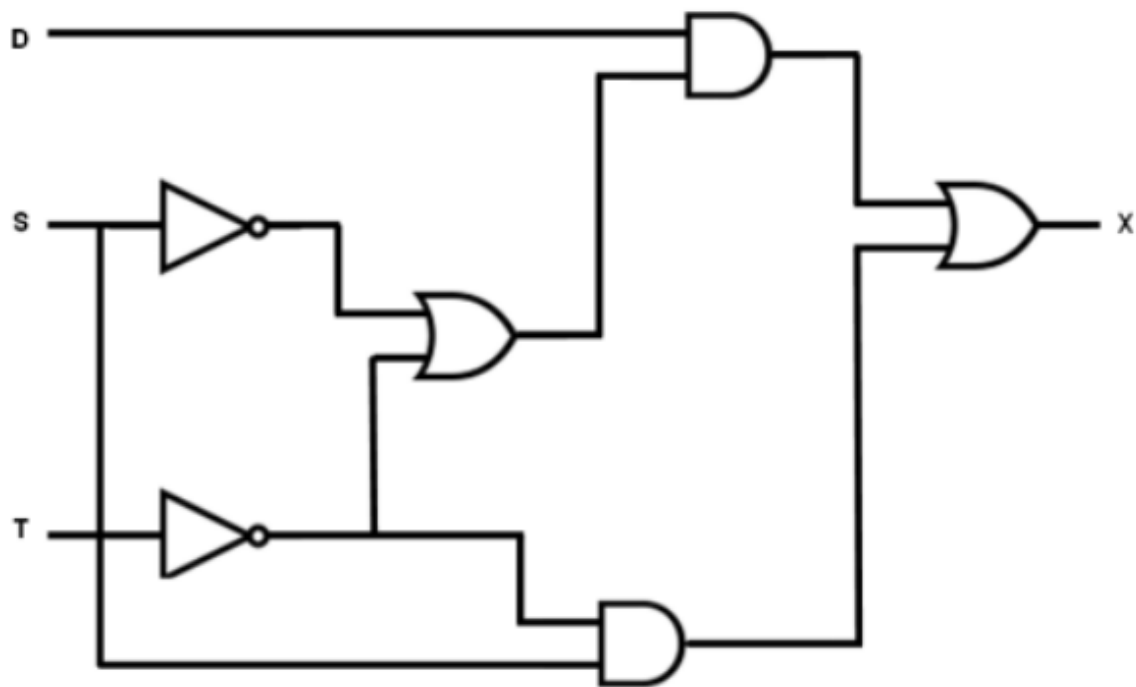(a) 1 mark for each correct gate, with correct source of input(s)



[6]

(b)

D	S	T	Working Space	X
0	0	0		0
0	0	1		0
0	1	0		1
0	1	1		0
1	0	0		1
1	0	1		1
1	1	0		1
1	1	1		0

4 marks for 8 correct X bits
3 marks for 6 correct X bits
2 marks for 4 correct X bits
1 mark for 2 correct X bits

[4]

Q4)

(a)

A	B	C	Working space	X
<i>0</i>	<i>0</i>	<i>0</i>		0
<i>0</i>	<i>0</i>	<i>1</i>		1
<i>0</i>	<i>1</i>	<i>0</i>		0
<i>0</i>	<i>1</i>	<i>1</i>		1
<i>1</i>	<i>0</i>	<i>0</i>		0
<i>1</i>	<i>0</i>	<i>1</i>		1
<i>1</i>	<i>1</i>	<i>0</i>		1
<i>1</i>	<i>1</i>	<i>1</i>		0

4 marks for 8 correct X bits


3 marks for 6 correct X bits

2 marks for 4 correct X bits

1 mark for 2 correct X bits


[4]

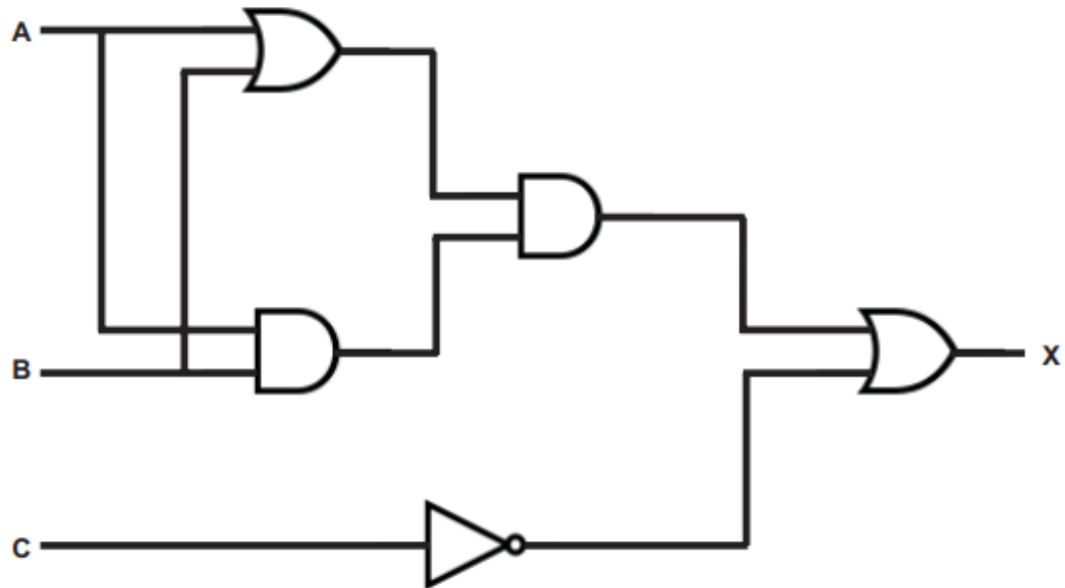(b) 1 mark for each correct gate with correct source of input



[5]


(c) Each dotted area is 1 mark

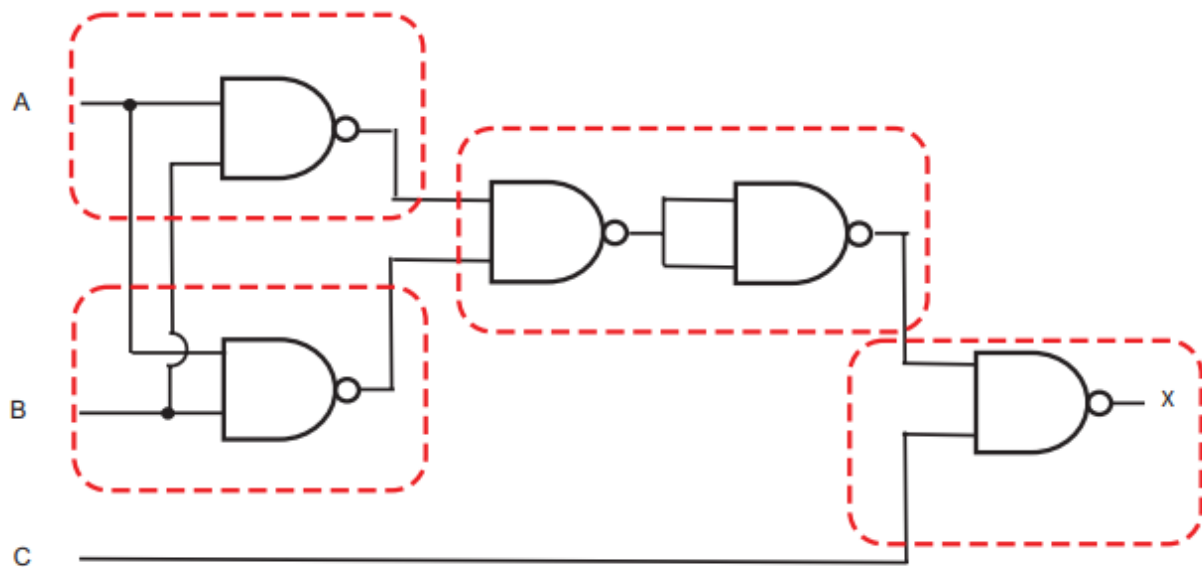

[4]

Q5)

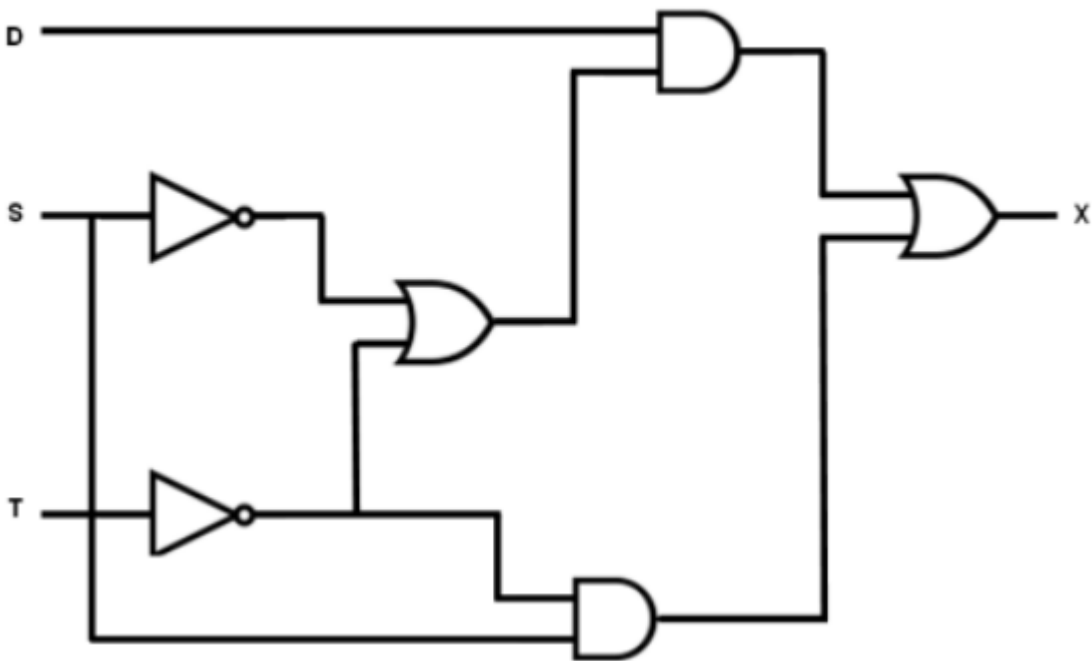(a) 1 mark for each correct gate, with correct source of input(s)



[6]

(b)


D	S	T	Working Space	X
0	0	0		0
0	0	1		0
0	1	0		1
0	1	1		0
1	0	0		1
1	0	1		1
1	1	0		1
1	1	1		0

4 marks for 8 correct X bits
3 marks for 6 correct X bits
2 marks for 4 correct X bits
1 mark for 2 correct X bits

[4]

Q6)

(a) 1 mark per correct section.

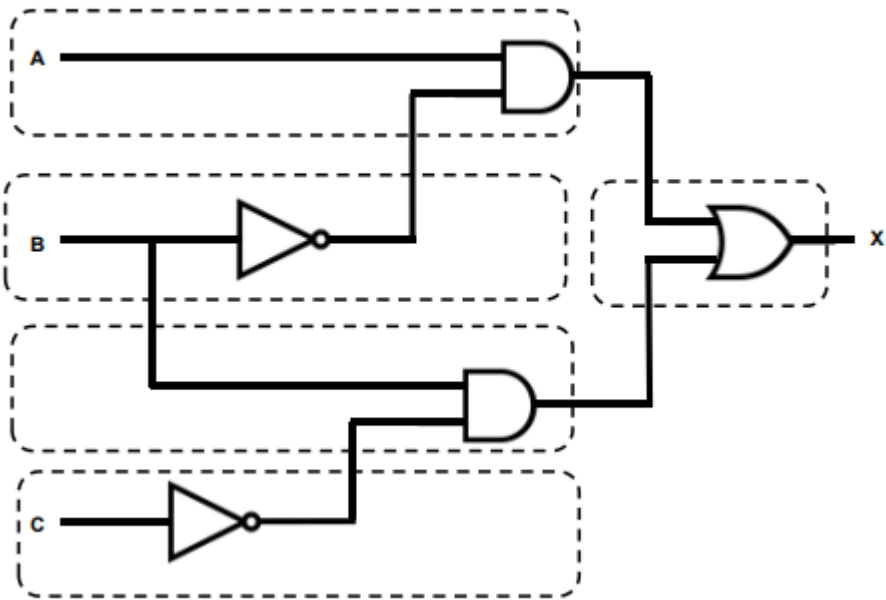

[5]

(b) 4 marks for 8 correct values
3 marks for 6 correct values
2 marks for 4 correct values
1 mark for 2 correct values

A	B	C	Working space	X
0	0	0		0
0	0	1		0
0	1	0		1
0	1	1		0
1	0	0		1
1	0	1		1
1	1	0		1
1	1	1		0

[4]

Q7)

- (a) (i) 2 marks for 4 correct outputs,
1 mark for 2 correct outputs

1 mark for correct gate

A	B	Working space	X
0	0		0
0	1		0
1	0		0
1	1		1

AND gate

[3]

- (ii) 2 marks for 4 correct outputs
1 mark for 2 correct outputs


1 mark for correct gate

A	B	Working space	X
0	0		0
0	1		1
1	0		1
1	1		1

OR gate

[3]

(b)(i) 1 mark per correct section.

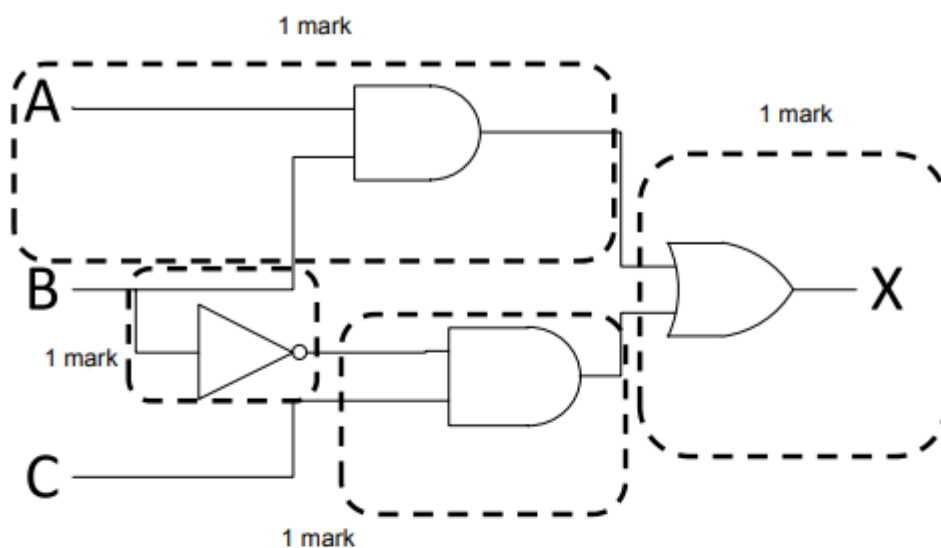

- (ii) 4 marks for 8 correct outputs
 3 marks for 6 correct outputs
 2 marks for 4 correct outputs
 1 mark for 2 correct outputs

[4]


A	B	C	Working space	X
0	0	0		0
0	0	1		1
0	1	0		0
0	1	1		0
1	0	0		0
1	0	1		1
1	1	0		1
1	1	1		1

[4]


Q8)


Question	Answer	Marks															
(a)	<p>1 mark for four correct outputs only</p> <table> <tr> <th>A</th><th>B</th><th>Output</th></tr> <tr> <td>0</td><td>0</td><td>1</td></tr> <tr> <td>0</td><td>1</td><td>0</td></tr> <tr> <td>1</td><td>0</td><td>0</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </table>	A	B	Output	0	0	1	0	1	0	1	0	0	1	1	0	1
A	B	Output															
0	0	1															
0	1	0															
1	0	0															
1	1	0															
(b)	<p>1 mark for each correct section of the statement</p> <p>∞ (A AND B)</p> <p>∞ AND</p> <p>∞ (C OR NOT B)</p>	3															

Q9)

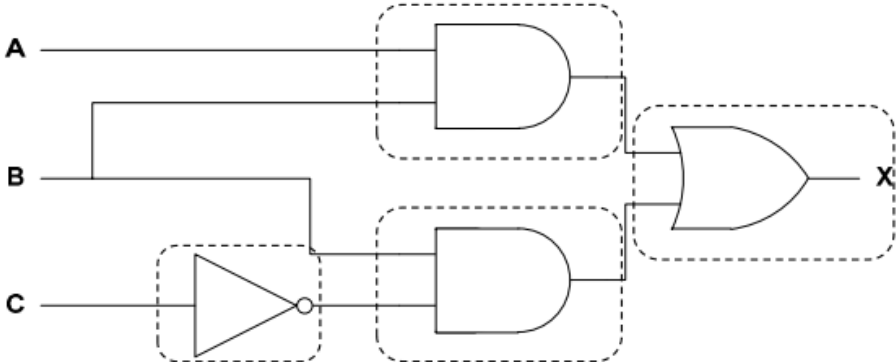
Question	Answer	Marks																																				
(a)	<p>1 mark for each correct gate, with the correct input(s)</p> 	4																																				
(b)	<table><thead><tr><th>A</th><th>B</th><th>C</th><th>X</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td></tr></tbody></table> <p>4 marks for 8 correct outputs 3 marks for 6 or 7 correct outputs 2 marks for 4 or 5 correct outputs 1 mark for 2 or 3 correct outputs</p>	A	B	C	X	0	0	0	0	0	0	1	0	0	1	0	1	0	1	1	0	1	0	0	0	1	0	1	0	1	1	0	1	1	1	1	1	4
A	B	C	X																																			
0	0	0	0																																			
0	0	1	0																																			
0	1	0	1																																			
0	1	1	0																																			
1	0	0	0																																			
1	0	1	0																																			
1	1	0	1																																			
1	1	1	1																																			

Q10)

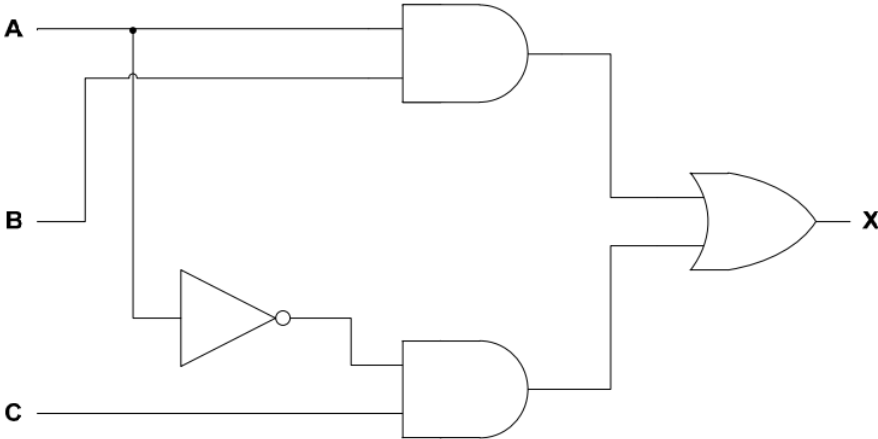
Question	Answer	Marks
(a)	<div>1 mark for each correct logic gate</div> <div></div>	4

Question	Answer	Marks
(b)	<div>1 mark for correct logic gate symbol:</div> <div></div> <div>Any four from:</div> <ul style="list-style-type: none">- similar to an OR gate- It has (at least) two inputs- Output will be high/1 if both inputs are different- Output will be high/1 if either input is high- Output will be low/0 if both inputs are high- Output will be low/0 if both inputs are low	5

Q11)

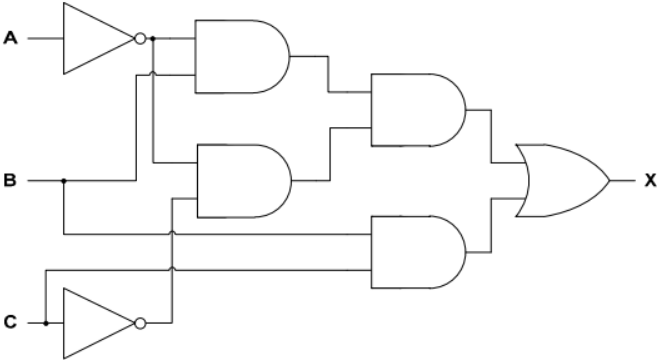
Question	Answer	Marks
	<div>1 mark for each correct logic gate with the correct input(s)</div> <div></div>	7

Q12)

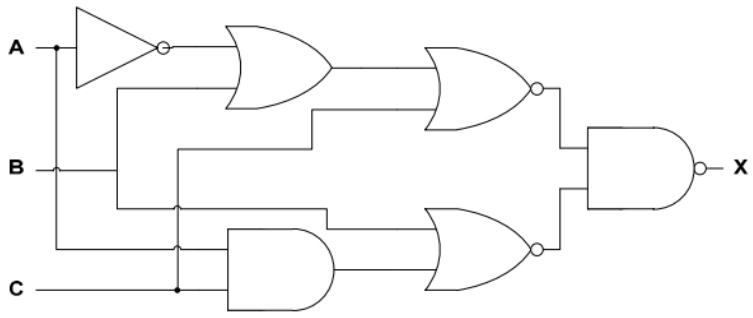Question	Answer	Marks
(a)	<div>1 mark for each correct logic gate (with the correct direction of input(s))</div> <div></div>	6

Question	Answer	Marks																																													
(b)	<div>4 marks for 8 correct outputs 3 marks for 6 or 7 correct outputs 2 marks for 4 or 5 correct outputs 1 mark for 2 or 3 correct outputs</div> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		1	0	0	1		1	0	1	0		1	0	1	1		1	1	0	0		0	1	0	1		1	1	1	0		1	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		1																																											
0	1	0		1																																											
0	1	1		1																																											
1	0	0		0																																											
1	0	1		1																																											
1	1	0		1																																											
1	1	1		1																																											

Q13)

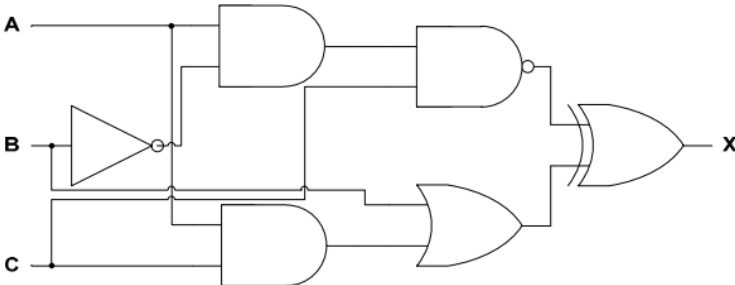Question	Answer	Marks																																													
(a)	<p>1 mark for each correct logic gate with correct direct of input(s):</p> 	6																																													
(b)	<p>4 marks for 8 correct outputs 3 marks for 6 or 7 correct outputs 2 marks for 4 or 5 correct outputs 1 mark for 2 or 3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table>	A	B	C	Working space	X	0	0	0		1	0	0	1		1	0	1	0		0	0	1	1		0	1	0	0		1	1	0	1		1	1	1	0		0	1	1	1		0	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		1																																											
0	1	0		0																																											
0	1	1		0																																											
1	0	0		1																																											
1	0	1		1																																											
1	1	0		0																																											
1	1	1		0																																											

Q14)

Question	Answer				Marks
(a)	A	B	C	X	4
	0	0	0	1	
	0	0	1	1	
	0	1	0	0	
	0	1	1	1	
	1	0	0	0	
	1	0	1	1	
	1	1	0	1	
	1	1	1	1	
	All 8 for 4 marks 6 or 7 for 3 marks 4 or 5 for 2 marks 2 or 3 for 1 mark				


Question	Answer	Marks
(b)	<p>1 mark per gate with correct inputs</p>	6

Question	Answer	Marks																																													
(a)	<p> \propto 4 marks for 8 correct outputs ∞ 3 marks for 6 or 7 correct outputs ∞ 2 marks for 4 or 5 correct outputs ∞ 1 mark for 2 or 3 correct outputs </p> <table border="1"> <thead> <tr> <th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr> <tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr> </tbody> </table>	A	B	C	Working space	X	0	0	0		1	0	0	1		1	0	1	0		1	0	1	1		1	1	0	0		0	1	0	1		1	1	1	0		1	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		1																																											
0	1	0		1																																											
0	1	1		1																																											
1	0	0		0																																											
1	0	1		1																																											
1	1	0		1																																											
1	1	1		1																																											
(b)	<p>Three from:</p> <ul style="list-style-type: none"> ∞ output of AND is 1 if both inputs are 1 ∞ output of AND is 0 if either or both inputs are 0 ∞ output of OR is 1 if either input is 1 ∞ output of OR is 0 if both inputs are 0 ∞ correct example of AND truth table ∞ correct example of OR truth table 	3																																													



Question	Answer	Marks
	<p>1 mark for each correct logic gate, with correct inputs.</p> <pre> graph LR W --- NOT1[NOT] T --- AND1[AND] T --- NOT2[NOT] NOT2 --- AND2[AND] H --- AND2 AND1 --- OR[OR] AND2 --- OR OR --- X </pre>	5


Q17)

Question	Answer	Marks																																				
(a)	<div>4 marks for 8 correct outputs 3 marks for 6 or 7 correct outputs 2 marks for 4 or 5 correct outputs 1 mark for 2 or 3 correct outputs</div> <table><tr><th>A</th><th>B</th><th>C</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	X	0	0	0	0	0	0	1	0	0	1	0	1	0	1	1	1	1	0	0	0	1	0	1	1	1	1	0	0	1	1	1	0	4
A	B	C	X																																			
0	0	0	0																																			
0	0	1	0																																			
0	1	0	1																																			
0	1	1	1																																			
1	0	0	0																																			
1	0	1	1																																			
1	1	0	0																																			
1	1	1	0																																			

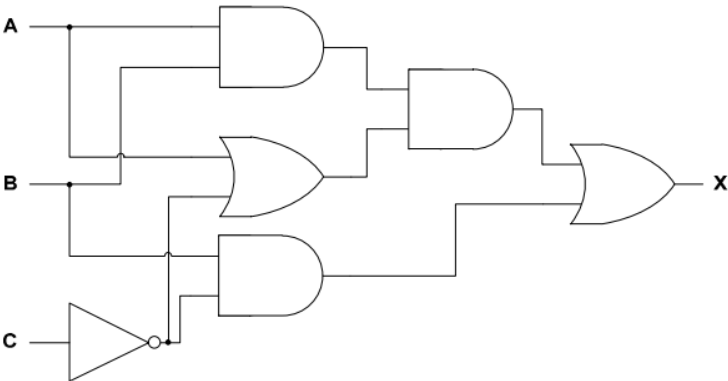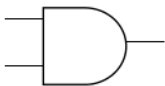
Question	Answer	Marks
(b)	<div>1 mark per correct gate with correct inputs.</div> 	6

Q18)

Question	Answer	Marks
(a)	1 mark for correct name, 1 mark for correct gate symbol – AND 	2
(b)	1 mark for correct name, 1 mark for correct gate symbol – NOR 	2

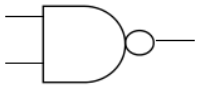
Question	Answer	Marks
(c)	1 mark for correct name, 1 mark for correct gate symbol – NAND 	2

Q19)

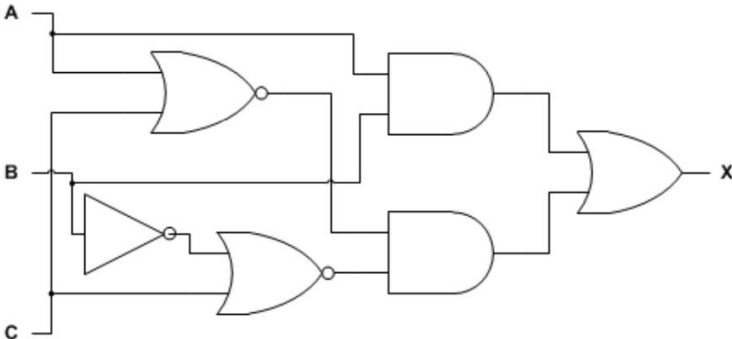Question	Answer	Marks
(a)	<div>1 mark per each correct logic gate, with correct input(s)</div> <div></div>	6

Question	Answer	Marks																																													
(b)	<div>4 marks for 8 correct outputs 3 marks for 6/7 correct outputs 2 marks for 4/5 correct outputs 1 mark for 2/3 correct outputs</div> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		0	0	0	1		0	0	1	0		1	0	1	1		0	1	0	0		0	1	0	1		0	1	1	0		1	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		0																																											
0	0	1		0																																											
0	1	0		1																																											
0	1	1		0																																											
1	0	0		0																																											
1	0	1		0																																											
1	1	0		1																																											
1	1	1		1																																											

Q20)

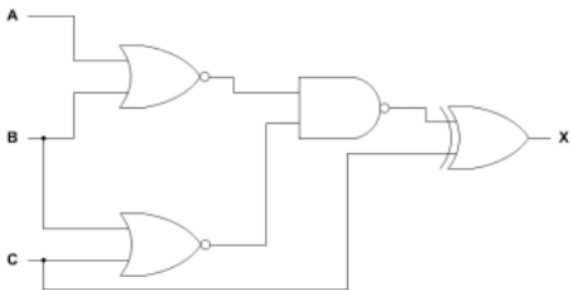Question	Answer	Marks
(a)	<p>1 mark for each correct logic gate, with correct inputs:</p> 	4

Question	Answer	Marks																																													
(b)	<p>4 marks for 8 correct outputs 3 marks for 6/7 correct outputs 2 marks for 4/5 correct outputs 1 mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table>	A	B	C	Working space	X	0	0	0		0	0	0	1		0	0	1	0		1	0	1	1		0	1	0	0		1	1	0	1		0	1	1	0		1	1	1	1		0	4
A	B	C	Working space	X																																											
0	0	0		0																																											
0	0	1		0																																											
0	1	0		1																																											
0	1	1		0																																											
1	0	0		1																																											
1	0	1		0																																											
1	1	0		1																																											
1	1	1		0																																											
(c)	<p>Two from:</p> <ul style="list-style-type: none">– To carry out a logical operation– To control the flow of electricity through a logic circuit– An input is given and the logic of the gate is applied to give an output // to alter the output from given inputs	2																																													

Q21)


Question	Answer	Marks															
(a)	<table border="1"> <thead> <tr> <th>Input A</th><th>Input B</th><th>Output</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>0</td></tr> <tr> <td>0</td><td>1</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	Input A	Input B	Output	0	0	0	0	1	1	1	0	1	1	1	1	1
Input A	Input B	Output															
0	0	0															
0	1	1															
1	0	1															
1	1	1															
(b)	∝ Exclusive OR / XOR / EOR	1															
(c)	<p>One mark for each correct logic gate with correct inputs</p>	5															
(d)	<p>Two from:</p> <ul style="list-style-type: none"> ∞ Can work continuously ∞ Avoids human error ∞ It could be a dangerous environment and will avoid human risk ∞ Detect errors instantly ∞ Maintain consistent and correct conditions 	2															

Q22)

Question	Answer	Marks
(a)	∞ $X = 1$ if (A is 1 XOR C is 1) OR (B is 1 NAND C is NOT 1) ∞ $X = (A \text{ XOR } C) \text{ OR } (B \text{ NAND NOTC})$ One mark for each bullet: ∞ (A XOR C) ∞ OR ∞ (B NAND NOTC)	3

Question	Answer	Marks																																													
(b)	<p>Four marks for 8 correct outputs Three marks for 6 or 7 correct outputs Two marks for 4 or 5 correct outputs One mark for 2 or 3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		1	0	0	1		1	0	1	0		0	0	1	1		1	1	0	0		1	1	0	1		1	1	1	0		1	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		1																																											
0	1	0		0																																											
0	1	1		1																																											
1	0	0		1																																											
1	0	1		1																																											
1	1	0		1																																											
1	1	1		1																																											

Q23)

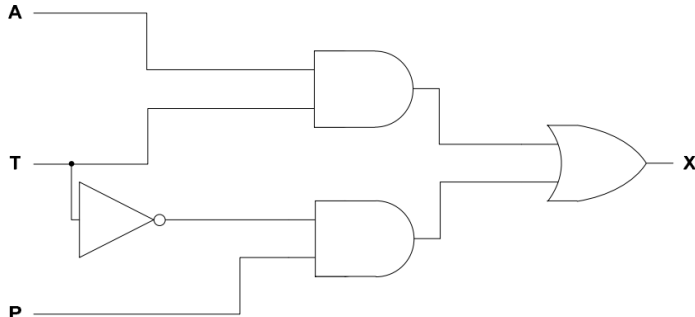Question	Answer	Marks
(a)	<p>One mark for each correct logic gate with correct input(s)</p> 	4



Question	Answer	Marks																																													
(b)	<p>Four mark for 8 correct outputs Three marks for 6 or 7 correct outputs Two mark for 4 or 5 correct outputs One mark for 2 or 3 correct outputs</p> <table><tr><th>A</th><th>T</th><th>P</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	T	P	Working space	X	0	0	0		0	0	0	1		1	0	1	0		0	0	1	1		0	1	0	0		0	1	0	1		1	1	1	0		1	1	1	1		1	4
A	T	P	Working space	X																																											
0	0	0		0																																											
0	0	1		1																																											
0	1	0		0																																											
0	1	1		0																																											
1	0	0		0																																											
1	0	1		1																																											
1	1	0		1																																											
1	1	1		1																																											
(c)	<p>Six from:</p> <ul style="list-style-type: none">∞ Sensor sends a signal/reading/data to the microprocessor∞ Signal/reading/data is analogue and is converted to digital using ADC∞ Reading/data is stored in the system∞ Microprocessor compares data/reading to the pre-set value of 7∞ If value is greater than 7 ...∞ ... a signal/data is sent by the microprocessor to display a warning message on a monitor∞ The process is continuous	6																																													

Q24)

Question	Answer	Marks
(a)	<div><p>1 mark for each correct gate.</p></div>	5

Question	Answer	Marks																																													
(b)	<table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table> <p>4 marks for 8 correct outputs 3 marks for 6 or 7 correct outputs 2 marks for 4 or 5 correct outputs 1 mark for 2 or 3 correct outputs</p>	A	B	C	Working space	X	0	0	0		1	0	0	1		0	0	1	0		1	0	1	1		0	1	0	0		1	1	0	1		0	1	1	0		1	1	1	1		0	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		0																																											
0	1	0		1																																											
0	1	1		0																																											
1	0	0		1																																											
1	0	1		0																																											
1	1	0		1																																											
1	1	1		0																																											

Q25)

Question	Answer	Marks
(a)(i)	<div>– NAND</div> 	2
(a)(ii)	<div>– NOR</div> 	2

Question	Answer	Marks																																													
(b)	<table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table> <p>4 marks for 8 correct outputs 3 marks for 6 or 7 correct outputs 2 marks for 4 or 5 correct outputs 1 mark for 2 or 3 correct outputs</p>	A	B	C	Working space	X	0	0	0		0	0	0	1		0	0	1	0		1	0	1	1		1	1	0	0		0	1	0	1		0	1	1	0		1	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		0																																											
0	0	1		0																																											
0	1	0		1																																											
0	1	1		1																																											
1	0	0		0																																											
1	0	1		0																																											
1	1	0		1																																											
1	1	1		1																																											

Q26)

Question	Answer	Marks
(a)	<div><p>One mark for each correct gate.</p></div>	4

Question	Answer					Marks																																													
(b)	<table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table>					A	B	C	Working space	X	0	0	0		1	0	0	1		0	0	1	0		1	0	1	1		1	1	0	0		1	1	0	1		1	1	1	0		1	1	1	1		0	4
	A	B	C	Working space	X																																														
	0	0	0		1																																														
	0	0	1		0																																														
	0	1	0		1																																														
	0	1	1		1																																														
	1	0	0		1																																														
	1	0	1		1																																														
	1	1	0		1																																														
	1	1	1		0																																														


Q27)

Question	Answer	Marks
(a)	<p>One mark for each correct gate with correct input</p>	4

Question	Answer	Marks																																													
(b)	<p>Four marks for 8 correct outputs Three marks for 6/7 correct outputs Two marks for 4/5 correct outputs One mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		1	0	0	1		0	0	1	0		0	0	1	1		0	1	0	0		1	1	0	1		0	1	1	0		1	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		0																																											
0	1	0		0																																											
0	1	1		0																																											
1	0	0		1																																											
1	0	1		0																																											
1	1	0		1																																											
1	1	1		1																																											

Question	Answer	Marks																														
(c)	<p>One mark for the correct gate and one mark for the correct truth table</p> <p>– AND</p> <table><tr><td>A</td><td>B</td><td>X</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> <p>– XOR</p> <table><tr><td>A</td><td>B</td><td>X</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0	4
A	B	X																														
0	0	0																														
0	1	0																														
1	0	0																														
1	1	1																														
A	B	X																														
0	0	0																														
0	1	1																														
1	0	1																														
1	1	0																														

Q28)

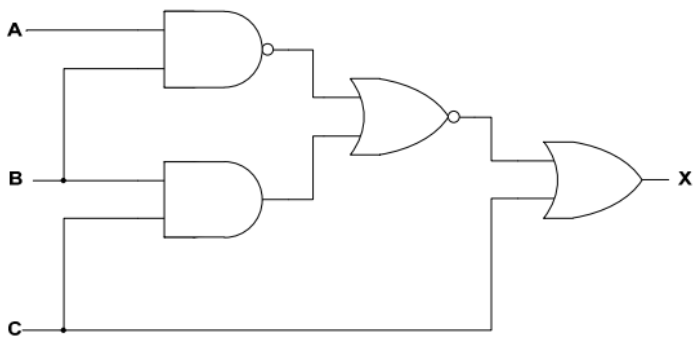Question	Answer	Marks
(a)	<p>One mark for each correct logic gate with correct input:</p> 	4


Question	Answer	Marks																																													
(b)	<p>Four marks for 8 correct outputs Three marks for 6/7 correct outputs Two marks for 4/5 correct outputs One mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		0	0	0	1		1	0	1	0		0	0	1	1		1	1	0	0		0	1	0	1		1	1	1	0		1	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		0																																											
0	0	1		1																																											
0	1	0		0																																											
0	1	1		1																																											
1	0	0		0																																											
1	0	1		1																																											
1	1	0		1																																											
1	1	1		1																																											

Q29)


Question	Answer	Marks
(a)	<p>One mark for each correct logic gate with the correct input:</p> <pre>graph LR; A((A)) --> NOT1[NOT]; B((B)) --> AND1[AND]; B --> OR1[OR]; C((C)) --> OR1; NOT1 --> AND1; AND1 --> OR2[OR]; OR1 --> OR2; OR2 --> X((X))</pre>	4

Question	Answer	Marks																																													
(b)	<p>Four marks for 8 correct outputs Three marks for 6/7 correct outputs Two marks for 4/5 correct outputs One mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		0	0	0	1		1	0	1	0		1	0	1	1		0	1	0	0		1	1	0	1		1	1	1	0		1	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		0																																											
0	0	1		1																																											
0	1	0		1																																											
0	1	1		0																																											
1	0	0		1																																											
1	0	1		1																																											
1	1	0		1																																											
1	1	1		1																																											

Q30)

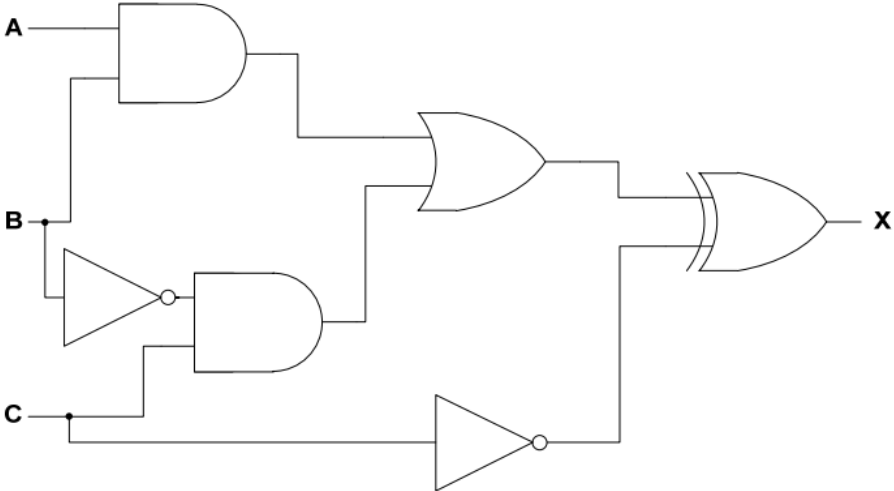Question	Answer	Marks
(a)	<div>One mark per each correct logic gate, with correct input:</div> <div></div>	6
(b)	<div><ul style="list-style-type: none">– Row 1– Row 3– Row 4– Row 5</div>	4

Q31)

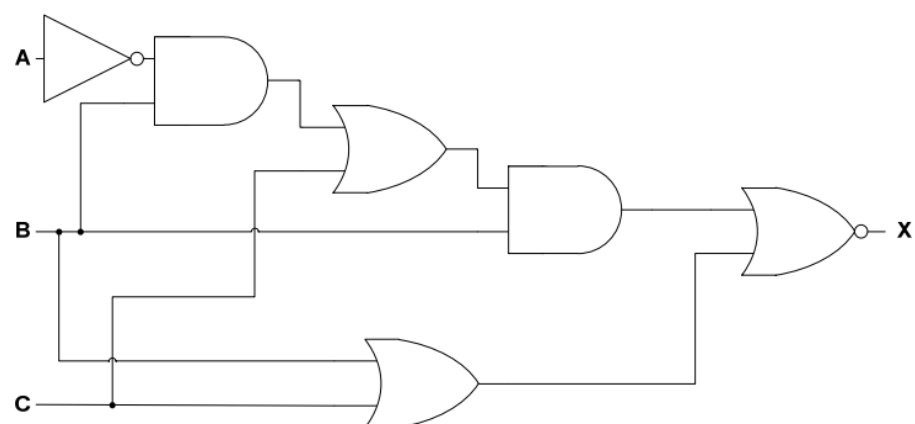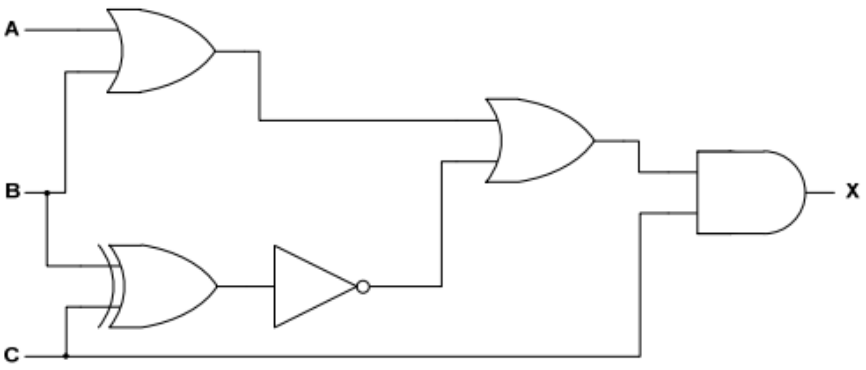

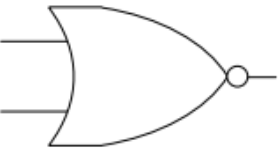
(a)	One mark for each correct logic gate with correct input.	6
		

Question	Answer	Marks
(b)	One mark per each correct row. – Row 2 – Row 3 – Row 7 – Row 8	4

Q32)

Question	Answer	Marks
(a)	– AND – NOR – XOR	3
(b)	– Row 1 – Row 4 – Row 7 – Row 8	4

Q33)

Question	Answer	Marks
(a)	<p>One mark per each correct logic gate with the correct input(s).</p> 	5
(b)	<p>One mark per logic gate name and one mark per correct drawing.</p> <p>– NAND</p>  <p>– NOR</p> 	2


Question	Answer					Marks
(c)	A	B	C	Working space	X	4
	0	0	0		0	
	0	0	1		0	
	0	1	0		0	
	0	1	1		1	
	1	0	0		0	
	1	0	1		1	
	1	1	0		0	
	1	1	1		1	
	4 marks per 8 correct outputs 3 marks per 6/7 correct outputs 2 marks per 4/5 correct outputs 1 mark per 2/3 correct outputs					

Q34)


Question	Answer	Marks
(a)	<p>One mark per each correct logic gate with correct input(s)</p> <pre>graph LR; A --> AND1[AND]; B --> AND1; AND1 --> OR1[OR]; C --> OR1; OR1 --> AND2[AND]; B --> AND2; AND2 --> X((X))</pre>	5

Question	Answer	Marks																																													
(b)	<div>4 marks for 8 correct outputs 3 marks for 6/7 correct outputs 2 marks for 4/5 correct outputs 1 mark for 2/3 correct outputs</div> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table>	A	B	C	Working space	X	0	0	0		1	0	0	1		1	0	1	0		1	0	1	1		1	1	0	0		1	1	0	1		1	1	1	0		1	1	1	1		0	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		1																																											
0	1	0		1																																											
0	1	1		1																																											
1	0	0		1																																											
1	0	1		1																																											
1	1	0		1																																											
1	1	1		0																																											
(c)	<div>– NOR – XOR / EOR</div>	2																																													

Q35)

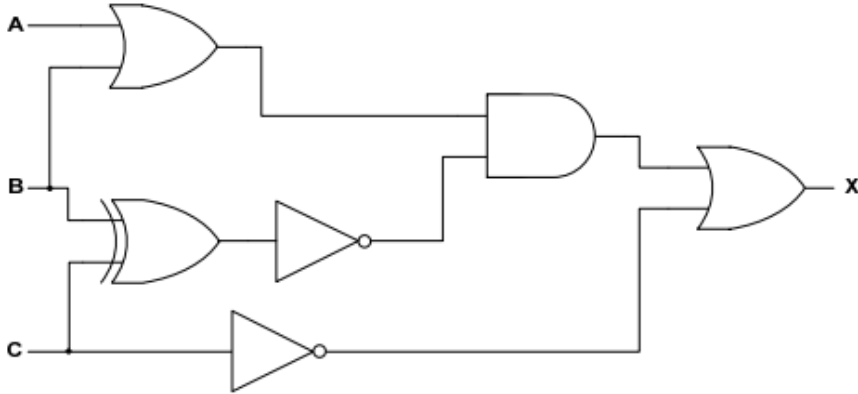
Question	Answer	Marks																																													
(a)	<p>One mark per each correct logic gate with correct inputs</p> 	6																																													
(b)	<p>4 marks for 8 correct outputs 3 marks for 6/7 correct outputs 2 marks for 4/5 correct outputs 1 mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		1	0	0	1		0	0	1	0		1	0	1	1		1	1	0	0		1	1	0	1		0	1	1	0		1	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		0																																											
0	1	0		1																																											
0	1	1		1																																											
1	0	0		1																																											
1	0	1		0																																											
1	1	0		1																																											
1	1	1		1																																											

Q36)

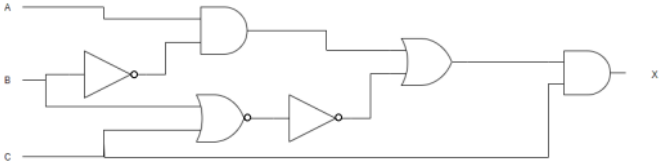Question	Answer	Marks
(a)	<p>One mark for each correct logic gate with correct input(s)</p> 	6

Question	Answer	Marks																																													
(b)	<p>Four marks for 8 correct outputs Three marks for 6/7 correct outputs Two marks for 4/5 correct outputs One mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		0	0	0	1		1	0	1	0		0	0	1	1		1	1	0	0		0	1	0	1		1	1	1	0		0	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		0																																											
0	0	1		1																																											
0	1	0		0																																											
0	1	1		1																																											
1	0	0		0																																											
1	0	1		1																																											
1	1	0		0																																											
1	1	1		1																																											

Q37)

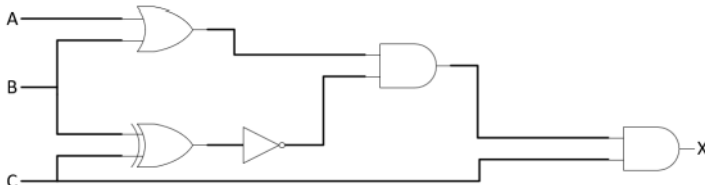
Question	Answer	Marks																																													
(a)	<p>One mark for each correct logic gate with correct input(s)</p> 	5																																													
(b)	<p>Four marks for 8 correct outputs Three marks for 6/7 correct outputs Two marks for 4/5 correct outputs One mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		0	0	0	1		0	0	1	0		0	0	1	1		1	1	0	0		0	1	0	1		0	1	1	0		0	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		0																																											
0	0	1		0																																											
0	1	0		0																																											
0	1	1		1																																											
1	0	0		0																																											
1	0	1		0																																											
1	1	0		0																																											
1	1	1		1																																											

Q38)

Question	Answer				Marks
(a)	One mark for each correct row				4
	Statement	AND (✓)	OR (✓)	XOR (✓)	
	if both inputs are 0, the output is 0	✓	✓	✓	
	if both inputs are different, the output is 1		✓	✓	
	if both inputs are 1, the output is 1	✓	✓		
	if both inputs are the same, the output is always 0			✓	

Question	Answer	Marks																														
(b)	<p>One mark for the correct name and one mark for the correct truth table</p> <ul style="list-style-type: none"> NOR <table> <tr> <th>A</th><th>B</th><th>Output</th></tr> <tr> <td>0</td><td>0</td><td>1</td></tr> <tr> <td>0</td><td>1</td><td>0</td></tr> <tr> <td>1</td><td>0</td><td>0</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </table> NAND <table> <tr> <th>A</th><th>B</th><th>Output</th></tr> <tr> <td>0</td><td>0</td><td>1</td></tr> <tr> <td>0</td><td>1</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </table> 	A	B	Output	0	0	1	0	1	0	1	0	0	1	1	0	A	B	Output	0	0	1	0	1	1	1	0	1	1	1	0	4
A	B	Output																														
0	0	1																														
0	1	0																														
1	0	0																														
1	1	0																														
A	B	Output																														
0	0	1																														
0	1	1																														
1	0	1																														
1	1	0																														

Q39)

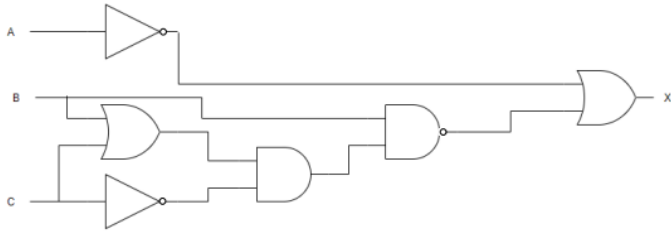
Question	Answer	Marks
(a)	<p>One mark for each correct logic gate with correct input(s)</p> 	6
(b)	<p>Any one from:</p> <ul style="list-style-type: none">• NOR• XOR // EOR	1

Question	Answer	Marks																																													
(c)	<p>Four marks for 8 correct outputs Three marks for 6/7 correct outputs Two marks for 4/5 correct outputs One mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		1	0	0	1		1	0	1	0		1	0	1	1		1	1	0	0		1	1	0	1		1	1	1	0		0	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		1																																											
0	1	0		1																																											
0	1	1		1																																											
1	0	0		1																																											
1	0	1		1																																											
1	1	0		0																																											
1	1	1		1																																											

Q40)


Question	Answer	Marks																				
(a)	<p>One mark for each correct row</p> <table><tr><th>Statement</th><th>NAND (✓)</th><th>OR (✓)</th><th>XOR (✓)</th></tr><tr><td>if both inputs are 1, the output is 1</td><td></td><td>✓</td><td></td></tr><tr><td>if both inputs are different from each other, the output is 1</td><td>✓</td><td>✓</td><td>✓</td></tr><tr><td>if both inputs are 0, the output is 0</td><td></td><td>✓</td><td>✓</td></tr><tr><td>if both inputs are the same as each other, the output is always 0</td><td></td><td></td><td>✓</td></tr></table>	Statement	NAND (✓)	OR (✓)	XOR (✓)	if both inputs are 1, the output is 1		✓		if both inputs are different from each other, the output is 1	✓	✓	✓	if both inputs are 0, the output is 0		✓	✓	if both inputs are the same as each other, the output is always 0			✓	4
Statement	NAND (✓)	OR (✓)	XOR (✓)																			
if both inputs are 1, the output is 1		✓																				
if both inputs are different from each other, the output is 1	✓	✓	✓																			
if both inputs are 0, the output is 0		✓	✓																			
if both inputs are the same as each other, the output is always 0			✓																			
(b)	<p>One mark for a correct logic gate, one mark for a corresponding truth table</p> <ul style="list-style-type: none">AND <table><tr><th>A</th><th>B</th><th>Output</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	Output	0	0	0	0	1	0	1	0	0	1	1	1	2					
A	B	Output																				
0	0	0																				
0	1	0																				
1	0	0																				
1	1	1																				

Q41)

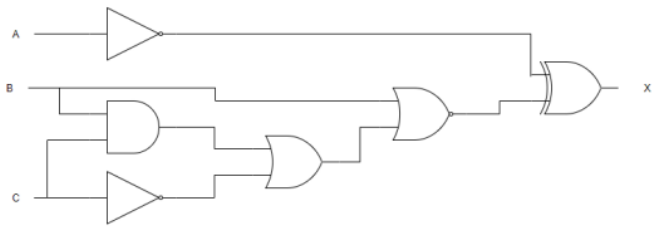Question	Answer	Marks
(a)	<p>One mark for each correct logic gate with the correct inputs</p> 	6



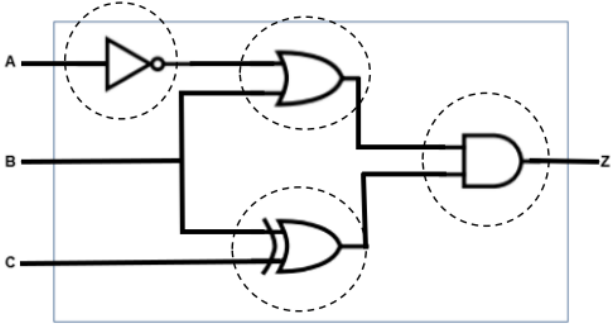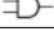

 
Question	Answer	Marks																																													
(b)	<p>Four marks for 8 correct outputs Three marks for 6/7 correct outputs Two marks for 4/5 correct outputs One mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table>	A	B	C	Working space	X	0	0	0		1	0	0	1		0	0	1	0		1	0	1	1		1	1	0	0		0	1	0	1		1	1	1	0		0	1	1	1		0	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		0																																											
0	1	0		1																																											
0	1	1		1																																											
1	0	0		0																																											
1	0	1		1																																											
1	1	0		0																																											
1	1	1		0																																											

Q42)

Question	Answer	Marks
(a)	<p>One mark for each correct gate, with the correct input(s) as shown.</p> 	4

Question	Answer	Marks																																				
(b)	<p>Four marks for eight correct outputs. Three marks for six or seven correct outputs. Two marks for four or five correct outputs. One mark for two or three correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	Z	0	0	0	0	0	0	1	1	0	1	0	1	0	1	1	0	1	0	0	0	1	0	1	0	1	1	0	1	1	1	1	0	4
A	B	C	Z																																			
0	0	0	0																																			
0	0	1	1																																			
0	1	0	1																																			
0	1	1	0																																			
1	0	0	0																																			
1	0	1	0																																			
1	1	0	1																																			
1	1	1	0																																			


Q43)

Question	Answer	Marks
	<p>One mark for each correct line</p> <div><div>Logic gate</div><div>Standard symbol</div><div><div>AND</div><div>OR</div><div>NAND</div><div>NOT</div></div><div><div></div><div></div><div></div><div></div><div></div></div></div>	4

Q44)

Question	Answer	Marks																																				
	<p>4 marks for 8 correct outputs 3 marks for 6/7 correct outputs 2 marks for 4/5 correct outputs 1 mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	X	0	0	0	0	0	0	1	0	0	1	0	0	0	1	1	0	1	0	0	0	1	0	1	1	1	1	0	0	1	1	1	0	4
A	B	C	X																																			
0	0	0	0																																			
0	0	1	0																																			
0	1	0	0																																			
0	1	1	0																																			
1	0	0	0																																			
1	0	1	1																																			
1	1	0	0																																			
1	1	1	0																																			

Q45)

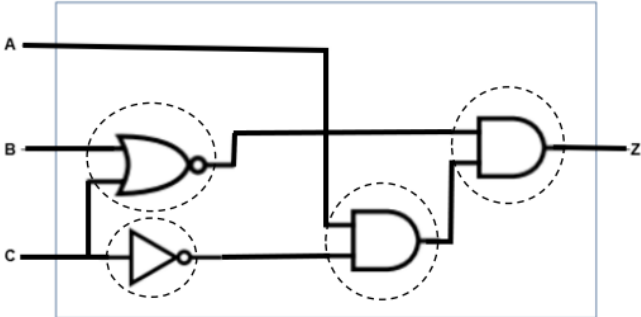Question	Answer	Marks
(a)	<p>One mark for each correct gate, with the correct input(s) as shown.</p> 	4


Question	Answer	Marks																																				
(b)	<p>Four marks for eight correct outputs. Three marks for six or seven correct outputs. Two marks for four or five correct outputs. One mark for two or three correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	Z	0	0	0	0	0	0	1	0	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	0	1	1	0	0	1	1	1	0	4
A	B	C	Z																																			
0	0	0	0																																			
0	0	1	0																																			
0	1	0	0																																			
0	1	1	0																																			
1	0	0	1																																			
1	0	1	0																																			
1	1	0	0																																			
1	1	1	0																																			

Q46)

Question	Answer	Marks
(a)	One mark for each point <ul style="list-style-type: none">NOT AAND BOR NOT Cexpression correct (NOT A AND B) OR NOT C	4


Question	Answer	Marks																																				
(b)	<table><tr><th>A</th><th>B</th><th>C</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table> <p>4 marks for 8 correct outputs 3 marks for 6/7 correct outputs 2 marks for 4/5 correct outputs 1 mark for 2/3 correct outputs</p>	A	B	C	X	0	0	0	1	0	0	1	0	0	1	0	1	0	1	1	1	1	0	0	1	1	0	1	0	1	1	0	1	1	1	1	0	4
A	B	C	X																																			
0	0	0	1																																			
0	0	1	0																																			
0	1	0	1																																			
0	1	1	1																																			
1	0	0	1																																			
1	0	1	0																																			
1	1	0	1																																			
1	1	1	0																																			

Q47)

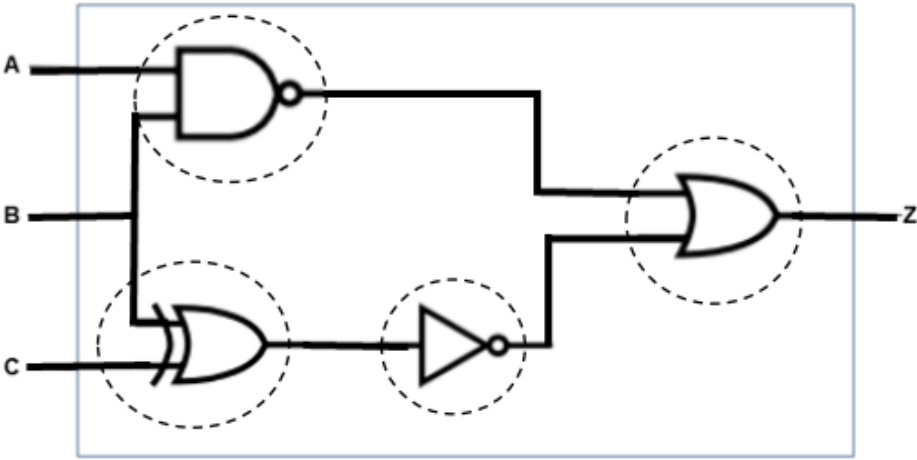
Question	Answer	Marks																																				
(a)	<p>One mark for each correct gate, with the correct input(s) as shown.</p> 	4																																				
(b)	<p>Four marks for eight correct outputs. Three marks for six or seven correct outputs. Two marks for four or five correct outputs. One mark for two or three correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td></tr></table>	A	B	C	Z	0	0	0	1	0	0	1	1	0	1	0	1	0	1	1	1	1	0	0	1	1	0	1	1	1	1	0	0	1	1	1	1	4
A	B	C	Z																																			
0	0	0	1																																			
0	0	1	1																																			
0	1	0	1																																			
0	1	1	1																																			
1	0	0	1																																			
1	0	1	1																																			
1	1	0	0																																			
1	1	1	1																																			

Q48)

Question	Answer	Marks															
(a)	<p>One mark for correct gate and one mark for correct truth table</p> <p>AND</p> <table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1	2
A	B	X															
0	0	0															
0	1	0															
1	0	0															
1	1	1															
(b)	<p>One mark for correct gate and one mark for correct truth table</p> <p>XOR // EOR</p> <table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0	2
A	B	X															
0	0	0															
0	1	1															
1	0	1															
1	1	0															

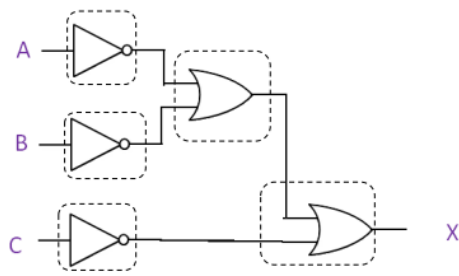



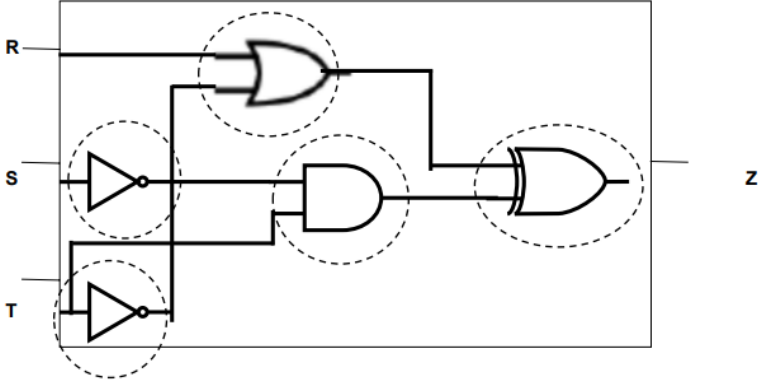







Question	Answer	Marks															
(c)	<p>One mark for correct gate and one mark for correct truth table</p> <p>NOR</p> <table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0	2
A	B	X															
0	0	1															
0	1	0															
1	0	0															
1	1	0															
(d)	<p>One mark for each correct gate, with the correct input(s) as shown.</p> 	5															

Q49)

Question	Answer	Marks
(a)	<p>One mark for each correct gate, with the correct input(s) as shown.</p> 	5

Question	Answer	Marks																																				
(b)	<p>Four marks for eight correct outputs. Three marks for six or seven correct outputs. Two marks for four or five correct outputs. One mark for two or three correct outputs</p> <table><tr><th>R</th><th>S</th><th>T</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td></tr></table>	R	S	T	Z	0	0	0	1	0	0	1	1	0	1	0	1	0	1	1	0	1	0	0	1	1	0	1	0	1	1	0	1	1	1	1	1	4
R	S	T	Z																																			
0	0	0	1																																			
0	0	1	1																																			
0	1	0	1																																			
0	1	1	0																																			
1	0	0	1																																			
1	0	1	0																																			
1	1	0	1																																			
1	1	1	1																																			

Q50)
















Question	Answer	Marks										
	<p>One mark for each correct line</p> <table><thead><tr><th>Logic function</th><th>Standard symbol</th></tr></thead><tbody><tr><td>AND</td><td></td></tr><tr><td>XOR</td><td></td></tr><tr><td>NAND</td><td></td></tr><tr><td>OR</td><td></td></tr></tbody></table>	Logic function	Standard symbol	AND		XOR		NAND		OR		4
Logic function	Standard symbol											
AND												
XOR												
NAND												
OR												

Q51)

Question	Answer	Marks
(a)	<p>X = (A AND B) // A AND B 1 mark AND NOT C 1 mark 1 mark</p> <p>X = (A AND B) AND NOT C</p>	3

Question	Answer	Marks																																				
(b)	<p>Four marks for 8 correct outputs Three marks for 6/7 correct outputs Two marks for 4/5 correct outputs One mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	X	0	0	0	0	0	0	1	0	0	1	0	0	0	1	1	0	1	0	0	0	1	0	1	0	1	1	0	1	1	1	1	0	4
A	B	C	X																																			
0	0	0	0																																			
0	0	1	0																																			
0	1	0	0																																			
0	1	1	0																																			
1	0	0	0																																			
1	0	1	0																																			
1	1	0	1																																			
1	1	1	0																																			

Q52)

Question	Answer	Marks												
(a)	<p>One mark for each correct line</p> <table><thead><tr><th>Logic gate symbol</th><th>Logic function</th></tr></thead><tbody><tr><td></td><td><input type="checkbox"/> AND</td></tr><tr><td></td><td><input type="checkbox"/> XOR</td></tr><tr><td></td><td><input type="checkbox"/> NOT</td></tr><tr><td></td><td><input type="checkbox"/> NAND</td></tr><tr><td></td><td><input type="checkbox"/> OR</td></tr></tbody></table>	Logic gate symbol	Logic function		<input type="checkbox"/> AND		<input type="checkbox"/> XOR		<input type="checkbox"/> NOT		<input type="checkbox"/> NAND		<input type="checkbox"/> OR	4
Logic gate symbol	Logic function													
	<input type="checkbox"/> AND													
	<input type="checkbox"/> XOR													
	<input type="checkbox"/> NOT													
	<input type="checkbox"/> NAND													
	<input type="checkbox"/> OR													


Question	Answer	Marks																																				
(b)	<table><tr><th>A</th><th>B</th><th>C</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table> <p>Four marks for eight correct outputs. Three marks for six or seven correct outputs. Two marks for four or five correct outputs. One mark for two or three correct outputs</p>	A	B	C	Z	0	0	0	0	0	0	1	1	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	0	1	1	0	0	1	1	1	0	4
A	B	C	Z																																			
0	0	0	0																																			
0	0	1	1																																			
0	1	0	0																																			
0	1	1	0																																			
1	0	0	1																																			
1	0	1	0																																			
1	1	0	0																																			
1	1	1	0																																			

Q53)

Question	Answer	Marks
(a)	<p>One mark for each point</p> <ul style="list-style-type: none"> NOT X Y XOR Z expression correct: NOT X OR (Y XOR Z) // (Y XOR Z) OR NOT X 	3

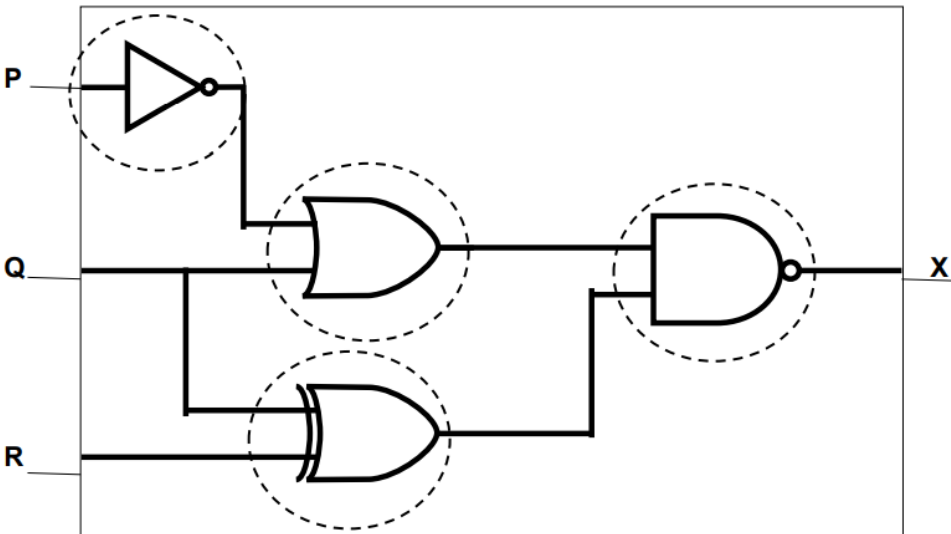
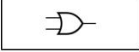

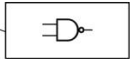

Question	Answer	Marks																																				
(b)	<p>4 marks for 8 correct outputs 3 marks for 6/7 correct outputs 2 marks for 4/5 correct outputs 1 mark for 2/3 correct outputs</p> <table><tr><th>X</th><th>Y</th><th>Z</th><th>W</th></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	X	Y	Z	W	0	0	0	1	0	0	1	1	0	1	0	1	0	1	1	1	1	0	0	0	1	0	1	1	1	1	0	1	1	1	1	0	4
X	Y	Z	W																																			
0	0	0	1																																			
0	0	1	1																																			
0	1	0	1																																			
0	1	1	1																																			
1	0	0	0																																			
1	0	1	1																																			
1	1	0	1																																			
1	1	1	0																																			

Q54)

Question	Answer	Marks
(a)	<p>One mark for each correct gate, with the correct input(s) as shown.</p> 	4

Question	Answer	Marks																																				
(b)	<p>Four marks for eight correct outputs Three marks for six or seven correct outputs Two marks for four or five correct outputs One mark for two or three correct outputs</p> <table><tr><th>P</th><th>Q</th><th>R</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td></tr></table>	P	Q	R	X	0	0	0	1	0	0	1	0	0	1	0	0	0	1	1	1	1	0	0	1	1	0	1	1	1	1	0	0	1	1	1	1	4
P	Q	R	X																																			
0	0	0	1																																			
0	0	1	0																																			
0	1	0	0																																			
0	1	1	1																																			
1	0	0	1																																			
1	0	1	1																																			
1	1	0	0																																			
1	1	1	1																																			

Q55)

Question	Answer	Marks
	<p>One mark for each correct line</p> <div><div>Logic gate</div><div><div>AND</div><div>NAND</div><div>NOR</div><div>XOR</div></div></div> <div><div>Logic gate symbol</div><div><div></div><div></div><div></div><div></div><div></div></div></div>	4