

# AQA A-Level Physics

## 7.4 Capacitance

### Flashcards

This work by [PMT Education](https://www.pmt.education) is licensed under [CC BY-NC-ND 4.0](https://creativecommons.org/licenses/by-nc-nd/4.0/)



# How is capacitance calculated?



# How is capacitance calculated?

$$C = Q \mid V$$

C = Capacitance (F)

Q = Charge in the plates (C )

V = potential difference across the plates (V)



What is the relative permittivity (a.k.a. dielectric constant)?



What is the relative permittivity (a.k.a. dielectric constant)?

- The ratio of the charge stored with the dielectric between the plates to the charge stored when the dielectric is not present.
- $\epsilon_r = Q / Q_0$
- The greater the relative permittivity, the greater the capacitance of the capacitor.



What does the area under the graph of charge against pd represent ?



What does the area under the graph of charge against pd represent ?

The energy stored by the capacitor.




Describe the  $Q$  against  $t$  graph for the discharging of a capacitor through a resistor.





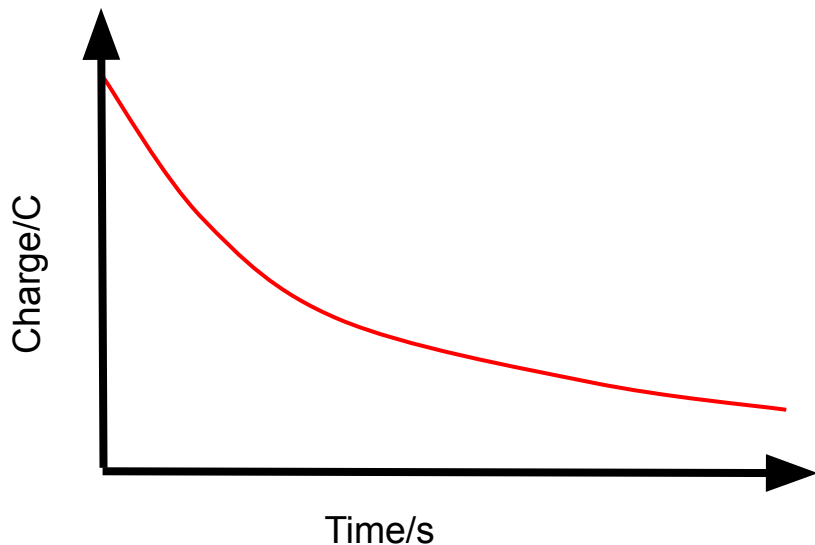
Describe the Q against t graph for the discharging of a capacitor through a resistor.



Describe the  $V$  against  $t$  graph for the discharging of a capacitor through a resistor.



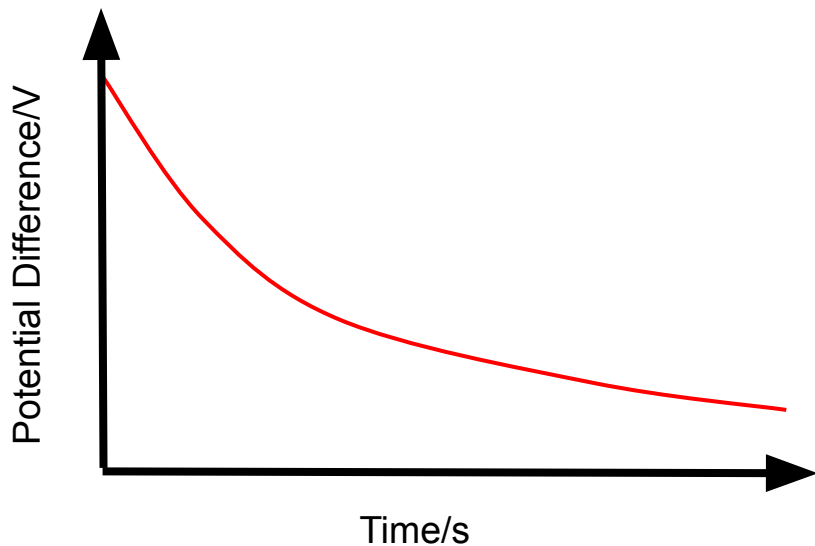
Describe the  $V$  against  $t$  graph for the discharging of a capacitor through a resistor.



Describe the  $I$  against  $t$  graph for the discharging of a capacitor through a resistor.



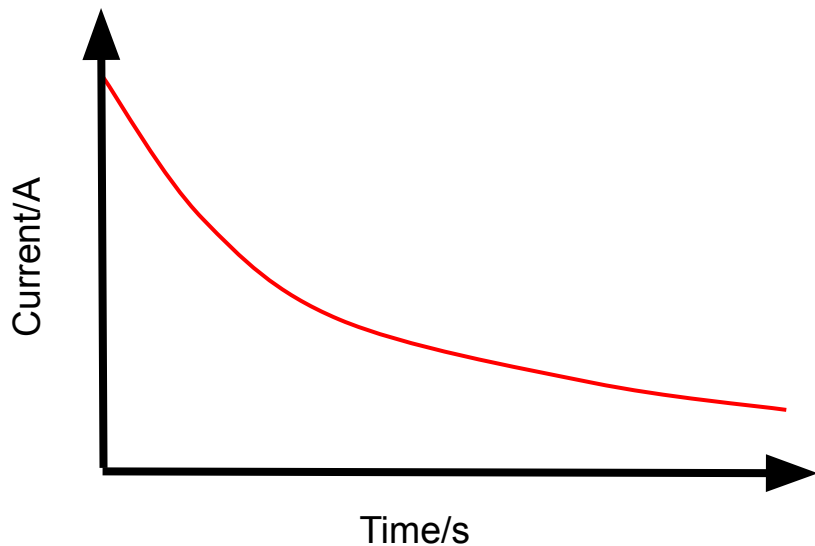
Describe the I against t graph for the discharging of a capacitor through a resistor.



Describe the  $Q$  against  $t$  graph for the charging of a capacitor through a fixed resistor.



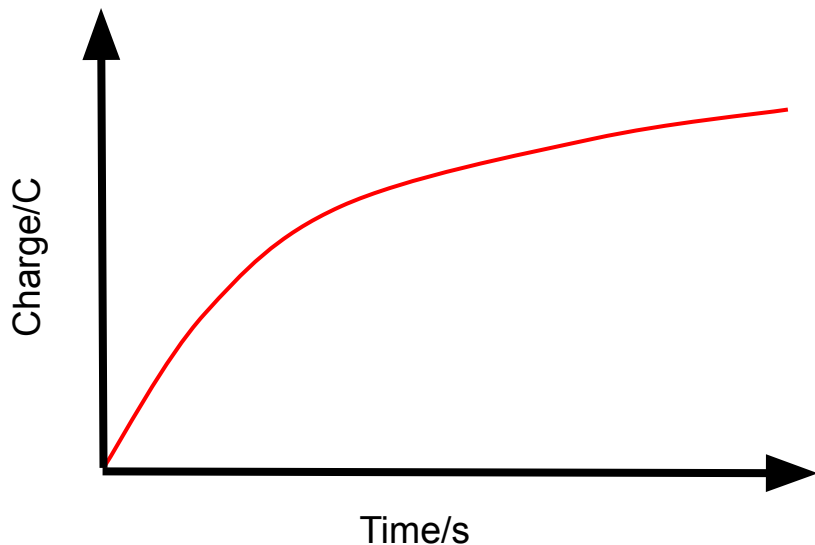Describe the Q against t graph for the charging of a capacitor through a resistor.




Describe the  $V$  against  $t$  graph for the charging of a capacitor through a fixed resistor.





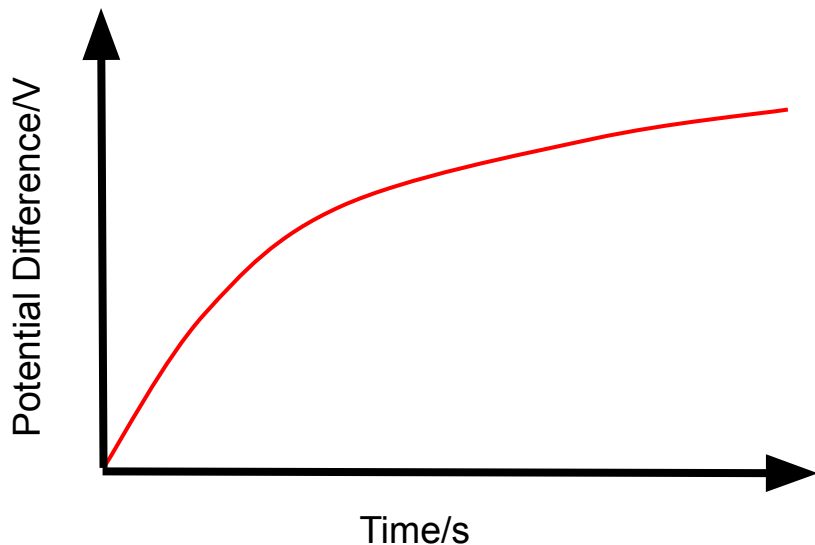Describe the  $V$  against  $t$  graph for the charging of a capacitor through a resistor.




# What is the time constant?


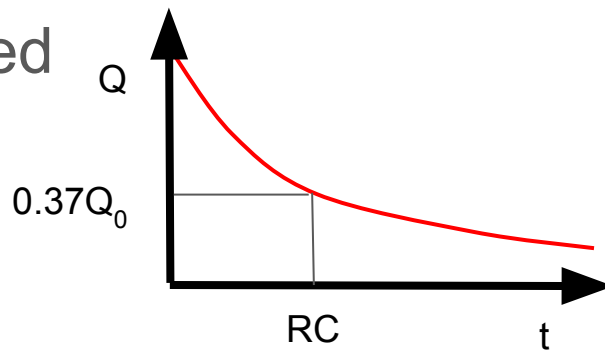
## What is the time constant?

The time it takes for the charge in a capacitor falls to 37% of the initial value (explained in the following slide) given by  $RC$  (resistance x capacitance).

A capacitor is considered fully discharged after 5 time constants.



How was 37% derived when using the time constant?



How was 37% derived when using the time constant?

- Start with the formula  $Q = Q_0 e^{-t/RC}$
- When  $t = RC$  (after 1 time constant), the formula becomes  $Q = Q_0 e^{-1}$
- $e^{-1} \approx 0.37$ , which is where 37% came from.



# What is the half time of a capacitor?



What is the half time of a capacitor?

$$T_{1/2} = 0.69RC$$



What equations do we require for charging a capacitor?





# What equations do we require for charging a capacitor?

Charging up a capacitor produces  $Q = Q_0(1 - e^{-t/RC})$  &  
 $V = V_0(1 - e^{-t/RC})$  where  $V_0$  is the battery PD and  $Q_0 = CV_0$ .



# How does a capacitor charge up?



# How does a capacitor charge up?

1. Electrons move from negative to positive around the circuit.
2. The electrons are deposited on plate A, making it negatively charged.
3. Electrons travel from plate B to the positive terminal of the battery, giving the plate a positive charge.
4. Electrons build up on plate A and an equal amount of electrons are removed from plate B, creating a potential difference across the plates.
5. When the p.d across plates = source p.d., the capacitor is fully charged and current stops flowing.



Describe and explain in terms of the movement of electrons how the p.d across a capacitor changes, when it discharges across a resistor.



Describe and explain in terms of the movement of electrons how the p.d across a capacitor changes, when it discharges across a resistor.

1. Electrons move in opposite direction than when the capacitor was charging up.
2. Charge on one plate A decreases as it loses electrons, and plate B gains electrons, neutralising them.
3. P.d. decreases exponentially across the plates.



State the 3 expressions for the energy stored by a capacitor.



State the 3 expressions for the energy stored by a capacitor.

$$E = \frac{1}{2} (Q^2/C) = \frac{1}{2} (QV) = \frac{1}{2} (CV^2)$$



What 2 factors affect the time taken for a capacitor to charge or discharge?





# What 2 factors affect the time taken for a capacitor to charge or discharge?

- The capacitance of the capacitor,  $C$ . This affects the amount of charge that can be stored by the capacitors at any given potential difference across it.
- The resistance of the circuit,  $R$ . This affects the current in the circuit and how quickly it flows, hence how quickly the capacitor charges/discharges.

