

AQA Physics A-level

Required Practical 9

Investigation of the charge and discharge of capacitors. Analysis techniques should include log-linear plotting leading to a determination of the time constant RC




Discharging capacitor

- Equipment:

- Electrolytic capacitor
- Resistor
- Battery
- Voltmeter
- Switch

- Method:

- Set up the apparatus as shown in the diagram.
- Set the switch to the A position to allow the capacitor to fully charge.
- Move the switch to the B position and start the stopwatch. Observe and record the voltage reading V at time $t=0$ and at 5s intervals as the capacitor discharges until about 120s have passed.
- Repeat the experiment twice more and obtain the average V at each t .
- (Note that the experiment can be repeated for different resistors or capacitors to investigate how the time constant varies with resistance and capacitance).

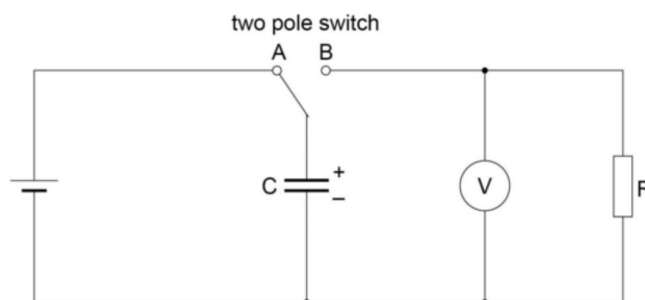

- Graphs and calculations:

- Calculate the natural logarithm of V at each t and tabulate this. Plot a graph of $\ln(V)$ against t and draw a line of best fit. This should yield a straight line graph with negative gradient, showing that the decay of voltage across the capacitor is exponential. The gradient will equal $-1/RC$ (or $-1/\text{time constant}$).
- $V = V_0 e^{-\frac{t}{RC}} \Rightarrow \ln(V) = \frac{-1}{RC}t + \ln(V_0) = \frac{-1}{\tau}t + \ln(V_0)$ where τ is the time constant of the RC circuit.
- If C is known, you can find the time constant using RC and also using the graph and check if they are the same. If C is not known, you can find it using the graph.

- Safety:

- Ensure the capacitor is connected with the correct polarity and that its voltage rating exceeds the voltage of the battery used to prevent it from exploding and releasing harmful chemicals.

- Improvements and notes:

- You can also plot a graph of V against t which will give an exponential decay curve. The time constant can be found from this by finding t when the voltage is approximately 37% of the original voltage (the voltage of the battery).



Charging capacitor

- Equipment:
 - Electrolytic capacitor
 - Resistor
 - Battery
 - Voltmeter
 - Switch
- Method:
 - Set up the apparatus as shown in the diagram.
 - Close the switch and observe and record the voltage reading V at time $t=0$ and at 5s intervals as the capacitor charges until about 120s have passed.
 - Repeat the experiment twice more and obtain the average V for each t .
 - (Like the discharging experiment, this experiment can also be repeated with different resistors or capacitors).
- Graphs and calculations:
 - Plot a graph of V against t . This graph will show an exponential growth curve.
 - $V = V_0(1 - e^{-\frac{t}{RC}})$
- Safety:
 - Ensure the capacitor is connected with the correct polarity and that its voltage rating exceeds the voltage of the battery used to prevent it from exploding and releasing harmful chemicals.
- Improvements and notes:
 - The time constant can be found from the exponential growth curve by finding t when the voltage is approximately 63% of the maximum voltage (the voltage of the battery).

