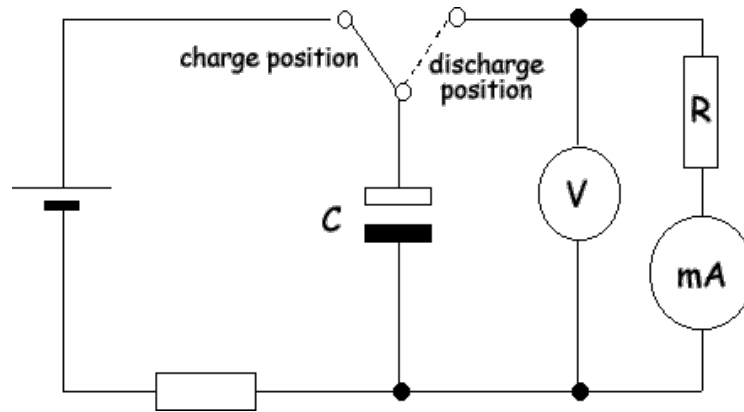


Edexcel Physics A Level

Core Practical 11


Analyse the PD across a charging and discharging Capacitor






Method 1: Charging Capacitor

- Set up a circuit with a **DC power supply**, **high resistance resistor**, **switch**, **capacitor**, **ammeter** and a **voltmeter** around the (initially discharged) capacitor
- Close the switch to **charging** position and start the timer
- Record the **PD** and **current** every **10s**
- Repeat process 3 times, and calculate mean **V** and **I**
- Plot graph of current against time and PD against time

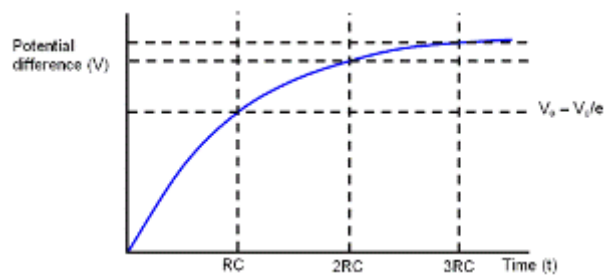

Method 2: Discharging Capacitor

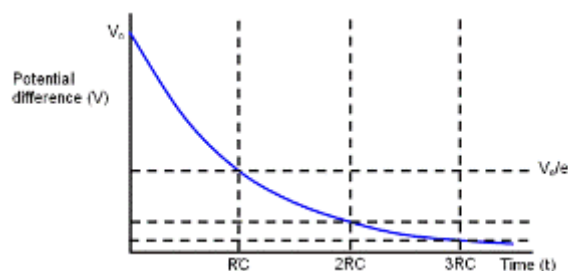- Move switch to the second position for the capacitor to **discharge**
- Record the PD and current every 10s
- Repeat process **3 times**, and calculate **mean V** and **I**
- Plot graph of current against time and PD against time



Safety

- Ensure that the capacitor is connected the right way in the circuit, as to prevent it exploding
- Use low (sub 40V) voltages for open circuit work

Evaluation

- Increasing the circuit **resistance** causes the capacitor to discharge slower; measuring a larger value for time reduces percentage uncertainty (and effect of reaction time)

