


# Edexcel Physics A Level

## Core Practical 12

Calibrate a Thermistor in a Potential Divider circuit as a  
Thermostat




## Method

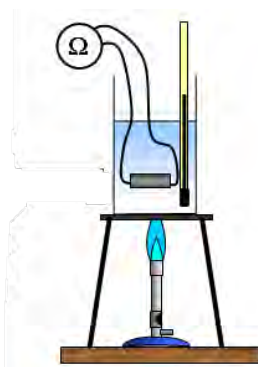

- Set up a circuit with a **power source**, a **fixed resistor**, a **thermistor**, and an **ohmmeter** (around the NTC thermistor)
- Set up a **Bunsen burner**, **tripod**, **gauze**, **beaker with ice**, **stirring rod**, **mercury thermometer to 0.5 C**, and **waterproof thermistor**
- The temperature of water in the beaker changes in **2-5°C increments from 0-100°C** (using crushed **melting ice** to get close to 0°C and placing the thermistor in the interface of the **steam** and water to get close to 100°C)
- Allow time for the temperature to reach **equilibrium**, stir the water, and ensure the thermometer bulb is **completely submerged** in the water and level with the thermistor
- Measure the resistance using the ohmmeter
- Vary the temperature and record resistance
- Plot a **calibration curve** of resistance against temperature
- Use the temperature graph to find the resistance at a given temperature, and use to set up a potential divider circuit using;

$$V_{out} = V_{in} \times \frac{R_1}{R_1 + R_2}$$

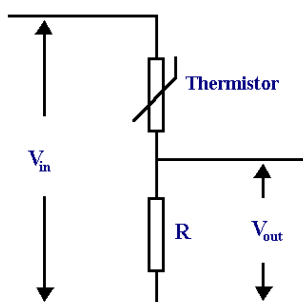for a required output voltage at a given temperature and input voltage



## Safety

- Boiling water/bunsen burner includes a risk of scalds and burns so, do not handle the beaker when hot
- Do not exceed the voltage limit of the thermistor
- Keep leads away from hot things to prevent melting the plastic coating
- Support the thermistor to prevent it tipping the beaker over



## Evaluation

- Alternative to using the ohmmeter: measure current and pd with **voltmeter and ammeter** with adequate ranges
- Fixed points with a **linear change** of a property in temperature are a requirement to form a temperature scale
- Heating slowly allows the semiconductor to **adjust** to the temperature of the water and the thermometer
- Improvement: Heat very slowly over long periods of time using a **data logger** with temperature and **resistance probes** for the water and thermistor respectively
- Read temperature off thermometer at eye level to avoid **parallax errors**
- If the fixed resistor's resistance is **too high**,  $V_{out}$  won't vary enough with temperature and if it's **too low**,  $V_{out}$  may vary across a bigger range than the voltmeter can handle
- Simultaneous reading of two variables (temperature and resistance) may result in systematic error
- Check meter for **zero error** by connecting a lead across terminals so no systematic error in resistance measurements
- Use a **small current** and switch off circuit between readings so no **heating effect** in addition to hot water which would make results inaccurate

