

UNIT 6485	Module 2	5.2.1	Capacitors	
<p>• PRACTICE QUESTIONS (4)</p>				
1	<p>A 2200 μF capacitor is charged to a p.d. of 9.0 V and then discharged through a 100 $\text{k}\Omega$ resistor.</p> <p>(a) Calculate :</p> <p>(i) The initial charge stored by the capacitor. (ii) The time constant of the circuit.</p> <p>(b) Calculate the p.d. after :</p> <p>(i) A time equal to the time constant. (ii) 300 s.</p>			<p>5 A capacitor is discharged through a resistor. The current through the resistor varies according to the following equation :</p> $I = 0.5 \text{ mA} \times e^{-(0.02t)\text{s}}$ <p>(a) What is the initial current flowing through the resistor (when $t = 0$) ?</p> <p>(b) Calculate the current flowing after 30 s.</p> <p>(c) What is the time constant for this circuit ?</p>
2	<p>A 1000 μF capacitor initially stores 20 mC of charge. It is discharged through a 500 $\text{k}\Omega$ resistor. How much charge does it store after 100 s ?</p>			<p>6 A 100 μF capacitor is charged to 6.0 V. It is then discharged through a 500 $\text{k}\Omega$ resistor.</p> <p>(a) What is the TIME CONSTANT for this circuit ?</p>
3	<p>A 2.2 μF capacitor is charged to a p.d. of 6.0 V and then discharged through a 100 $\text{k}\Omega$ resistor. Calculate :</p> <p>(a) The charge and energy stored in the capacitor at 6.0 V,</p> <p>(b) The p.d across the capacitor 0.5 s after the discharge started,</p> <p>(c) The energy stored at this time.</p>			<p>(b) Write down equations of the form $x = x_0 e^{-t/CR}$ to show how :</p> <p>(i) The charge stored by the capacitor,</p> <p>(ii) The current through the resistor,</p> <p>(iii) The p.d. across the capacitor, vary with time.</p>
4	<p>A 4.7 μF capacitor is charged to a p.d. of 12.0 V and then discharged through a 220 $\text{k}\Omega$ resistor. Calculate :</p> <p>(a) The energy stored in this capacitor at 12.0 V,</p> <p>(b) The time taken for the p.d. to fall from 12.0 V to 3.0 V,</p> <p>(c) The energy lost by the capacitor in this time.</p>			<p>7 A washing machine timer uses a capacitor and a resistor in series to switch off the heater after a pre-set time. A 1000 μF capacitor is charged to a p.d. of 25 V, and allowed to discharge through a resistor of 470 $\text{k}\Omega$. If the switch is triggered when the p.d. falls to 5 V, calculate :</p> <p>(a) The time for which the heater is on.</p> <p>(b) The new value of resistor required to operate the heater for 25 minutes.</p>

• HOMEWORK QUESTIONS

- 1 A $5\ \mu\text{F}$ capacitor and a $20\ \mu\text{F}$ capacitor are connected (a) **in series** and (b) **in parallel** to a $100\ \text{V}$ d.c. supply.

Calculate the values of **charge** on and **p.d.** across **each capacitor** in each of the circuits.

- 2 A variable capacitor is set to $200\ \text{pF}$ and connected across a $6.0\ \text{V}$ cell.

(a) Calculate or state the values of the **stored charge Q** , the **capacitance C** , the **p.d. V** across the capacitor and the **energy E** stored in the capacitor.

(b) The capacitance is reduced to $100\ \text{pF}$ with the capacitor still connected to the cell. Which of the four quantities in (a) is **unchanged**? Calculate or state the new values of **Q , C , V and E** .

(c) The capacitor is disconnected from the cell. The capacitance is increased back to $200\ \text{pF}$. Which value of the four quantities will remain **unchanged**? Calculate or state the final values of **Q , C , V and E** .

- 3 (a) One expression for the **energy stored, W** on a charged capacitor is :

$$W = \frac{1}{2} QV$$


Where **Q** is the charge stored and **V** is the potential difference across the capacitor. Show that two other expressions for the energy stored are :

$$W = \frac{1}{2} CV^2 \quad \text{and} \quad W = \frac{1}{2} Q^2/C$$

Where **C** is the capacitance of the capacitor.

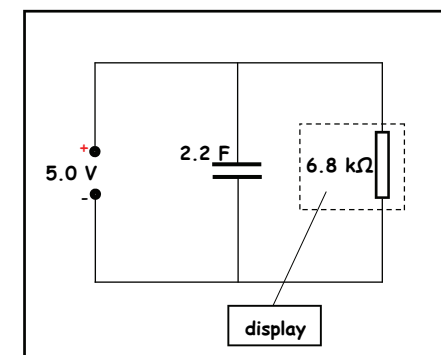- (b) Draw a graph to show how the **energy W in J** stored on a $2.2\ \text{F}$ capacitor varies with the **potential difference V** from 0 to $5.0\ \text{V}$ across the capacitor.

A $2.2\ \text{F}$ capacitor is connected in parallel with the power supply to a digital display for a video/DVD recorder. The purpose of the capacitor is to keep the display working during any disruptions to the electrical power supply.



The diagram opposite shows the $5.0\ \text{V}$ power supply, the capacitor and the display. The input to the display behaves as a $6.8\ \text{k}\Omega$ resistor. The display will light up as long as the voltage across it is at or above $4.0\ \text{V}$.

Suppose the power supply is disrupted.

- (a) Show that the **time constant** of the circuit is **more than 4 hours**.


(b) Find the **energy lost in J** by the capacitor as it discharges from $5.0\ \text{V}$ to $4.0\ \text{V}$.

(c) The **voltage** across the capacitor varies with **time t** according to the equation : $V = V_0 e^{-t/CR}$

Calculate the **time in s** that it takes for the voltage to fall to $4.0\ \text{V}$.

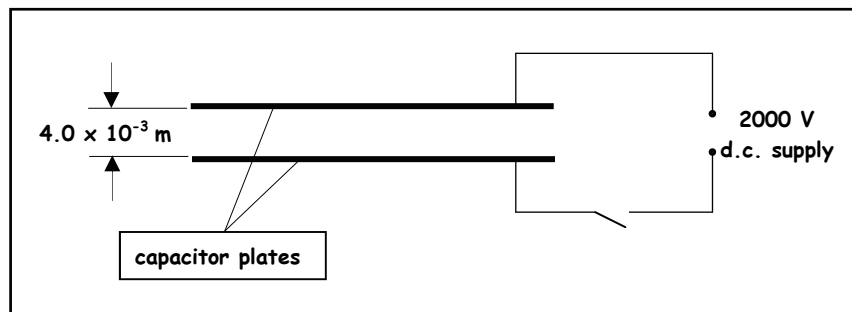(d) Calculate the **mean power consumption in W** of the display during this time.


- 5 The diagram below shows two large, insulated capacitor plates, separated by an air gap of 4.0×10^{-3} m. The capacitance of the arrangement is **200 pF**. The plates are connected by a switch to a **2000 V** d.c. power supply. The switch is closed and then opened.



- (a) Calculate :
- The magnitude of the **electric field strength** between the plates giving a suitable **unit** for your answer.
 - The magnitude in μC of the **charge** on each plate.
 - The **energy** in μJ stored in the capacitor.
- (b) With the switch remaining **open**, the plates are pulled apart until their separation is **doubled**. The capacitor maintains the **same charge**. The electric field strength between the plates is **unchanged**. State the new :
- Voltage** between the plates.
 - Capacitance** of the plates.
 - Energy stored** in the capacitor.
- (c) The energy stored in the capacitor has increased. State the source of this energy.

(OCR A2 Physics - Module 2824 - January 2003)

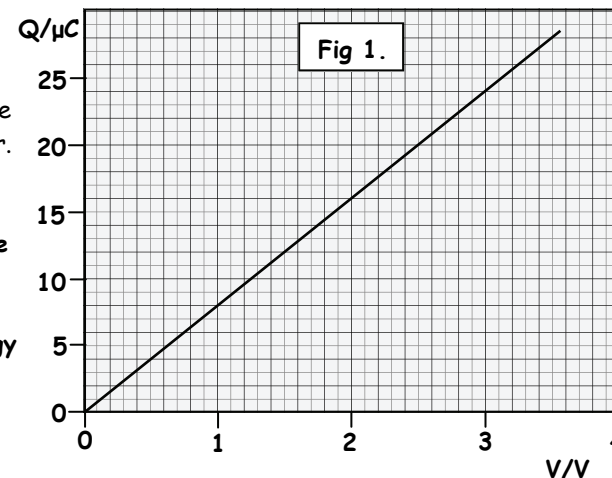- (a) Fig 1. shows the graph of charge Q stored against potential difference V across a capacitor.




- Use the graph to find the **capacitance** of the capacitor.
- Calculate the **energy** in the capacitor when it is charged to **3.0 V**.

- The capacitor is discharged through a resistor. The charge falls to **0.37** of its initial value in a time of **0.040 s**. This is the **time constant** of the circuit. Calculate the **resistance** of the resistor.

- Explain why the **discharge time** of the capacitor is **independent** of the **initial charge** on the capacitor.

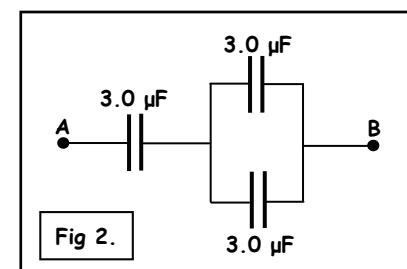
- (b) You are provided with a number of **identical** capacitors, each of capacitance **3.0 μF** . Three are connected in a **series** and **parallel** combination as shown in Fig 2.



- Show that the total capacitance between the terminals **A** and **B** is **2.0 μF** .
- Draw a diagram to show how you can produce a **total capacitance** of **2.0 μF** using six **3.0 μF** capacitors.

(OCR A2 Physics - Module 2824 - January 2005)

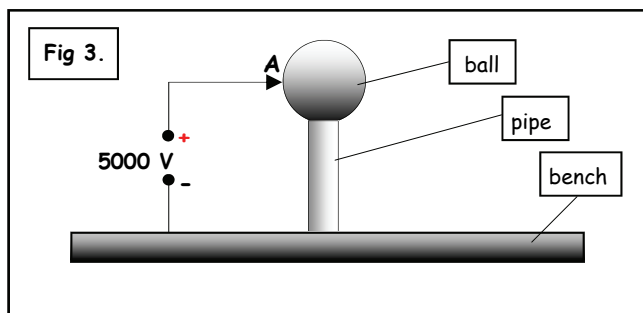
- 7 Fig 3. shows a football balanced above a metal bench on a length of plastic drain pipe. The surface of the ball is coated with a smooth layer of an electrically conducting paint. The pipe insulates the ball from the bench.



- (a) The ball is charged by touching it momentarily with a wire **A** connected to the **positive** terminal of a **5000 V** power supply. The capacitance **C** of the ball is $1.2 \times 10^{-11} \text{ F}$. Calculate the charge Q_0 on the ball. Give a suitable **unit** for your answer.
- (b) The charge on the ball leaks slowly to the bench through the plastic pipe, which has a resistance **R** of $1.2 \times 10^{15} \Omega$.
- (i) Show that the **time constant** for the ball to discharge through the pipe is about $1.5 \times 10^4 \text{ s}$.
- (ii) Show that the **initial** value of the **leakage current** is about $4 \times 10^{-12} \text{ A}$.
- (iii) Suppose that the ball continues to discharge at the constant rate calculated in (ii). Show that the charge Q_0 would leak away in a time equal to the **time constant**.
- (iv) Using the equation for the charge Q at time t , $Q = Q_0 e^{-t/CR}$

Show that, in practice, the ball loses about 2/3 of its charge in a time equal to **one time constant**.

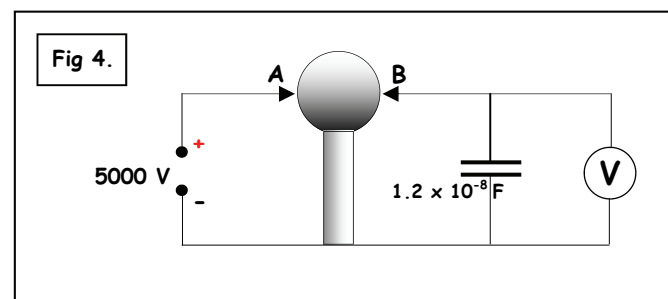- (c) The ball is recharged to **5000 V** by touching it momentarily with wire **A**. The ball is now connected in **parallel** via wire **B** to an uncharged capacitor of capacitance $1.2 \times 10^{-8} \text{ F}$ and a voltmeter as shown in Fig 4.



- (i) The ball and the uncharged capacitor act as two capacitors in **parallel**. The total charge Q_0 is shared instantly between the two capacitors. **Explain** why the charge is $Q_0/1000$.
- (ii) Hence or otherwise calculate the **initial reading V** on the voltmeter.

UNIT 6484

Module 2

4.2.3

UNIT 6484

Module 2

4.2.3

UNIT 6484

Module 2

4.2.3

UNIT 6484

Module 2

4.2.3

UNIT 6484

Module 2

4.2.3

UNIT 6484

Module 2

4.2.3