

Centre Number						Candidate Number			
Surname									
Other Names									
Candidate Signature									

For Examiner's Use	
Examiner's Initials	
Question	Mark
1	
2	
TOTAL	



General Certificate of Education
Advanced Subsidiary Examination
June 2015

Physics

(Specifications A and B)

PHA3/B3/XPM1

Unit 3 Investigative and Practical Skills in AS Physics
Route X Externally Marked Practical Assignment (EMPA)

Section A Task 1

For this paper you must have:

- a calculator
- a pencil
- a ruler.

Instructions

- Use black ink or black ball-point pen.
- Fill in the boxes at the top of this page.
- Answer **all** questions.
- You must answer the questions in the spaces provided. Do not write outside the box around each page or on blank pages.
- Show all your working.
- Do all rough work in this book. Cross through any work you do not want to be marked.

Information

- The marks for questions are shown in brackets.
- The maximum mark for Section A Task 1 is 16.

Section A Task 1


Follow the instructions given below.

Give the information required in the spaces provided.

No description of the experiment is required.

- 1** You are to determine the resistance per metre of a resistance wire using the circuit in **Figure 1**.

Figure 1

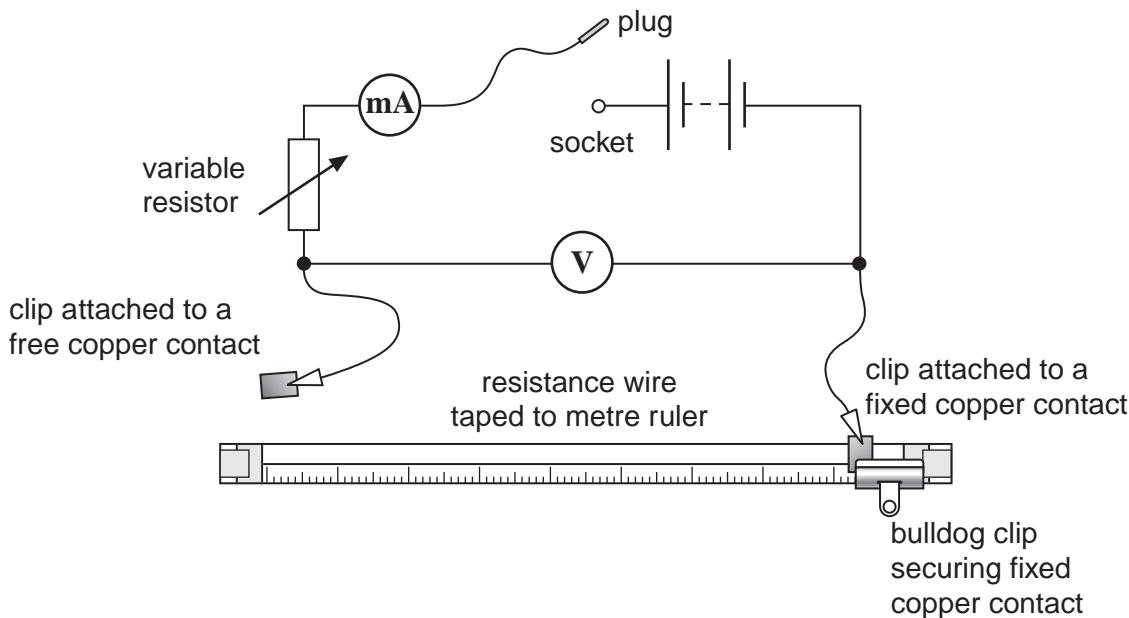

- 1 (a)** Connect the plug to the socket.
 Hold the free copper contact firmly on the resistance wire so there is about 0.8 m of wire between the free and fixed contacts.
 Without moving the free contact, adjust the setting of the variable resistor until the current in the circuit is about 20 mA.
- 1 (a) (i)** Determine and record the length l_a of the wire connected between the contacts.

$$l_a = \dots$$

- 1 (a) (ii)** Read and record the current I_a in the wire and the potential difference (pd) V_a across the wire.

$$I_a = \dots$$

$$V_a = \dots$$

1 (b) Move the free contact so there is about 0.2 m of resistance wire between the free and fixed contacts.

Without moving the free contact adjust the setting of the variable resistor until the current in the circuit is once again about 20 mA.

1 (b) (i) Determine and record the length l_b of the wire now connected between the clips.

$$l_b = \dots$$

1 (b) (ii) Read and record the current I_b in the wire and the pd V_b across the wire.

[2 marks]

$$I_b = \dots$$

$$V_b = \dots$$

When you have completed parts (a) and (b) remove the plug from the socket.

Unclip the two crocodile clips from the copper contacts and place these and the resistance wire arrangement to one side.

Question 1 continues on the next page

Turn over ►

- 1 (c) (i) Determine r_a , the resistance per metre of the resistance wire based on your readings from part (a).

.....
.....
.....

$$r_a = \dots$$

- 1 (c) (ii) Determine r_b , the resistance per metre of the resistance wire based on your readings from part (b).

[2 marks]

.....
.....
.....

$$r_b = \dots$$

- 1 (d) Explain, without calculation, why the percentage uncertainty in r_a is less than the percentage uncertainty in r_b .

[3 marks]


.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....

Turn over for the next question

**DO NOT WRITE ON THIS PAGE
ANSWER IN THE SPACES PROVIDED**

Turn over ►

- 2** You are to investigate a circuit containing resistors X and Y of unknown resistance and a switch S.
 Connect the circuit consisting of X and Y so that the clips are **attached directly** to the ends of X, as shown in **Figure 2**.

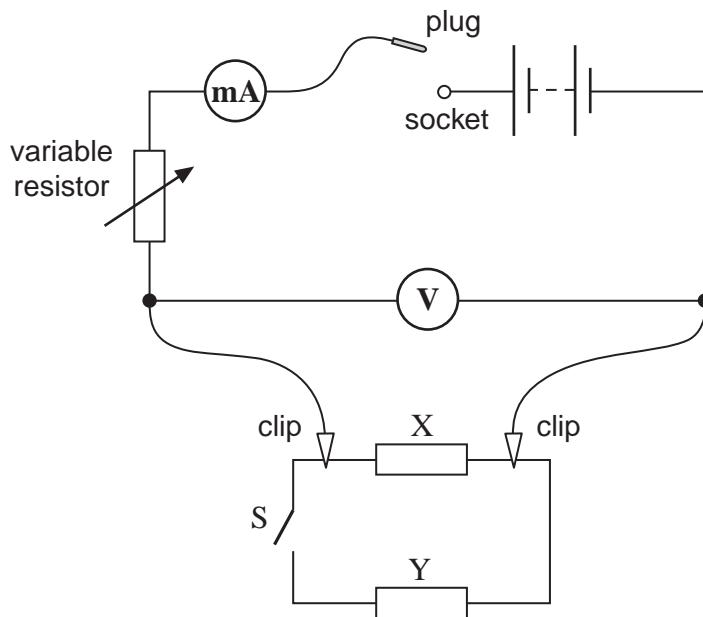Figure 2

- 2 (a) (i)** With S in the off (open) position, connect the plug to the socket.
 Adjust the variable resistor until the current in the circuit is a **minimum**.
- 2 (a) (ii)** Read and record in **Table 1** the current I_1 and potential difference V_1 .
- 2 (a) (iii)** Without adjusting the variable resistor, turn S on.
 Read and record in **Table 2** the current I_2 and potential difference V_2 .
- 2 (a) (iv)** Turn S off.
 Adjust the variable resistor so that the current in the circuit increases.
 Using the procedure as before obtain new values of I_1 and V_1 and of I_2 and V_2 .
 Continue until you have **five** sets of readings.
Disconnect the plug from the socket.

[2 marks]**Table 1**

I_1 / mA	V_1 / V

Table 2

I_2 / mA	V_2 / V


2 (b) Add a suitable **single** scale to the vertical axis on **Figure 3** below and plot,
[2 marks]

2 (b) (i) a graph of I_1 against V_1 ,

2 (b) (ii) a graph of I_2 against V_2 .

Figure 3

I / mA

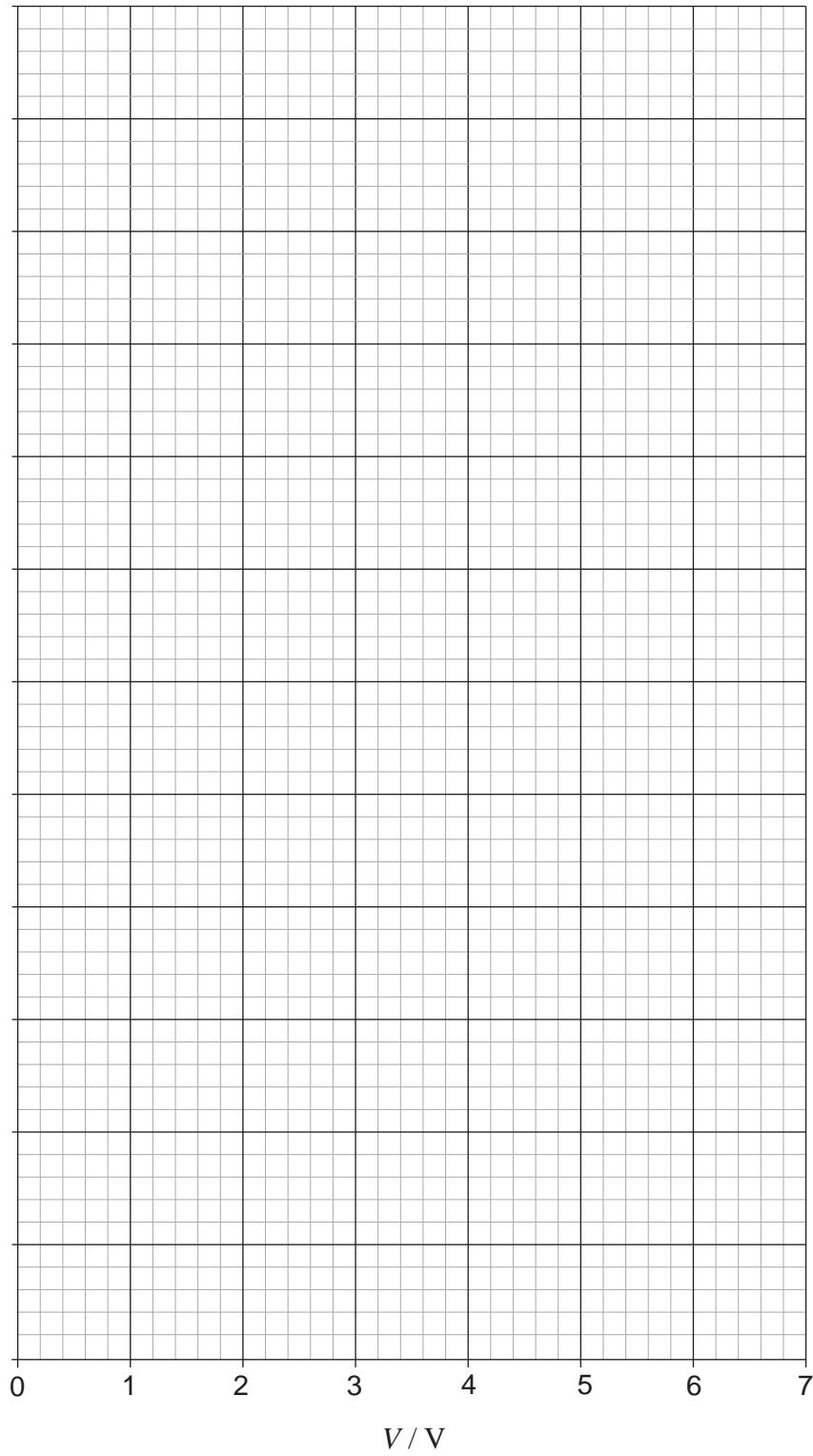

Turn over ►

2 (c) Use your graphs (**Figure 3**) to determine

2 (c) (i) the resistance of X,

[2 marks]

.....
.....
.....

resistance of X =

2 (c) (ii) the resistance of Y.

[3 marks]

.....
.....
.....
.....
.....
.....
.....

resistance of Y =

9

END OF QUESTIONS