

## Physics

### Unit 3 Investigative and Practical Skills in AS Physics ISA (P) Emf and Internal Resistance

#### Task Sheet

**This task is worth 10 marks**

*You are advised to read through these instructions before beginning your work.*

**You are going to carry out an experiment to investigate the relationship between the terminal potential difference across and the current through a cell or battery when connected to a range of different value resistors.**

- *SWITCH OFF OR DISCONNECT THE CELL BETWEEN READINGS*
- *Set up a circuit with the cell, ammeter and a resistor in **series**. Connect a voltmeter to measure the pd across the cell terminals.*
- *Write down the precision of the instruments used.*
- *For each resistor, record the current and terminal pd values in a suitable table. Include the resistor values in the table. Take readings for the eight different resistors provided.*
- *Draw a circuit diagram of the circuit you used.*
- *Plot a graph of terminal pd (on the y-axis) and current (on the x-axis).*

#### **After the Investigation**

*At the end of the investigation, hand in all your written work, including the graph, to the supervisor.*

*This documentation will be required for Stage 2 of the ISA. Please ensure that you have entered your centre details, candidate number and name on all the sheets you have completed.*