

Centre Number						Candidate Number				
Surname										
Other Names										
Candidate Signature										

For Examiner's Use	
Examiner's Initials	
Question	Mark
1	
2	
TOTAL	



General Certificate of Education
Advanced Level Examination
June 2014

Physics (Specifications A and B)

PHA6/B6/XPM1

Unit 6 Investigative and Practical Skills in A2 Physics
Route X Externally Marked Practical Assignment (EMPA)

Section A Task 1

For this paper you must have:

- a calculator
- a pencil
- a ruler.

Instructions

- Use black ink or black ball-point pen.
- Fill in the boxes at the top of this page.
- Answer **all** questions.
- You must answer the questions in the spaces provided. Do not write outside the box around each page or on blank pages.
- Show all your working.
- Do all rough work in this book. Cross through any work you do not want to be marked.

Information

- The marks for questions are shown in brackets.
- The maximum mark for Section A Task 1 is 14.

There are no questions printed on this page

**DO NOT WRITE ON THIS PAGE
ANSWER IN THE SPACES PROVIDED**

Section A Task 1


Follow the instructions given below.

Give the information required in the spaces provided.

No descriptions of the experiments are required.

- 1** You are to determine the resistance of a resistor R of unknown resistance using the circuit shown in **Figure 1**.

Figure 1

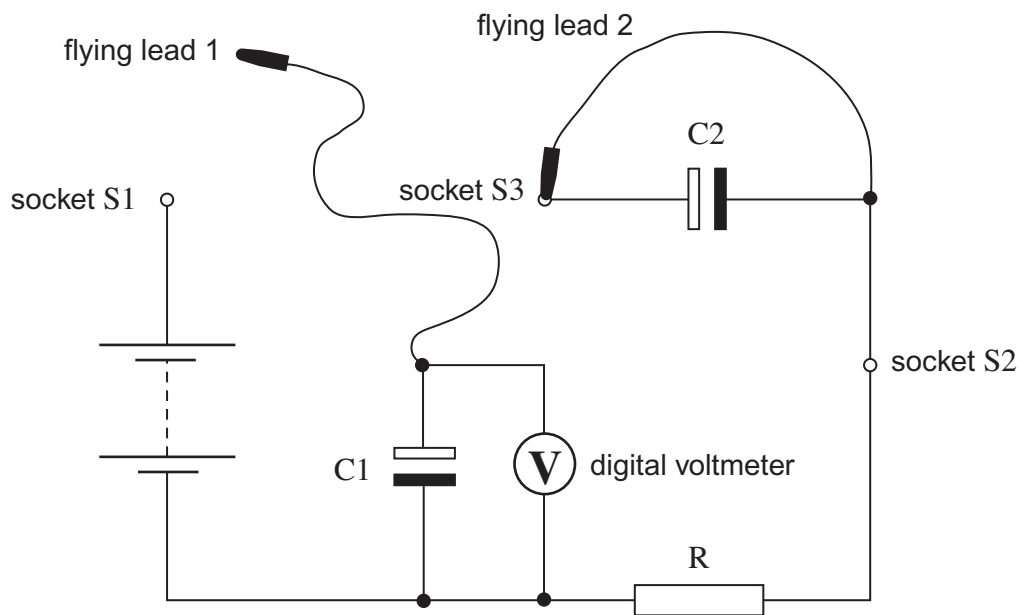

This circuit is used for both Question 1 and Question 2 in Section A Task 1. Connect flying lead 2 to socket S3 as shown in **Figure 1**; **Keep this lead connected to S3 whilst making the measurements in Question 1.**

- 1 (a)** Connect flying lead 1 to socket S1 so that capacitor C1 is fully charged.
- 1 (a) (i)** Read and record the voltmeter reading, \mathcal{E} .

$\mathcal{E} = \dots\dots\dots$

Turn over ►

- 1 (a) (ii) Remove flying lead 1 from socket S1 and connect this **without delay** to socket S2 so the voltmeter reading decreases as C1 discharges through resistor R.

Start the stopwatch when the voltmeter reads 80% of ε .

Measure and record in **Table 1**, the times at which the voltmeter reads 40% and 20% of ε .

[2 marks]

Table 1

Voltmeter reading	Time/s
40% of ε	
20% of ε	

- 1 (b) Explain whether the results in part (a) show that the voltmeter reading is decreasing exponentially.

[1 mark]

.....

.....

.....

.....

- 1 (c) Use your results to calculate the resistance of resistor R.
The capacitance of capacitor C1 is provided for your use; you may assume that the voltmeter has infinite resistance.


You may wish to use the equation $V = V_0 e^{-\frac{t}{RC}}$

[2 marks]

resistance of resistor R =

- 1 (d) Most analogue voltmeters, such as that shown in **Figure 2**, have a finite resistance.

Figure 2

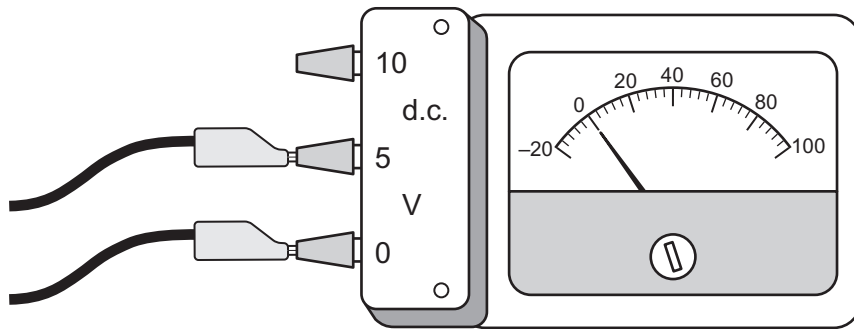

A student carries out the experiment using an analogue voltmeter that has the same resistance as resistor R.

State and explain how the result for resistance of R obtained by the student will compare with **your** result.

[3 marks]

.....

.....

.....

.....

.....

.....

.....

.....

.....

Turn over for the next question

Turn over ►

- 2 (a) (iii)** Remove flying lead 1 from S3 and connect it to S1 to recharge C1.
Record the voltmeter reading, V_B , in the top row of **Table 3**.
- 2 (a) (iv)** Disconnect the lead from S1 and without delay connect it to S3, starting the stopwatch as you do this.
Read and record further values of V_B at 10 second intervals to complete **Table 3**.

[1 mark]

Table 3

t/s	V_B/V
0	
10	
20	
30	
40	
50	
60	

You are not required to repeat the experiment but should you need to do so, disconnect flying lead 1 from S3 and flying lead 2 from S2. Briefly connect flying lead 2 to S3 to discharge C2 before reconnecting this lead to S2. You may now recommence the procedure starting at part 2 (a)(i).

- 2 (b)** Evaluate $\frac{2\varepsilon - V_A}{V_B}$ using your values of V_A and V_B at $t = 60$ s.

[1 mark]

.....

.....

.....


$$\frac{2\varepsilon - V_A}{V_B} = \dots\dots\dots$$

Turn over ►

- 2 (c)** A student performed the experiment you carried out in part 2 (a).
The student did not stop the watch at the end of part 2 (a)(ii). He connected flying lead 1 to S1 at $t = 65$ s then reconnected this lead to socket S3 at $t = 70$ s.
- 2 (c) (i)** Complete the sketch graph in **Figure 4** to show how the pd across C1 varied between $t = 70$ s and $t = 130$ s.
- 2 (c) (ii)** Add a second line to **Figure 4** to show how the pd across C2 varied between $t = 0$ s and $t = 130$ s.

[4 marks]

Figure 4

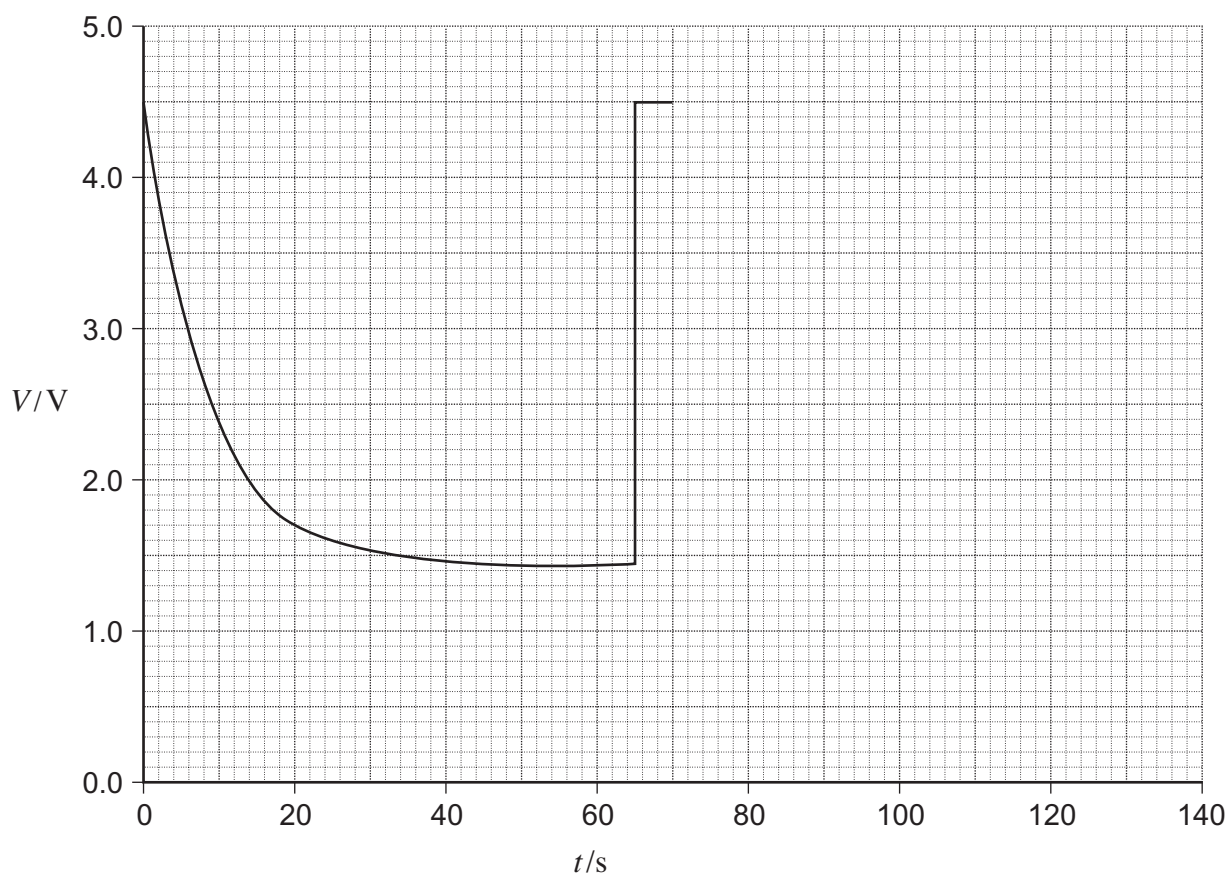

6

END OF QUESTIONS