

Cambridge International Examinations

Cambridge International Advanced Subsidiary and Advanced Level

AS & A Level	Cambridge International Advanced Subsidiary	and Advanced Le	VCI
CANDIDATE NAME			
CENTRE NUMBER		CANDIDATE NUMBER	
PHYSICS			9702/35
Paper 3 Adva	nced Practical Skills 1		May/June 2016
			2 hours
Candidates ar	swer on the Question Paper.		
Additional Mat	erials: As listed in the Confidential Instructions.		

READ THESE INSTRUCTIONS FIRST

Write your Centre number, candidate number and name on all the work you hand in.

Write in dark blue or black pen.

You may use an HB pencil for any diagrams or graphs.

Do not use staples, paper clips, glue or correction fluid.

DO NOT WRITE IN ANY BARCODES.

Answer both questions.

You will be allowed to work with the apparatus for a maximum of one hour for each question.

You are expected to record all your observations as soon as these observations are made, and to plan the presentation of the records so that it is not necessary to make a fair copy of them.

You are reminded of the need for good English and clear presentation in your answers.

Electronic calculators may be used.

You may lose marks if you do not show your working or if you do not use appropriate units.

Additional answer paper and graph paper should be used only if it becomes necessary to do so.

At the end of the examination, fasten all your work securely together.

The number of marks is given in brackets [] at the end of each question or part question.

For Exam	iner's Use
1	
2	
Total	

This document consists of 10 printed pages and 2 blank pages.





2

BLANK PAGE

You may not need to use all of the materials provided.

- 1 In this experiment, you will investigate how the current in a circuit changes as the resistance of the circuit is changed.
 - (a) (i) Set up the apparatus as shown in Fig. 1.1.

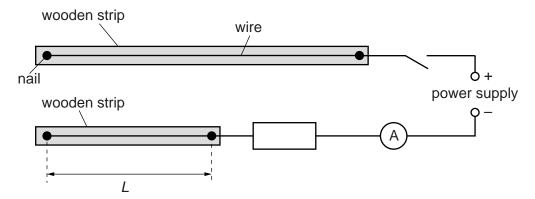


Fig. 1.1

(ii) Measure and record the length *L* of the shorter wire.



(b) (i) Complete the circuit as shown in Fig. 1.2.

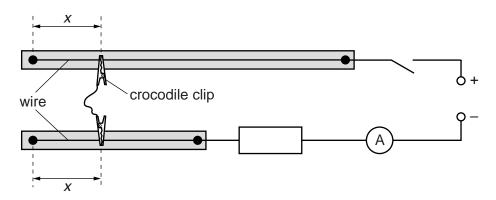


Fig. 1.2

Each crocodile clip should be attached to a wire at the **same distance** *x* from the end of the wire, as shown in Fig. 1.2.

(ii) Measure and record the distance x.




(iii) Close the switch.

(iv) Record the ammeter reading I.

(v) Open the switch.

(c)	Change x and repeat (b) until you have six sets of readings of x and I .
	Include values of $\frac{1}{I}$ in your table.

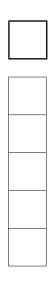

[9]

- (d) (i) Plot a graph of $\frac{1}{I}$ on the *y*-axis against *x* on the *x*-axis. [3]
 - (ii) Draw the straight line of best fit. [1]
 - (iii) Determine the gradient and *y*-intercept of this line.

© UCLES 2016

	-		-	\bot		+++++	\bot		\bot	$oldsymbol{\sqcup}$		+++
	++++		++++++	+++++	\cdots	++++++	+++++	++++++	++++			+++
+++++	++++	++++++	++++++++++++++++++++++++++++++++++++	+++++	\cdots	\cdots	+++++	++++++	++++	++	+	+++
++++	++++	+++++	++++++++++++++++++++++++++++++++++++	+++++	 	+++++	+++++	+++++	++++	++++++	 	+++
	++++	++++++	+++++		 		+++++		++++			
												+++
			++++++++++++++++++++++++++++++++++++									
\bot	+		\square	\bot		\cdots	\perp	\cdots	\Box			
\bot	++++		++++++	\bot			+++++	++++++	++++			+++
++++	++++		++++++++++++++++++++++++++++++++++++	+++++	\cdots	\cdots	+++++		++++	+++++		+++
	++++		++++++	+++++			+++++	++++++	++++	+++++		+++
-	++++		++++++	+++++	+++++		+++++		+++++	-		+++
	++++				 			 		 		+++
++++			+++++							-		+++
	++++				 			 				
	++++											
++++	++++		+++++	+++++	+++++	++++++++++++++++++++++++++++++++++++	+++++	+++++	++++			
\perp	\perp								\Box			$\perp \perp \perp$
\longrightarrow	+		\cdots	\bot		\cdots	+	++++++	++++	\Box		$\perp \perp \perp$
\bot	+						+	++++++	++++			+++
++++	++++		++++++	+++++					++++	$\overline{}$		+++
-	++++		++++++++++++++++++++++++++++++++++++	+++++			+++++		++++	+++++		+++
++++	++++	+++++	++++++	+++++	+++++	+++++	+++++	+++++	++++			+++
++++	++++	++++++	++++++	+++++	+++++	+++++	+++++	++++++	++++	++++++++++++++++++++++++++++++++++++	 	+++
 	++++	 	 	 	 	 	 	 	++++	 	 	+++
 	++++	 	 	 	 	 	 	 	++++	 	 	+++
 	 	 	 				 					+++
	$\Box\Box\Box$											
												ш
\bot	+		\Box	++			+		\Box			\Box
+++T	+++1	\Box	++++	++++	+++++	+++++	++++	+++++	++++	$\sqcup \sqcup \sqcup \sqcup \sqcup$		Π
++++	++++	+++++	+++++	++++	+++++	+++++	+++++	+++++	++++	+++++		+++
++++	++++	++++++	++++++++++++++++++++++++++++++++++++	++++++	++++++	++++++++++++++++++++++++++++++++++++	++++++	++++++	++++	++++++++++++++++++++++++++++++++++++	++++++	+++
++++	++++	+++++	++++++++++++++++++++++++++++++++++++	++++++	 	 	+++++	+++++	++++	++++++++++++++++++++++++++++++++++++	 	+++
++++	++++	+++++	++++++++++++++++++++++++++++++++++++	++++++	 	 	+++++	+++++	++++	+++++	 	+++
++++	++++	 	+++++	+++++	 	 	+++++	+++++	++++	 	 	+++
 	++++	 	 	 	 	 	 	 	++++	 	 	+++
1111	++++	 	 	 	 	 	11111	 				+++
 	 	 	 	 	 	 	 	 	 	 	 	+++
++++							 	 				
+++T	+++T	\Box	++++	++++		$\sqcup \sqcup \sqcup \sqcup \sqcup$	++++	++++	\Box	$\sqcup \sqcup \sqcup \Box$		++T
++++	++++	+++++	++++++++++++++++++++++++++++++++++++	+++++	+++++	+++++	+++++	++++++	++++	+++++		+++
++++	++++	++++++	++++++++++++++++++++++++++++++++++++	+++++	+++++	++++++	+++++	+++++	++++	++++++	+++++	+++
++++	++++		++++++++++++++++++++++++++++++++++++	+++++					++++	$\overline{}$		+++
	+									$\overline{}$		+++
 	++++	 	 	 	 	 	 	 	 	 	 	+++
 	++++	 	 	 	 	 	 	 				+++
-	+		+++++									+++
\rightarrow												
												1 1 1
												Ш

(e) The quantities I and x are related by the equation

$$\frac{1}{I} = -Px + Q$$

where P and Q are constants.

Using your answers in **(d)(iii)**, determine values for P and Q. Give appropriate units.

P=		
Q =		
	2	

(f) (i) The e.m.f. *E* of the d.c. power supply is given on the card. Record *E*.

(ii) Theory suggests that

$$Q = \frac{R}{E} + \frac{3PL}{2}$$

where *R* is the resistance of the resistor.

Use values in (a)(ii), (e) and (f)(i) to determine the value of R.

[Total: 20]



PMT

You may not need to use all of the materials provided.

- 2 In this experiment, you will investigate the position of a wooden strip with several forces acting on it.
 - (a) (i) Balance the wooden strip on the pivot as shown in Fig. 2.1.

The distance between one end of the wooden strip and the pivot is *C* when the wooden strip is balanced.

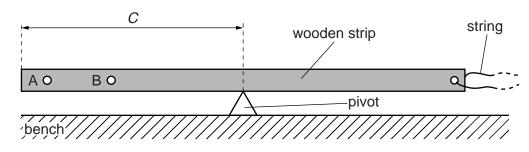


Fig. 2.1

(ii) Measure and record C.

(iii) Measure and record the distance *d* between the end of the wooden strip and the centre of hole A as shown in Fig. 2.2.



Fig. 2.2

(iv) Calculate (C-d).

$$(C-d) = \dots [1]$$

(b) (i) Set up the apparatus as shown in Fig. 2.3 with the nail through hole A.

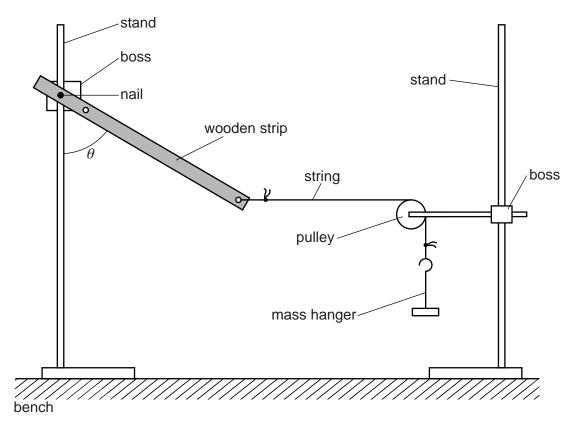


Fig. 2.3

Adjust the apparatus so that the string is parallel to the bench. The angle θ is the angle between the wooden strip and the stand.

(ii) Measure and record θ .

(iii) Estimate the percentage uncertainty in your value of θ .

	N Calculato	(tan A _ 1	١
TO.	Calculate	(lano – i	,

Give your answer to a suitable number of significant figures.

$(\tan \theta - 1) = \dots [2]$	

(d) Using hole B, repeat (a)(iii), (a)(iv), (b)(i), (b)(ii) and (c).

$$(C-d) = \dots$$

$$(\tan\theta - 1) = \dots$$
 [3]

(e) It is suggested that the relationship between θ are	
	ו מ חו
(c) It is suggested that the relationship between v an	iu u i

$$(\tan\theta - 1) = \frac{k}{(C - d)}$$

where k is a constant.

1	/i\	Llcina	VOLIE	data	calculate	two	Values	Ωf	1
١	1)	USITING	your	uala,	caiculaie	LWO	values	ΟI	n.

	first value of $k = \dots$	
	second value of $k = \dots$	
	[1]	
(ii)	Explain whether your results support the suggested relationship.	

(f)	(i)	Describe four sources of uncertainty or limitations of the procedure for this experiment.
		1
		2
		3
		4
		[4]
	(ii)	Describe four improvements that could be made to this experiment. You may suggest the use of other apparatus or different procedures.
		1
		2
		3
		4
		[4]

[Total: 20]



12

BLANK PAGE

Permission to reproduce items where third-party owned material protected by copyright is included has been sought and cleared where possible. Every reasonable effort has been made by the publisher (UCLES) to trace copyright holders, but if any items requiring clearance have unwittingly been included, the publisher will be pleased to make amends at the earliest possible opportunity.

To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced online in the Cambridge International Examinations Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download at www.cie.org.uk after the live examination series.

Cambridge International Examinations is part of the Cambridge Assessment Group. Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.