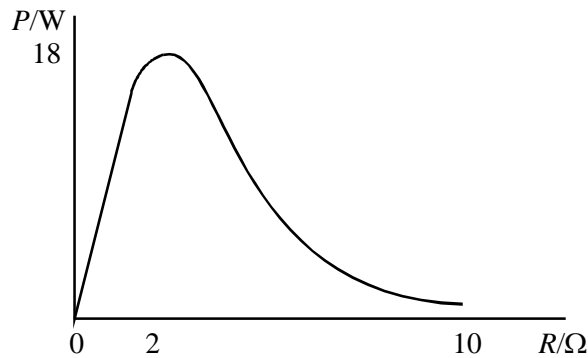


## Internal resistance practice question answers

1. As  $I$  rises terminal voltage of A falls (1)  
 due to internal resistance of A/ "lost volts" (1) 2
- (i) 'Lost volts'  $V = Ir = 10.0 \times 0.40 = 4.0 \text{ V}$  (1)  
 $V_B = 28.0 - V_A = 28.0 - (20.0 + 4.0) = 12.0$  (1) 2
- (ii)  $P = VI = 28.0 \times 10.0 = 280 \text{ W}$   
 Power supplied = 280 W (1) 1
- (iii)  $P = I^2r = 10.0^2 \times 0.40 = 40 \text{ W}$   
 Power wasted = 40 W (1) 1
- (iv)  $\text{Eff} = \frac{280}{320} = 0.88 = 88\%$  (1) 2
- Advantage = Renewable supply/last longer (1)
- Disadvantage = Depends on illumination/high internal resistance/large array needed for power required (1) 2

**[10]**

2. Explanation: .
- $I = E/r + R$  (1) 1
- Appropriate formula for cell E9:  
 $C9 * D9 \text{ OR } RI \text{ OR } 1 \Omega \times 4 \text{ A}$  (1) 1
- Appropriate formula for cell F 11  
 $D11 * E11 \text{ OR } VI \text{ OR } 3\text{A} \times 6\text{V} \text{ OR } C11 * D11 * D11$   
 $\text{OR } RI^2 \text{ OR } 2 \Omega \times (3 \text{ A})^2$  (1) 1
- Short circuit current:  
 6 A (1) 1
- Explanation:  
 $r$  and  $R$  in series  $\rightarrow$  potential division (1) 1  
 as  $R \uparrow$ ,  $r$  constant  $\rightarrow R$  has greater share of 12 V (1) 1  
 OR other valid argument
- Sketch graph of power against resistance:



18 (1)  
 2 (1)  
 Shape including asymptote (1) 3

Comment:

Maximum when  $R = r$  (1)  
 in accordance with maximum power theorem (1)  
 OR  $P \rightarrow 0$  as  $R \rightarrow \infty$  (1) Max 2

[11]

3. Meaning of m

$\times 10^{-3}$  (1) 1

Calculation of resistance for reading 3

$R = V/I$  OR  $R = 74 \times 10^3 \text{ V} \div 150 \times 10^{-9} \text{ A}$  [ecf for milli] (1)

$R = 4.9 \times 10^5 \Omega$  (1) 2

Calculation of power for reading 4

$P = I \times V$  OR  $P = \frac{V^2}{R}$  OR  $P = I^2 R$  (1)

$= 210 \times 10^{-9} \text{ A} \times 57 \times 10^{-3}$  (1) 2

$= 1.2 \times 10^{-8} \text{ W}$

Plotting points on graph

Two correct points (1)

Third correct point (1)

Best fit straight line for points as they appear on student's graph (1) 3

Predicting short-circuit current

Correct from graph, e.g 450 nA (1) 1

Suggested e.m.f

Correct from graph, or table, 110 mV (1) 1

Explanation of why voltage falls

Cell has internal resistance/ "lost volts" (1)

"Lost volts" =  $Ir$ , so lost volts increase as current increases

OR

$V = E - Ir$ , so  $V$  decreases as  $I$  increases (1) 2

[12]

4. Explanation of assumption that voltmeter does not affect values
- Voltmeter has very high resistance/takes very small current (1) 1
- Current through X
- $4.8 \text{ A} \div 6 = 0.8 \text{ A}$
- OR  $48 \text{ V} \div 60 \Omega = 0.8 \text{ A}$  (1) 1
- Value missing from E7
- $P = IV$
- $P = 4.4 \text{ A} \times 53 \text{ V} = 233 \text{ W}$  (1) 1
- Description of appearance of lamp X as lamps switched on
- Gets dimmer
- from table, voltage decreasing / current in X decreasing / power per lamp decreasing (1)
- So  $P$  decreases (1) 3
- Formula for cell C6
- $I = \epsilon / R_{tot}$  (1)
- $I = 120 / (15 + B6)$  (1) 2
- Effect of internal resistance on power
- Power has a maximum value (1)
- when external resistance = internal resistance (1) 2

[10]