

Q1. A $1000\ \mu\text{F}$ capacitor, initially uncharged, is charged by a steady current of $50\ \mu\text{A}$. How long will it take for the potential difference across the capacitor to reach $2.5\ \text{V}$?

- A 20 s
- B 50 s
- C 100 s
- D 400 s

(Total 1 mark)

Q2. In experiments to pass a very high current through a gas, a bank of capacitors of total capacitance $50\ \mu\text{F}$ is charged to $30\ \text{kV}$. If the bank of capacitors could be discharged completely in $5.0\ \text{ms}$ what would be the mean power delivered?

- A 22 kW
- B 110 kW
- C 4.5 MW
- D 9.0 MW

(Total 1 mark)

Q3. A $400\ \mu\text{F}$ capacitor is charged so that the voltage across its plates rises at a constant rate from $0\ \text{V}$ to $4.0\ \text{V}$ in $20\ \text{s}$. What current is being used to charge the capacitor?

- A $5\ \mu\text{A}$
- B $20\ \mu\text{A}$
- C $40\ \mu\text{A}$
- D $80\ \mu\text{A}$

(Total 1 mark)

Q4. A $1000\ \mu\text{F}$ capacitor and a $10\ \mu\text{F}$ capacitor are charged so that the potential difference across each of them is the same. The charge stored in the $1000\ \mu\text{F}$ capacitor is Q_1 and the charge stored in the $10\ \mu\text{F}$ capacitor is Q_2 .

What is the ratio $\frac{Q_1}{Q_2}$?

- A 100
- B 10
- C 1
- D $\frac{1}{100}$

(Total 1 mark)

Q5. A $1.0 \mu\text{F}$ capacitor is charged by means of a **constant** current of $10 \mu\text{A}$ for 20 s . What is the energy finally stored in the capacitor?

A $4.0 \times 10^{-4} \text{ J}$


B $2.0 \times 10^{-3} \text{ J}$

C $2.0 \times 10^{-2} \text{ J}$



D $4.0 \times 10^{-2} \text{ J}$

(Total 1 mark)

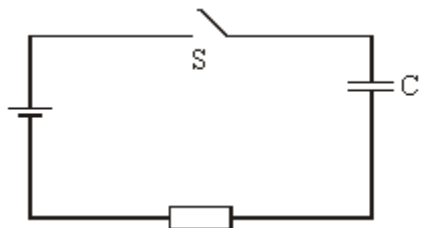Q6. In the circuit shown, the capacitor C is charged to a potential difference V when the switch S is closed.



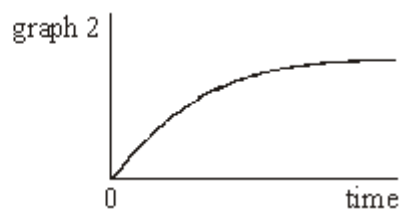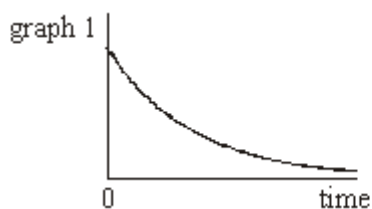
Which line, **A** to **D**, in the table gives a correct pair of graphs showing how the charge and current change with time after S is closed?



	charge	current
A	graph 1	graph 1
B	graph 1	graph 2
C	graph 2	graph 2
D	graph 2	graph 1

(Total 1 mark)

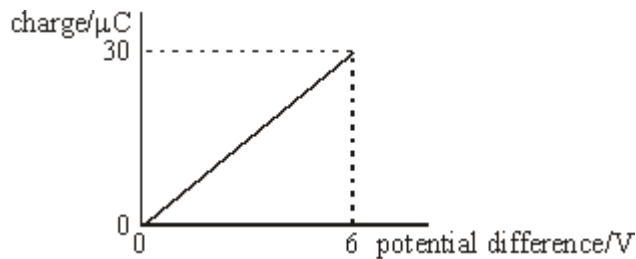Q7. The graph shows how the charge stored by a capacitor varies with the potential difference across it as it is charged from a 6 V battery.



Which one of the following statements is **not** correct?

- A** The capacitance of the capacitor is $5.0 \mu\text{F}$.
- B** When the potential difference is 2 V the charge stored is $10 \mu\text{C}$.
- C** When the potential difference is 2 V the energy stored is $10 \mu\text{J}$.
- D** When the potential difference is 6 V the energy stored is $180 \mu\text{J}$.

(Total 1 mark)

Q8. A capacitor of capacitance C discharges through a resistor of resistance R . Which one of the following statements is **not** true?

- A** The time constant will increase if R is increased.
- B** The time constant will decrease if C increased.
- C** After charging to the same voltage, the initial discharge current will increase if R is decreased.
- D** After charging to the same voltage, the initial discharge current will be unaffected if C is increased.


(Total 1 mark)

Q9. A 10 mF capacitor is charged to 10 V and then discharged completely through a small motor. During this process, the motor lifts a weight of mass 0.10 kg. If 10% of the energy stored in the capacitor is used to lift the weight, through what approximate height will the weight be lifted?

- A 0.05 m
- B 0.10 m
- C 0.50 m
- D 1.00 m

(Total 1 mark)

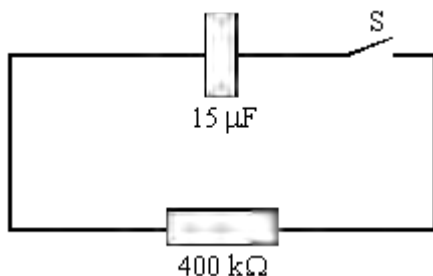Q10. A capacitor of capacitance $15 \mu\text{F}$ is fully charged and the potential difference across its plates is 8.0 V. It is then connected into the circuit as shown.



The switch S is closed at time $t = 0$. Which one of the following statements is correct?

- A The time constant of the circuit is 6.0 ms.
- B The initial charge on the capacitor is $12 \mu\text{C}$.
- C After a time equal to twice the time constant, the charge remaining on the capacitor is $Q_0 e^2$, where Q_0 is the charge at time $t = 0$.
- D After a time equal to the time constant, the potential difference across the capacitor is 2.9 V.


(Total 1 mark)

Q11. A $1\ \mu\text{F}$ capacitor is charged using a constant current of $10\ \mu\text{A}$ for $20\ \text{s}$. What is the energy finally stored by the capacitor?

- A $2 \times 10^{-3}\ \text{J}$
- B $2 \times 10^{-2}\ \text{J}$
- C $4 \times 10^{-2}\ \text{J}$
- D $4 \times 10^{-1}\ \text{J}$

(Total 1 mark)

Q12.

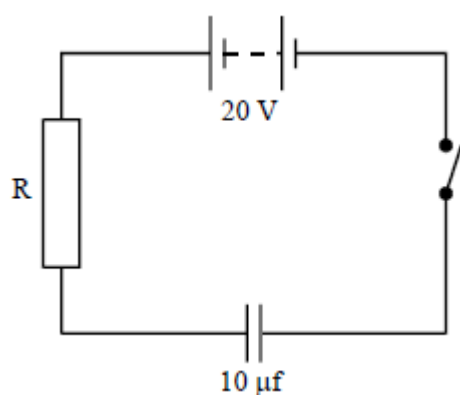

A capacitor of capacitance $10\ \mu\text{F}$ is fully charged through a resistor R to a p.d. of $20\ \text{V}$ using the circuit shown. Which one of the following statements is **incorrect**?

- A The p.d. across the capacitor is $20\ \text{V}$.
- B The p.d. across the resistor is $0\ \text{V}$.
- C The energy stored by the capacitor is $2\ \text{mJ}$.
- D The total energy taken from the battery during the charging process is $2\ \text{mJ}$.

(Total 1 mark)

Q13. A capacitor of capacitance C stores an amount of energy E when the p.d. across it is V . Which line, **A** to **D**, gives the correct stored energy and p.d. when the charge is increased by 50%?

	energy	p.d.
A	$1.5E$	$1.5V$
B	$2.25E$	$1.5V$
C	$1.5E$	$2.25V$
D	$2.25E$	$2.25V$

(Total 1 mark)

Q14. In experiments to pass a very high current through a gas, a bank of capacitors of total capacitance $50 \mu\text{F}$ is charged to 30 kV . If the bank of capacitors could be discharged completely in 5.0 ms what would be the mean power delivered?

- A** 9.0 MW
- B** 4.5 MW
- C** 110 kW
- D** 22 kW


(Total 1 mark)

Q15. Which of the following does **not** give a value in seconds?

- A capacitance \times resistance
- B $\frac{1}{\text{frequency}}$
- C half-life
- D $\frac{\text{power}}{\text{work}}$

(Total 1 mark)

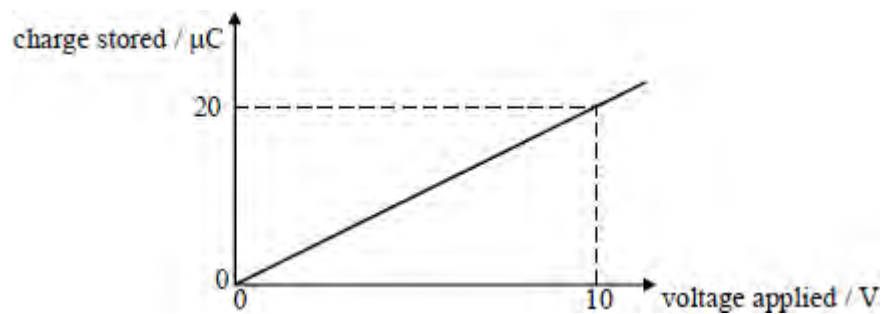Q16. The graph shows the charge stored in a capacitor as the voltage across it is varied.



The energy stored, in μJ , when the potential difference across the capacitor is 5 V, is

- A 25
- B 50
- C 100
- D 200

(Total 1 mark)


Q17. A capacitor is first charged through a resistor and then discharged through the same resistor.

The magnitude of which one of the following quantities varies with time in the same way during both charging and discharging?

- A Energy stored
- B Current
- C Potential difference
- D Charge

(Total 1 mark)

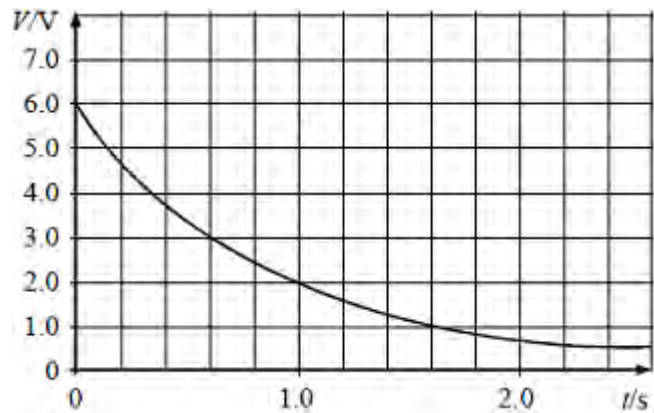Q18. The graph shows the variation of potential difference V with time t across a $470\ \mu\text{F}$ capacitor discharging through a resistor.



The resistance of the resistor is approximately

- A $900\ \Omega$
- B $1300\ \Omega$
- C $1900\ \Omega$
- D $4700\ \Omega$

(Total 1 mark)