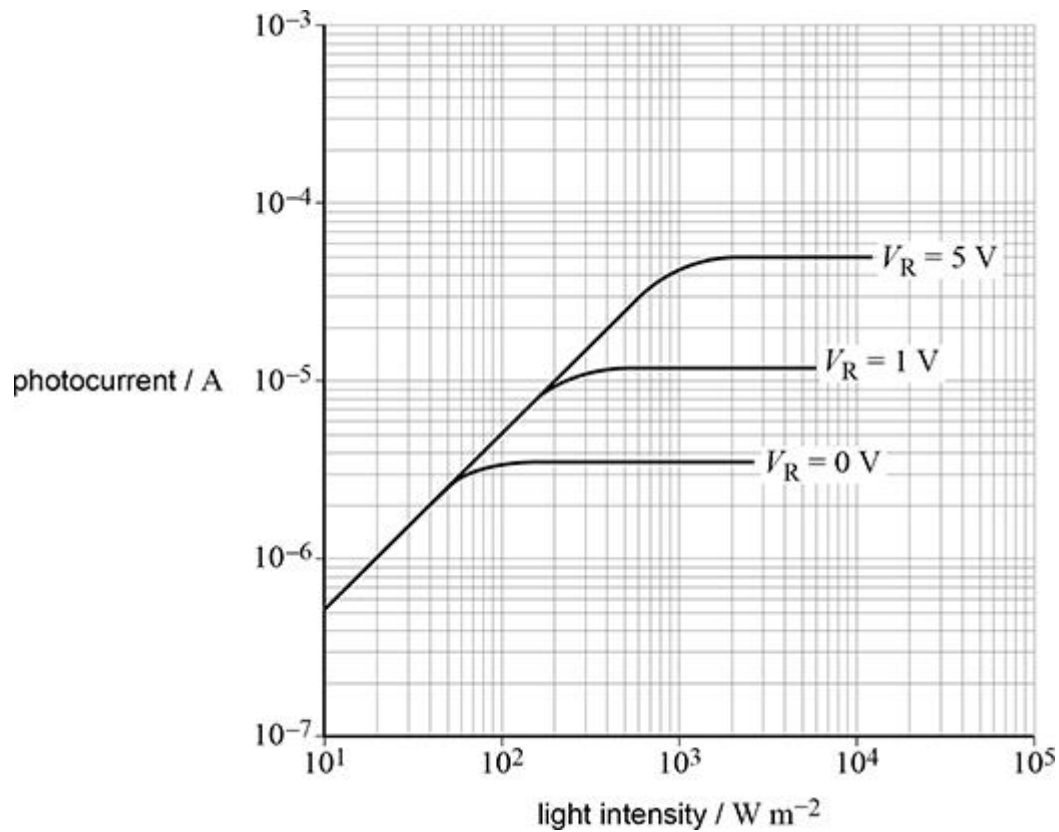


Q1.

- (a) **Figure 1** shows the response of a photodiode for different values of reverse-bias voltage V_R .

Figure 1

The photodiode is used as the input for a light-intensity meter.

The light intensity changes from 100 W m^{-2} to 400 W m^{-2} .

Explain which value of V_R in **Figure 1** should be used for this application.
Go on to deduce the change in photocurrent for this change in light intensity.

change in photocurrent = _____ A

(2)

- (b) Describe how a photodiode is used in a particle detector to detect sub-atomic particles.

(2)

- (c) The particle detector produces an analogue signal that is the input voltage V_{in} to an amplifier circuit.
 V_{in} is amplified by a factor of +10

Draw, on **Figure 2**, a circuit that uses a single operational amplifier to produce an amplification of +10

Use resistors with resistance values in the range 10 k Ω to 1 M Ω in the circuit.

On your diagram you should label:

- the value of the resistors
- the output of the circuit as V_{out} .

Do **not** show the power supplies for the operational amplifier.

Figure 2

V_{in}  — 

0 V  ————— 


(3)

(Total 7 marks)

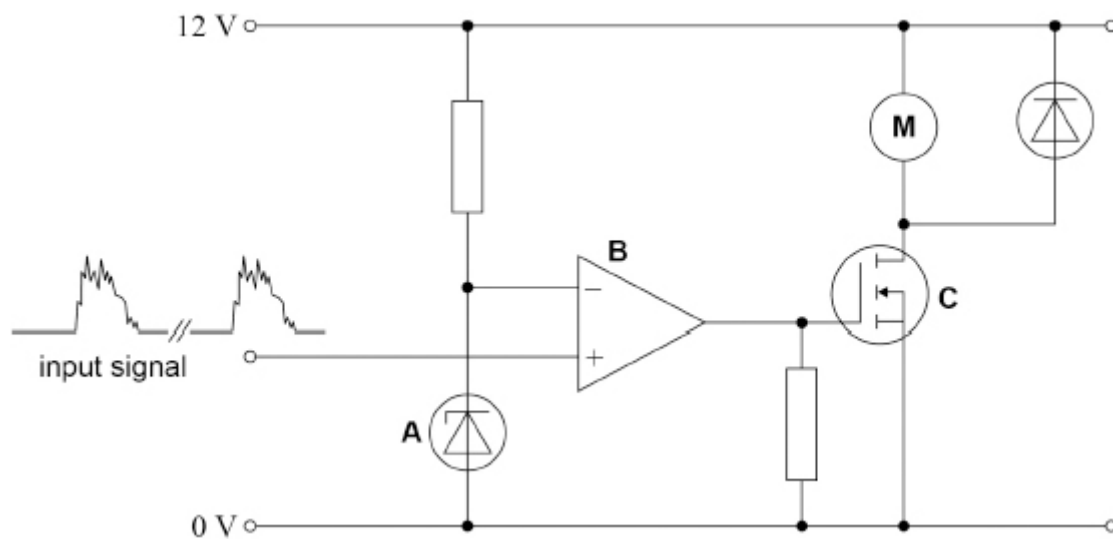Q2.

The figure below shows a circuit that has an input signal which is a noisy square wave.

The circuit is used to remove the noise and switch a motor **M** on and off.



Explain the functions of components **A**, **B** and **C**.

For each of these components you should:

- explain its role in the circuit
- identify the characteristic properties that make the component suitable for this role.

[illegible]

(Total 6 marks)