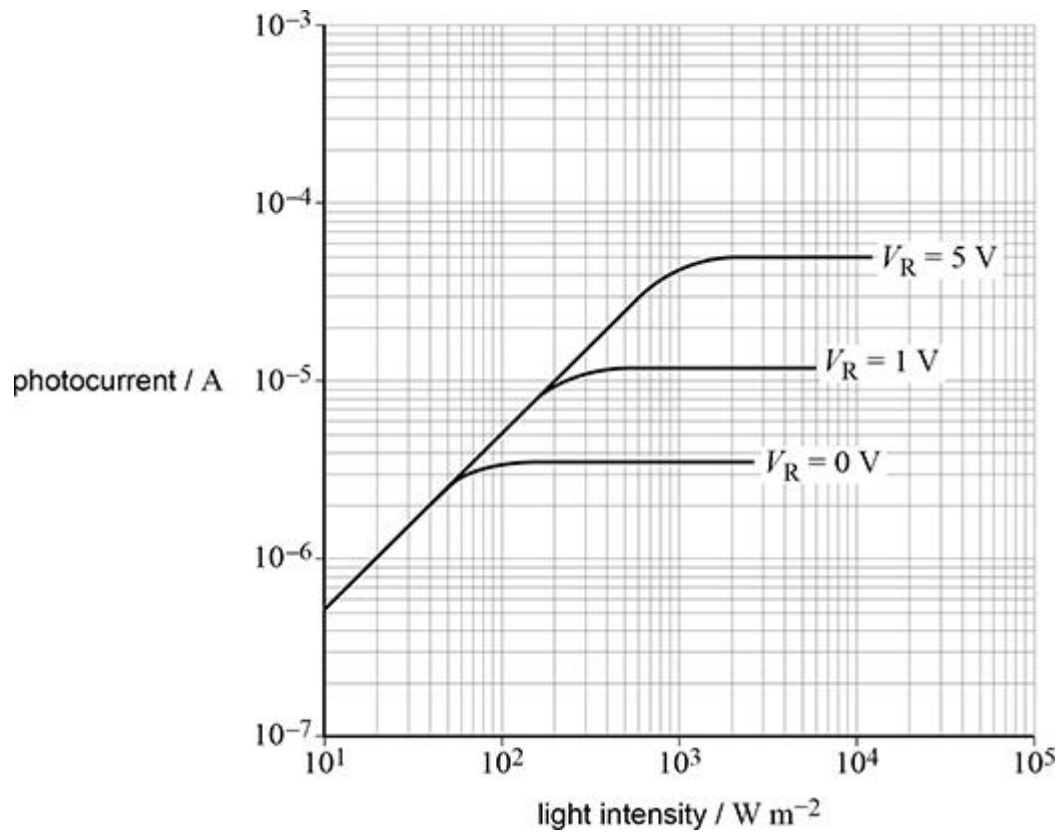


**Q1.**

- (a) **Figure 1** shows the response of a photodiode for different values of reverse-bias voltage  $V_R$ .

**Figure 1**

The photodiode is used as the input for a light-intensity meter.

The light intensity changes from  $100 \text{ W m}^{-2}$  to  $400 \text{ W m}^{-2}$ .

Explain which value of  $V_R$  in **Figure 1** should be used for this application.  
Go on to deduce the change in photocurrent for this change in light intensity.

---



---



---

change in photocurrent = \_\_\_\_\_ A

(2)

- (b) Describe how a photodiode is used in a particle detector to detect sub-atomic particles.

---



---



---



---



---



---

(2)

- (c) The particle detector produces an analogue signal that is the input voltage  $V_{in}$  to an amplifier circuit.  
 $V_{in}$  is amplified by a factor of +10

Draw, on **Figure 2**, a circuit that uses a single operational amplifier to produce an amplification of +10

Use resistors with resistance values in the range 10 k $\Omega$  to 1 M $\Omega$  in the circuit.

On your diagram you should label:

- the value of the resistors
- the output of the circuit as  $V_{out}$ .

Do **not** show the power supplies for the operational amplifier.

**Figure 2**

$V_{in}$   \_\_\_\_\_ 


0 V  \_\_\_\_\_ 

(3)

(Total 7 marks)

**Q2.**

**Figure 1** shows a strain gauge that consists of a folded metal wire glued to a piece of insulating material.

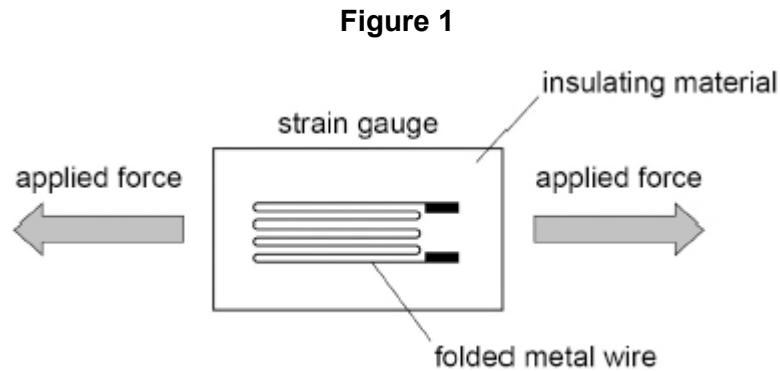

The resistance of the metal wire:

- increases when the gauge is stretched by forces applied as shown
- changes when there is a change in temperature.


(a) **Figure 2** shows a circuit that contains two identical strain gauges **A** and **B**. The resistance of each strain gauge is  $120.00\ \Omega$  when the strain is zero.

$R_1$  is a  $560\ \Omega$  fixed resistor.

$R_2$  is a  $100\ \Omega$  variable resistor.

$R_3$  is a  $510\ \Omega$  fixed resistor.

Assume that the voltmeter is ideal.

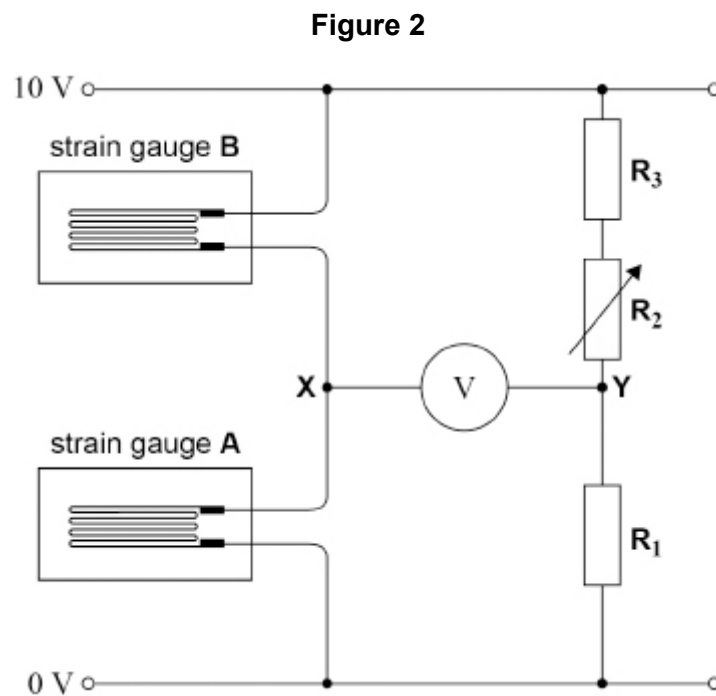

The circuit is used to measure changes in strain in a metal beam.

**A** is glued firmly to the metal beam.

**B** is placed on the beam near **A** but is not glued to the beam.

Initially, with the gauges under zero strain,  $R_2$  is adjusted to produce 0 V on the voltmeter.

When the beam bends, **A** stretches and **B** remains unstretched.

The resistance of **A** increases to  $120.06\ \Omega$ .

Calculate, in mV, the new reading on the voltmeter.

reading on the voltmeter = \_\_\_\_\_ mV

(3)

- (b) Explain the advantage of using strain gauge **B** rather than a  $120.00\ \Omega$  resistor in the circuit.

---

---

---

---

---

---

(2)

- (c) The voltages at **X** and **Y** in **Figure 2** are now used as inputs to an operational amplifier.  
The operational amplifier is configured as a difference amplifier with a gain of +5

Complete **Figure 3** to show the difference amplifier circuit.  
Any resistors used must be labelled with their values. These values must be in the range  $10\text{ k}\Omega$ – $10\text{ M}\Omega$ .  
Do not show the supply rails.

**Figure 3**

**Y** ○

**X** ○

0 V ○ ————— ○

(3)

(Total 8 marks)


**Q3.**

(a) A particular operational amplifier has the following properties:

- open-loop gain =  $1 \times 10^5$
- break frequency (cutoff frequency) = 10 Hz
- gain  $\times$  bandwidth = 1 MHz.

Draw, on **Figure 1**, the variation of gain with frequency for this operational amplifier in open-loop mode.


**Figure 1**

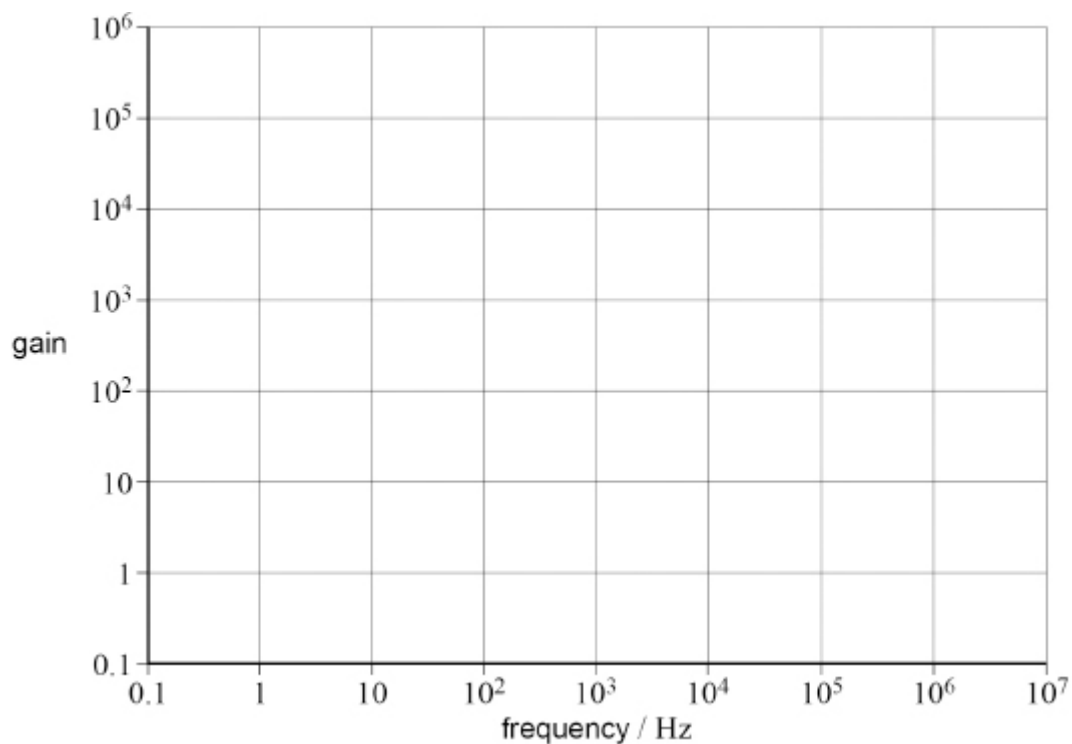

(2)

(b) **Figure 2** shows the operational amplifier being used in an inverting amplifier circuit.

**Figure 2**

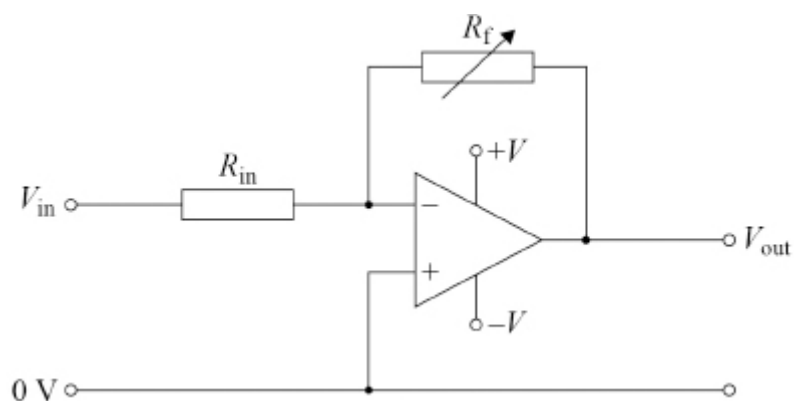

Annotate **Figure 2** with:

- an **X** to indicate a point that acts as a virtual earth
- arrows to show the direction of current  $I$  in both resistors when the

input voltage  $V_{\text{in}}$  is negative.

(2)

- (c) The value of  $R_{\text{f}}$  in the feedback loop in **Figure 2** is increased.

State and explain the effect of this change on the bandwidth of the inverting amplifier.

---

---

---

---

---

---


(2)

(Total 6 marks)

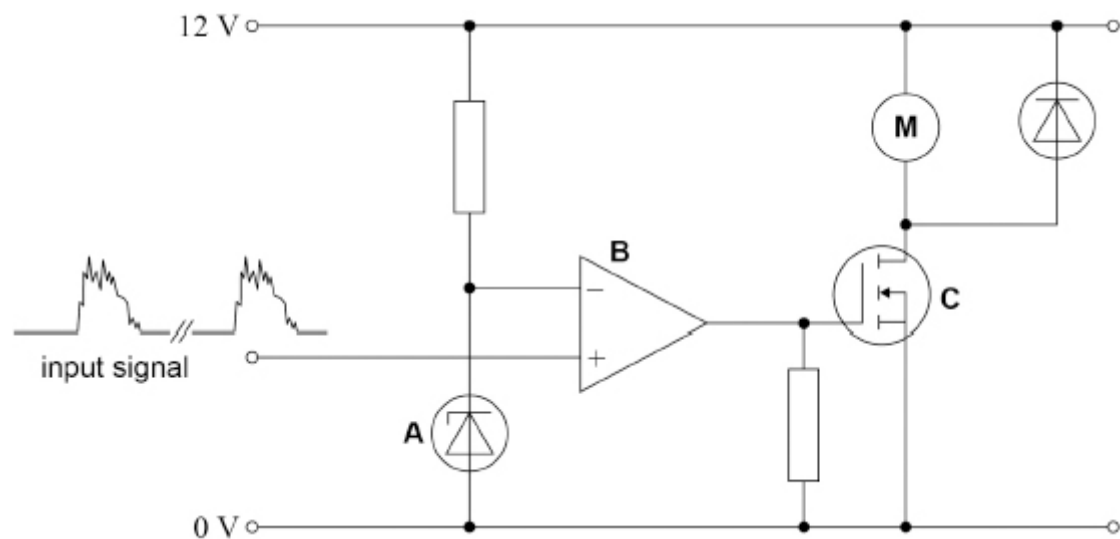**Q4.**

The figure below shows a circuit that has an input signal which is a noisy square wave.

The circuit is used to remove the noise and switch a motor **M** on and off.



Explain the functions of components **A**, **B** and **C**.

For each of these components you should:

- explain its role in the circuit
- identify the characteristic properties that make the component suitable for this role.


[illegible]

**(Total 6 marks)**



**Q5.**

**Figure 1** shows a circuit containing an ideal operational amplifier. A signal  $V_{in}$  is applied to one of the amplifier inputs.

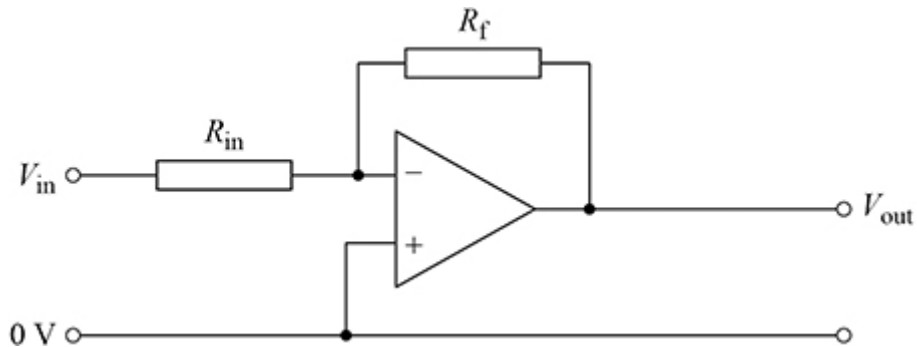**Figure 1**

- (a) Draw an **X** on the circuit in **Figure 1** to indicate a virtual earth point.

**(1)**

- (b) Show that the closed loop voltage gain for the amplifier in **Figure 1** is given by:

$$\frac{R_f}{R_{in}} = - \frac{V_{out}}{V_{in}}$$

State any assumptions made in your answer.


assumptions \_\_\_\_\_

\_\_\_\_\_


**(2)**

- (c) **Figure 2A** shows the input signal  $V_{in}$  that is applied to the circuit in **Figure 1**.

**Figure 2A**

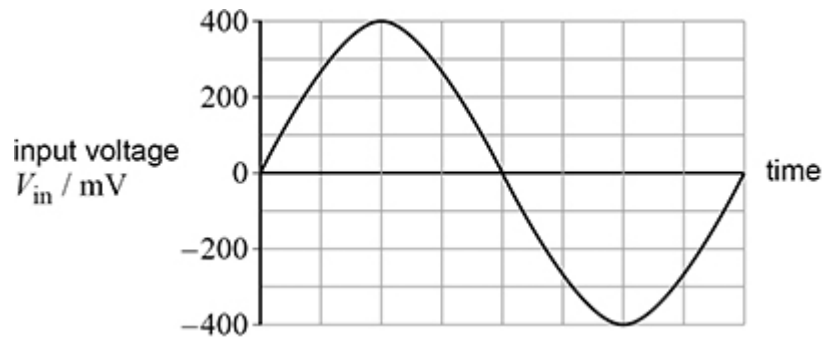

**Figure 2B**

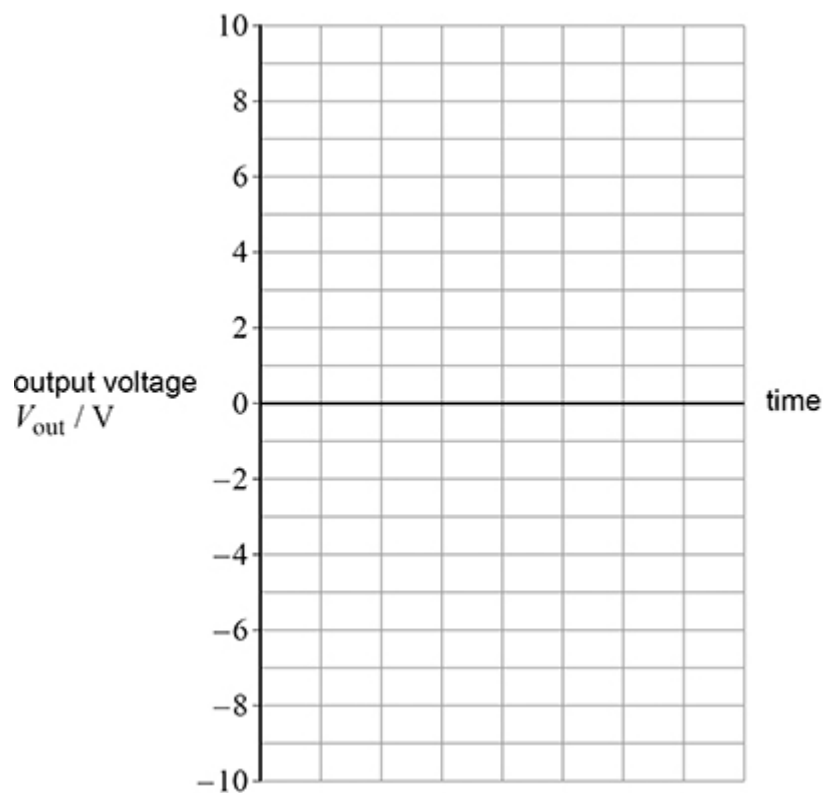

The circuit in **Figure 1** has a closed loop gain of  $-20$  and has power-supply voltages of  $\pm 6.0$  V.

Draw, on **Figure 2B**, the output waveform from the operational amplifier circuit over the same time interval as that shown on **Figure 2A**.

(2)

- (d) A student converts the circuit in **Figure 1** into one that will add two input signals  $V_1$  and  $V_2$ .


The new circuit produces an output voltage  $V_{\text{out}}$  so that:

$$V_{\text{out}} = - (1.5V_1 + 0.75V_2)$$

The circuit is to include a  $27 \text{ k}\Omega$  feedback resistor.

Complete **Figure 3** to show the circuit that the student constructs.  
Annotate your circuit with the values of any additional components.

**Figure 3**

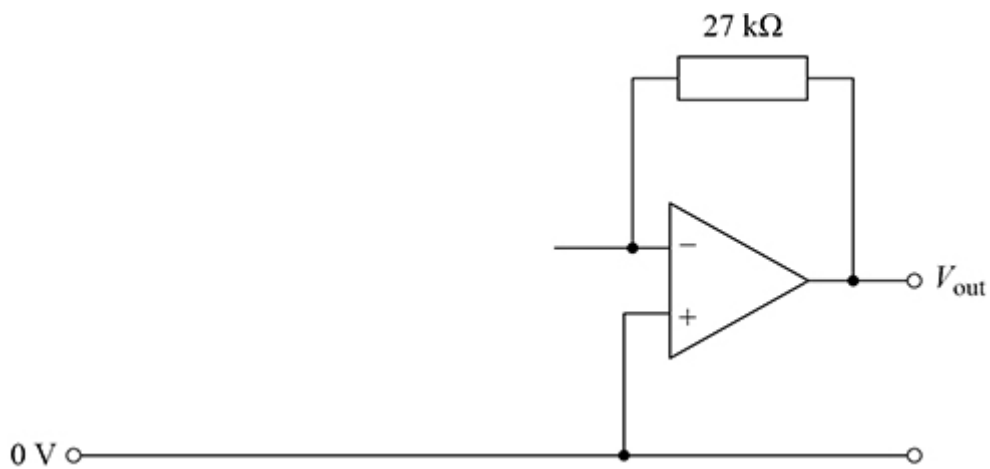

(3)

(Total 8 marks)