

Mark schemes

Q1.

- (a) When B = logic 0, (point D is logic 1.) (Result: closes the lower AND gate and opens the upper AND gate.) Only the 1024 Hz signal is allowed to (pass through to the OR gate) output Q. ✓

1st mark:

- *explanation for either logic 1 or logic 0 input*
- *reference as to which frequency passes through OR gate.*

When B = logic 1, (point D is logic 0). (Result: closes the upper AND gate and opens the lower AND gate.) Only the 512 Hz signal is allowed to (pass through to the OR gate) output Q. ✓

2nd mark:

reference to other half of the cycle and output frequency.

1 Max if there is no reference to the action of at least 1 gate.


2

- (b) $Q = (A \cdot \bar{B}) + (B \cdot C)$ ✓ ✓

1st mark for: contents of either bracket

2nd mark for: contents of other bracket and the '+'

2

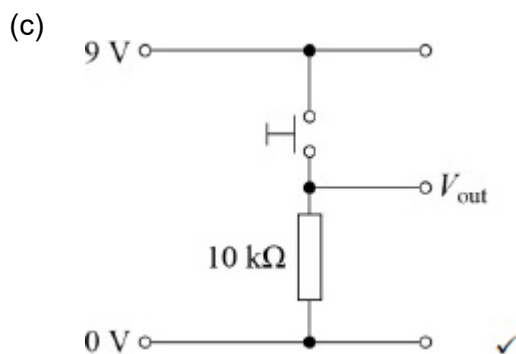

Mark awarded if all the following are present:

- *resistor and push-to-make switch are in correct position*
- *output point in correct position and labelled.*

1

- (d) Q_9 ✓

$$2^{(n+1)} = 1024$$

Condone $n = 9$

1

- (e) Option 1 requires a total of 6 ICs whereas Option 2 requires a total of 3 ICs ✓

Advantage: One from: ✓

- smaller circuit to fit toys
- less power consumed / extended battery life
- less complex circuits / lower production costs

1st mark: identifies the main advantage (must be numerical)

2nd mark: gives one advantage from the list /or other valid explanation

*Allow one mark for answers that only consider number of **logic gates** in the two systems leading to the correct conclusion.*

2

[8]

Q2.

- (a) 1 from ✓

- $160 \times 7 = 1120$ bits
- 140 bytes seen
- their number of bits $\div (64 \times 10^3)$
- their number of bytes $\div (8 \times 10^3)$

1st mark for correct bits or bytes conversion in message or time calculation

$$= 17.5 \times 10^{-3} \text{ s } \checkmark$$

2nd mark for answer

Allow 2 sf answer.

2

- (b) Internal noise:
thermal agitation of electrons / charge carriers in a conductor

Accept one example for the mark

OR

External noise:
idea of electromagnetic interference (EMI) eg cross-talk / power switching etc. ✓

1

(c) Effect of electrical noise on the signal:



- degrades the quality of the signal ✓

Effect of electrical noise on the communication system:

- reduces the efficiency of the transmission e.g. increased latency of the system ✓

2

(d)

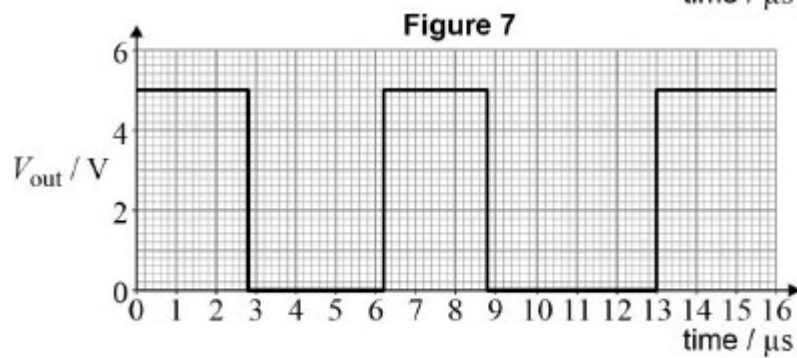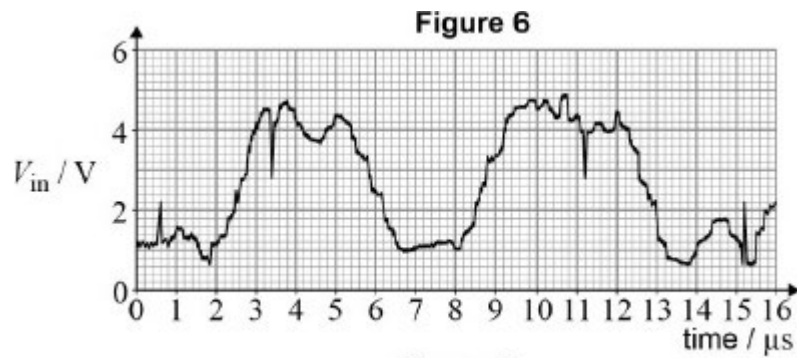

1st mark - 0 to 5 V sq wave with 3 marks and two spaces ✓✓


2nd mark - any three correct transitions.

2

[7]

Q3.

(a)

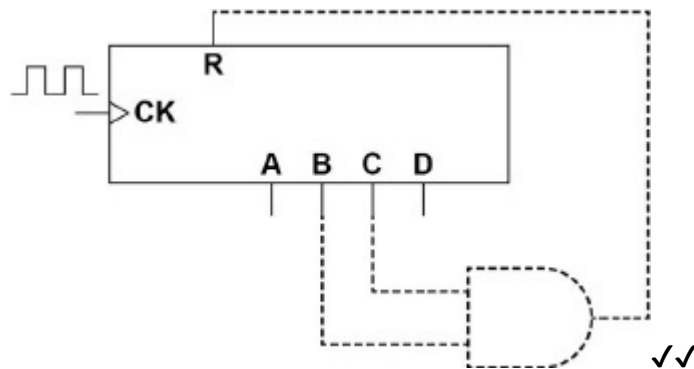

1 mark for use of the correct counter outputs
1 mark for the correct logic gate connected to reset
R

2

(b) input **C**
segment **b** ✓

Both input and segment needed for the mark
Do not allow **B** for **b**


1

(c) **f** ✓

Allow **F** for **f**

1

(d)

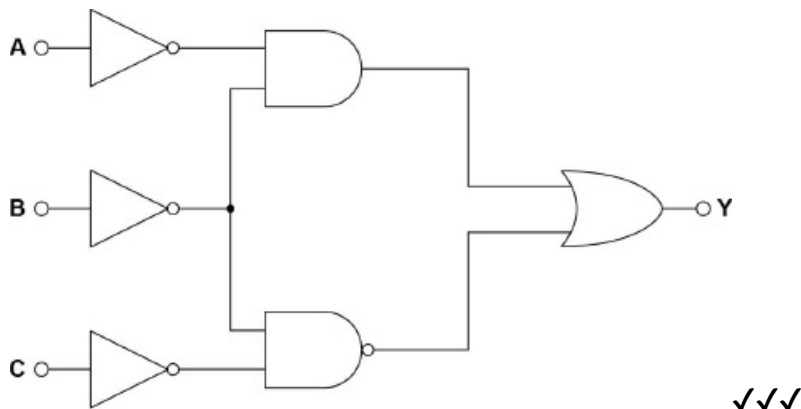

MP1: all inputs inverted (accept a shorted-out
NAND or NOR gates for the inverters)
MP2: for correct use of AND and NAND
Condone a NOT following an AND for the NAND
gate.
MP3: for final gate being OR

3

[7]

Q4.(a) \bar{A} ✓ $\cdot B$ ✓ $\bar{A} \cdot B$ ✓Do not allow $\overline{A+B}$

2

(b) EOR ✓

Accept: XOR ; EXOR; Exclusive OR gate

1

(c)

B	A	C	D	E	X	Y	Z
0	0	1	1	0	0	1	0
0	1	0	1	1	0	0	1
1	0	1	0	1	1	0	0
1	1	0	0	0	0	1	0

X and Z correct ✓

Y correct ✓

2

(d) NOR gate ✓

Also accept any of:

EXNOR; ENOR; XNOR; Exclusive NOR gate

1

(e)

X	Y	Z	
A = B	A < B	A > B	<input type="checkbox"/>
A < B	A = B	A > B	<input checked="" type="checkbox"/>
A < B	A > B	A = B	<input type="checkbox"/>
A > B	A = B	A < B	<input type="checkbox"/>

1

[7]

Q5.

- (a)
- When V_c reaches a value of V_u , the output voltage V_{out} drops LOW. ✓
 - The capacitor now discharges through the resistor causing the value of V_c to fall. ✓
 - When V_c reaches a value of V_L , the output voltage V_{out} jumps HIGH. ✓

3

(b) **Mark-to-space ratio**

R_B gets smaller and hence (t_H) is reduced

OR

R_A gets bigger and hence (t_L) is increased ✓

First mark: Either statement or equivalent labelled diagram(s).

Hence mark:space ratio is reduced / smaller ✓

Second mark: Conclusion

$$\text{PRF} = \frac{1}{T} = \frac{1}{(t_H + t_L)} = \frac{1}{0.7C(2R + R_A + R_B)}$$

The total resistance $(2R + R_A + R_B)$ is constant ✓

As a result of a constant resistance in the circuit, PRF does not change ✓

First mark: explanation of how total resistance in the circuit affects the periodic time

Second mark: Conclusion.

4

[7]