

Current & Resistance MS

M1. (a) $R = \frac{\rho l}{A}$ **(1)**

$$= \frac{1.7 \times 10^{-8} \times 1.4}{7.8 \times 10^{-7}} = 0.031 \Omega \text{ **(1)** (0.0305 } \Omega)$$

2

(b) constant volume gives $l_1 A_1 = l_2 A_2$

[or $l_2 = 2l_1$ and $A_2 = A_1/2$] **(1)**

$$R = \frac{\rho 2l}{A/2} = 4R \text{ **(1)**}$$

[or calculation with $l_2 = 2.8$ (m) and $A_2 = 3.9$ (m²) **(1)**]

gives $R = 0.124 \Omega$ **(1)**

2

[4]

M2. (a) superconductivity means a material has zero resistivity/resistance **(1)**

resistivity decreases with temperature **or** idea of cooling **(1)**

becomes superconducting when you reach the critical/certain/
transition temperature **(1)**

3

(b) (i) (use of $R = \rho l/A$)

$$0.075 = \rho \times 1/(2.28 \times 10^{-7}) \text{ **(1)** (must see working or equation)}$$

$$R = 1.7 \times 10^{-8} \text{ **(1)** } \Omega\text{m **(1)**}$$

(ii) **max 3 from**

the resistance decreases (to zero) **(1)**

copper still has resistance **(1)**

but this is in parallel with filaments (which have zero resistance) **(1)**

hence **total** resistance is zero **(1)**

current goes through filaments **(1)**

6

[9]

M3. (a) (i) (use of $R = \rho l/A$)

$$R = 4.0 \times 10^{-3} \times 0.060 \text{ (1)} / (\pi \times 0.012^2) \text{ (1)}$$

$$R = 0.53 \text{ (}\Omega\text{)} \text{ (1)}$$

2 significant figures **(1)**

4

(ii) halving the diameter **will** increase resistance by factor of 4 or increasing the length by a factor of 4 will increase resistance by factor of 4 **(1)**

(hence) resistance will be 16 times greater **(1)**

2

- (b) the mark scheme for this part of the question includes an overall assessment for the Quality of Written Communication

circuit must include:

voltmeter and ammeter connected correctly **(1)**

power supply with means of varying current **(1)**

2

QWC	descriptor	mark range
good-excellent	<p>(i) Uses accurately appropriate grammar, spelling, punctuation and legibility.</p> <p>(ii) Uses the most appropriate form and style of writing to give an explanation or to present an argument in a well structured piece of extended writing. [may include bullet points and/or formulae or equations]</p> <p>An excellent candidate will have a working circuit diagram with correct description of measurements (including range of results) and processing. An excellent candidate uses a range of results and finds a mean value or uses a graphical method, eg I-V characteristics. They also mention precision eg use of vernier callipers.</p>	5-6
modest-adequate	<p>(i) Only a few errors.</p> <p>(ii) Some structure to answer, style acceptable, arguments or explanations partially supported by evidence or examples.</p> <p>An adequate candidate will have a working circuit and a description with only a few errors, eg do not consider precision. They have not taken a range of results and fail to realise that the diameter needs to be measured in several places.</p>	3-4
poor-limited	<p>(i) Several significant errors.</p> <p>(ii) Answer lacking structure, arguments not supported by evidence and contains limited information.</p> <p>Several significant errors, eg important measurement missed, incorrect circuit, no awareness of how to calculate resistivity.</p>	1-2
incorrect, inappropriate or no response		0

The explanation expected in a good answer should include a coherent account of the procedure and include most of the following points.

- length with a ruler
- thickness/diameter with vernier callipers/micrometer
- measure voltage
- measure current
- calculate resistance
- use of graph, eg I - V or resistance against length
- use of diameter to calculate cross-sectional area
- mention of precision, eg vernier callipers or full scale readings for V and I
- flat metal electrodes at each end to improve connection

6

[14]

M4. (a) $R = \frac{\rho l}{A}$ (1)

ρ is resistivity, l is the length of the wire, A is the cross-sectional area (1)

2

(b) (i) $P = \frac{V^2}{R}$ (1)

$$R = \frac{230^2}{500} = 106(\Omega)(1) \quad (105.8 \Omega)$$

$$l = \left(\frac{RA}{\rho} \right) = \frac{105.8 \times 8.0 \times 10^{-8}}{1.1 \times 10^{-6}} = 7.7 \text{ m (1)} \quad (7.69 \text{ m})$$

(allow C.E. for incorrect value of R)

- (ii) in series, voltage across each < 230 V or pd shared **(1)**
 \therefore power ($= V^2/R$) is less than 500 W in each **(1)**
 in parallel, voltage across each = 230 V **(1)**
 \therefore correct rating, \therefore conclusion **(1)**
 [or, in series, high resistance or combined resistance **(1)**
 \therefore low current **(1)**
 in parallel, resistance is lower, \therefore higher current **(1)**
 more power, justified **(1)**]

max 6

[8]

M5. (a) $\rho = \frac{RA}{l}$ **(1)**

R = resistance (of wire), A = **cross-sectional** area,
 l = length (of wire) **(1)**

2

(b) (i) $R = \frac{\rho l}{A} = \frac{4.0 \times 10^{-8} \times 30 \times 10^{-3}}{8 \times 10^{-3} \times 2 \times 10^{-6}}$ **(1)**
 $= 75 \Omega$ **(1)**

- (ii) length has decreased causing resistance to decrease **(1)**
 area increased, causing resistance to decrease **(1)**
 each changed by factor of 1.5×10^3 **(1)**

4
 QWC 1

[6]

M6. (i) $I = \frac{\Delta Q}{\Delta t}$ [or $Q = It$] **(1)**

$Q = 40 \times 10^{-3} \times 3 \times 60 = 7.2 \text{ C}$ **(1)**

(ii) number of electrons = $\frac{7.2}{1.6 \times 10^{-19}}$ = 4.5×10^{19} **(1)**

(allow C.E. for value of Q from (i))

(iii) $V = \frac{W}{Q}$ (1)

$$= \frac{8.6}{7.2} = 1.2 \text{ V}$$

(allow C.E. for value of Q from (i))

(iv) (use of $V = IR$ gives) $R = \frac{1.2}{40 \times 10^{-3}} = 30 \Omega$ (1)

(allow C.E. for value of V from (iii))

[6]

M7. (a) $I = \frac{\Delta Q}{\Delta t}$ (or $I = \frac{Q}{t}$) (1)

$$\Delta Q = 0.25 \times 6 \times 60 = 90 \text{ C (1)}$$

2

(b) (i) $V = \frac{W}{Q}$ (1) [or $E = VI$]

$$= \frac{9.0 \times 10^4}{0.25 \times 20 \times 60 \times 60} = 5.0 \text{ V (1)}$$

(ii) (use of $P = \frac{W}{t}$ gives) $P = \frac{9.0 \times 10^4}{20 \times 60 \times 60} = 1.2(5) \text{ W (1)}$


[or $P = IV$ gives $P = 0.25 \times 5 = 1.2(5) \text{ W}$]

(allow C.E. in alternative method for value of V from (i))

3

[5]

M8. (a) (i)

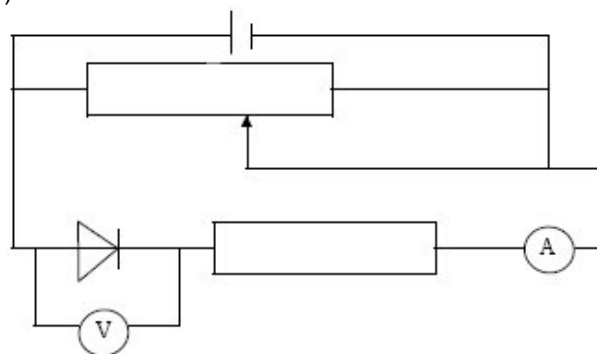

suitable variable input (variable power supply or variable resistor) **(1)**

protective resistor **and** diode **forward** biased **(1)**

correct current **and** pd measuring devices **(1)**

3

(ii) the mark scheme for this part of the question includes an overall assessment for the Quality of Written Communication

QWC	descriptor	mark range
good-excellent	Uses accurately appropriate grammar, spelling, punctuation and legibility. Uses the most appropriate form and style of writing to give an explanation or to present an argument in a well structured piece of extended writing. [May include bullet points and/or formulae or equations]. Answer refers to at least 5 of the relevant points listed below.	5-6
modest-adequate	Only a few errors. Some structure to answer, style acceptable, arguments or explanations partially supported by evidence or examples. Answer refers to at least 3 of the relevant points listed below.	3-4
poor-limited	Several significant errors. Answer lacking structure, arguments not supported by evidence and contains limited information. Answer refers to no more than 2 of the relevant points.	1-2
incorrect, inappropriate or no response	No answer at all or answer refers to unrelated, incorrect or inappropriate physics.	0

The explanation expected in a competent answer should include a coherent selection of the following physics ideas.

connect circuit up **(1)**

measure current (I) and pd/voltage (V) **(1)**

vary resistance/voltage **(1)**

obtain a range of results **(1)**

reverse connections to power supply (and repeat) **(1)**

plot a graph (of pd against current) **(1)**

mention of significance of 0.6V **or** disconnect between readings **or** change range on meters when doing reverse bias **(1)**

(b) (i) (use of $I = V/R$)

$$I = 12/8 \text{ (1)} = 1.5\text{A (1)}$$

(ii) $I = (12 - 0.65 \text{ (1)})/4 = 2.8 \text{ A (1)}$ sig figs **(1)**

5

[14]

M9. (a) reverse mode: current zero or just negative at 50 -500 V **(1)**
sharp downward curve **(1)**

forward mode: current zero or just positive up to $\approx 0.7 \text{ V (1)}$
rapid increase of for small increase in V **(1)**

4

(b) at low V , I increases proportionally (or Ohm's law obeyed) **(1)**
(as V increases) greater I heats filament/wire
(or temp of filament/wire increases) **(1)**
resistance increases **(1)**
rate of increase of I with V decreases [or ref. to gradient = $1/R$] **(1)**
reference to same form of the curve in negative quadrant **(1)**

4

[8]

- M10.** (a) (i) battery, milliammeter, and wire in series **(1)** **(1)**
 voltmeter across the wire **(1)**
 variable resistor/potential divider in series **(1)**

- (ii) alter variable resistor **(1)**
 to obtain a series of values of I and V **(1)**

QWC 1

- (iii) plot a graph of V against I **(1)**
 gradient = R **(1)**

QWC 1

[or calculate $R = V/I$ for each reading and take mean]

8

(b) (i) ($P = \frac{V^2}{R}$ gives) $1200 = \frac{230^2}{R}$
 $R = 44.1 \Omega$ **(1)**

(ii) $R = \frac{\rho l}{A}$ **(1)**

$$l = \frac{44.1 \times 9.4 \times 10^{-8}}{1.1 \times 10^{-6}} \quad \mathbf{(1)}$$

$$= 3.8 \text{ m} \quad \mathbf{(1)}$$

(allow C.E. for value of R in (i))

5

[13]

M11. (a) $R = \frac{\rho l}{A}$ **(1)**

$$= \frac{1.7 \times 10^{-8} \times 1.4}{7.8 \times 10^{-7}} = 0.031 \Omega \quad \mathbf{(1)} \quad (0.0305 \Omega)$$

2

(b) constant volume gives $l_1 A_1 = l_2 A_2$

[or $l_2 = 2l_1$ and $A_2 = A_1/2$] **(1)**

$$R = \frac{\rho 2l}{A/2} = 4R \text{ (1)}$$

[or calculation with $l_2 = 2.8$ (m) and $A_2 = 3.9$ (m²) **(1)**]

gives $R = 0.124 \Omega$ **(1)**

2

[4]