


Potential Dividers, EMF and Internal Resistance - Mark Scheme

Q1.

Question Number	Answer	Mark
a	Energy (supplied) to/per unit charge Or Work done (supplied) to/per unit charge Or The work done moving unit charge around the whole circuit	(1)
		(1)
bi	Use of sum of e.m.f. = sum of p.d. Or see $\mathcal{E} = V + Ir$ with correct substitutions $r = 1.9 \times 10^{-2} \Omega$ <u>Example of calculation</u> $\mathcal{E} = V + Ir$, $12.0 \text{ V} = 11.81 \text{ V} + (9.83 \text{ A}) r$. so $r = 0.0193 \Omega$	(1) (1)
		(2)
bii	Plot V against I Determine the gradient Gradient is $-r$ OR Plot I against V Determine the gradient Gradient is $-(1/r)$ OR Plot $(\mathcal{E} - V)$ against I Determine the gradient Gradient is r	(1) (1) (1) (1) (1) (1) (1) (1) (1)
		(3)

Q2.

c	<p>Calculates circuit current using $I = \mathcal{E} / \text{Total } R$ Or Calculates p.d. across fixed resistor using potential divider equation (1)</p> <p>Use of a power equation (to calculate Power dissipated in fixed resistor) (1)</p> <p>Divides final power by initial power Or Divides difference in power by initial power Or Calculates 70% of initial power (1)</p> <p>Calculated value for final power/initial power is greater than 70% of initial power so student incorrect Or Calculated value for difference between initial and final power is less than 30% so student incorrect Or Calculated value for 70% of initial power is less than the final power so student incorrect (1)</p> <p>(Candidates who use incorrect values of I, V or R in either power calculation for MP2 cannot be awarded MP3 or MP4)</p> <p><u>Example of calculation</u> Initially $I = \mathcal{E} / \text{Total } R = 9.0 \text{ V} / (5.0 + 0.10 \Omega) = 1.76 \text{ A}$ Power of external resistor = $I^2 R = (1.76 \text{ A})^2 (5.0 \Omega) = 15.5 \text{ W}$ When $r = 0.50 \Omega$, $I = \mathcal{E} / \text{Total } R = 9.0 \text{ V} / (5.0 + 0.50 \Omega) = 1.64 \text{ A}$ Power of external resistor = $I^2 R = (1.64 \text{ A})^2 (5.0 \Omega) = 13.4 \text{ W}$ Percentage of original value = $(13.4 \text{ W}) / (15.5 \text{ W}) = 0.86$ (or 86%)</p>	(4)
----------	--	------------

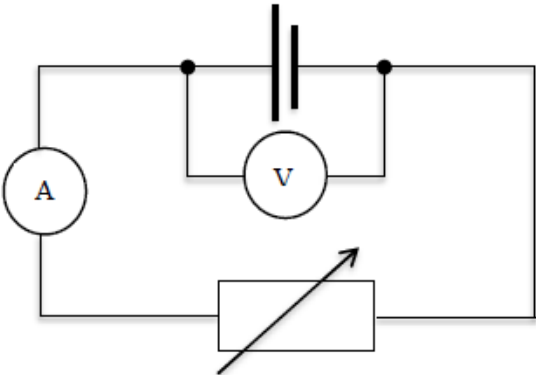Question Number	Answer	Mark
a	<p>Ammeter in series with cell, voltmeter in parallel with cell Variable resistor</p> <div style="text-align: center;">  </div> <p>(Voltmeter can be drawn in parallel with the (variable) resistor for MP1, as long as there are no other components with resistance in the circuit).</p>	<p>(1) (1) 2</p>
b	<p>Line of best fit drawn $\mathcal{E} = 0.28 - 0.29 \text{ V}$ (Magnitude of) gradient calculated using a best fit line $r = 400 - 430 \Omega$</p> <p>(If no best fit line has been drawn, only MP2 and MP4 are available)</p> <p><u>Example of calculation</u> Gradient = $\Delta V / \Delta I = -0.18 \text{ V} / (0.44 \times 10^{-3} \text{ A}) = -409 \Omega$ so $r = 409 \Omega$</p>	<p>(1) (1) (1) (1) 4</p>

c	In series/A there is a greater (combined) resistance than in parallel/B Or Resistance in series/A is $2R$, resistance in parallel/B is $R/2$. (1)	4
	So greater current in parallel/B Or so less current in series/A (1)	
	As \mathcal{E} and r the same Or since $\mathcal{E} = V + Ir$ Or more lost volts in parallel/B (1)	
	Terminal potential difference is greater in series/A (1)	
	OR	
	In series/A there is a greater (combined) resistance than in parallel/B Or Resistance in series/A is $2R$, resistance in parallel/B is $R/2$. (1)	
	as \mathcal{E} and r the same (1)	
$V = \frac{\mathcal{E}R}{R+r}$ (1)	4	
Terminal potential difference is greater in series/A (1)		
Total for question		10

Q3.

Question Number	Answer	Mark
	<p>A is the correct answer as this represents the current in the internal resistance multiplied by the p.d. across the internal resistance.</p> <p>B is not the correct answer as this is the power dissipated by the external resistance C is not the correct answer as this is the power dissipated by the whole circuit. D is not the correct answer as this equation combines the p.d. across the external resistance with the value for the internal resistance – as a result, it does not represent the power of any of the components in the circuit</p>	(1)

Q4.

Question Number	Answer	Mark
	<p>D is the correct answer</p> <p>A is not the correct answer as these are the units of charge B is not the correct answer as these are the units of energy C is not the correct answer as these are the units of force</p>	(1)