

Capacitance - Mark Scheme

Q1.

Question Number	Answer	Mark
(a)	Use of $C=Q/V$ $Q = 1.0 \times 10^{-6} \text{ C}$ <u>Example of calculation</u> $Q = 680 \times 10^{-9} \text{ F} \times 1.5 \text{ V}$ $Q = 1.02 \times 10^{-6} \text{ C}$	(1) (1) 2
(b)	Use of $Q = Q_0 e^{-t/RC}$ converts ms \rightarrow and nF \rightarrow F $Q = 1.3 \times 10^{-9} \text{ C}$ (ecf their Q from (a)) Negligible charge Or fully discharged Or % charge remaining quoted correctly	(1) (1) (1) (1) 4
(c)	$I = fQ$ $I = 5.1 \times 10^{-4} \text{ A}$ ecf their Q from (a) <u>Example of calculation</u> $I = fQ = 500 \text{ Hz} \times 1.02 \times 10^{-6} \text{ C}$ $I = 5.1 \times 10^{-4} \text{ A}$	(1) (1) 2
Total for Question		8

Q2.

Answer	Mark
A	1

Q3.

Question Number	Answer	Mark
	D	1

Q4.

Question Number	Answer	Mark
(a)(i)	<p>Use of $I = I_0 / e$ (I_0 from 2.35 mA to 2.4 mA) to find time constant (1)</p> <p>Or intercept with t axis using initial tangent to find time constant (range 125 s to 135 s)</p> <p>Use of time constant = RC (1)</p> <p>$C = 0.015$ (F) to 0.017 (F) (1)</p> <p>Or</p> <p>Attempts a pair of readings of I and t from graph (1)</p> <p>Use of $I = I_0 e^{-t/RC}$ (1)</p> <p>$C = 0.015$ (F) to 0.017 (F) (1)</p> <p>Or</p> <p>Attempts to obtain 'half-life' from graph (1)</p> <p>Use of $t_{1/2} = RC \ln 2$ (1)</p> <p>$C = 0.015$ (F) to 0.017 (F) (1)</p> <p><u>Example of calculation</u></p> <p>$131 \text{ s} = 8200 \Omega \times C$</p> <p>$C = 1.60 \times 10^{-2} \text{ F}$</p>	3
(a)(ii)	<p>Use of $V = IR$ for initial p.d. using initial current (1)</p> <p>Use of $C = Q/V$ ecf from (i) (1)</p> <p>$Q = 0.32 \text{ C}$ (1)</p> <p><u>Example of calculation</u></p> <p>$V = 0.0024 \text{ A} \times 8200 \Omega = 19.7 \text{ V}$</p> <p>$\Delta Q = 1.60 \times 10^{-2} \text{ F} \times 19.7 \text{ V} = 0.316 \text{ C}$</p>	3
(a)(iii)	<p>Use of suitable equation, e.g. $W = \frac{1}{2} QV$ ecf from (i) and (ii) (1)</p> <p>$W = 3.1 \text{ J}$ (1)</p> <p><u>Example of calculation</u></p> <p>$W = \frac{1}{2} \times 0.316 \text{ C} \times 19.7 \text{ V}$</p> <p>$W = 3.08 \text{ J}$</p>	2
(b)	<p>Use of $V = V_0 e^{-\frac{t}{RC}}$ (1)</p> <p>Correct use of 15% (1)</p> <p>$R = 240 \text{ k}\Omega$ (1)</p> <p><u>Example of calculation</u></p> <p>$0.15 V_0 = V_0 e^{-\frac{t}{RC}}$</p> <p>$\ln 0.15 + \ln V_0 = \ln V_0 - \frac{t}{RC}$</p> <p>$\ln 0.15 = \frac{-210 \text{ s}}{R \times 470 \times 10^{-6} \text{ F}}$</p> <p>$R = 2.36 \times 10^5 \Omega$</p>	3
Total for question		11

Q5.

Question Number	Answer	Mark
(a)	at least 3 horizontal straight lines touching both sides equispaced (by eye) arrow pointing to the right	(1) (1) (1)
		(3)
(b)	Use of $W = \frac{1}{2} CV^2$ Or $Q = CV$ and $E = QV/2$ $W = 1.5 \times 10^{-10} \text{ J}$ <u>Example of calculation</u> $W = \frac{1}{2} \times 12 \times 10^{-12} \text{ F} \times (5.0 \text{ V})^2$ $W = 1.5 \times 10^{-10} \text{ J}$	(1) (1)
		(2)
(c)	Use of $Q = CV$ Use of total charge before = total charge after Or Use of $Q_1 / Q_2 = C_1 / C_2$ (accept use of total capacitance = sum of capacitances) $V = 4.4 \text{ V}$ <u>Example of calculation</u> Total charge = $12 \times 10^{-12} \text{ F} \times 5.0 \text{ V} = 6.0 \times 10^{-11} \text{ C}$ $6.0 \times 10^{-11} \text{ C} = 12 \times 10^{-12} \text{ F} \times V + 1.5 \times 10^{-12} \text{ F} \times V$ $V = 4.4 \text{ V}$	(1) (1) (1)
		(3)
	Total for question 12	8

Q6.

Question Number	Answer	Mark
(a)(i)	<p>The idea that electrons move from one plate to the other plate through the external circuit (1)</p> <p>When fully charged there is no movement of electrons Or As capacitor charges, rate of flow of electrons decreases Or (when fully charged) p.d. across the plates/capacitor is equal (and opposite) to the supply p.d. Or (when fully charged) equal and opposite charge/electrons on each plate (1)</p>	2
(a)(ii)	<p>Use of $W = \frac{1}{2} CV^2$ Or use of $Q=CV$ and $W=\frac{1}{2}QV$ (1)</p> <p>$W = 0.34 \text{ J}$ (1)</p> <p><u>Example of calculation</u></p> <p>$W = 0.5 \times 4700 \times 10^{-6} \text{ F} \times (12 \text{ V})^2 = 0.34 \text{ J}$</p>	2
(b)(i)	<p>Current decreases (over time) (1)</p> <p>Exponentially (1)</p> <p>(a graph of I/t with I decreasing can score MP1. Must be indicated as exponential for MP2)</p>	2
(b)(ii)	<p>Use of $V = V_0 e^{-t/RC}$ Or see $\ln(V/V_0) = -t/RC$ (1)</p> <p>Use $V = 1.2 \text{ (V)}$ and $V_0 = 12 \text{ (V)}$ Or use $\frac{V}{V_0} = 0.1$ (1)</p> <p>$R = 2300 \Omega$ (1)</p> <p><u>Example of calculation</u></p> <p>$V = V_0 e^{-t/RC}$</p> <p>$\ln\left(\frac{V}{V_0}\right) = \frac{-t}{RC}$</p> <p>$\ln(0.1) = \frac{-25 \text{ s}}{R \times 4700 \times 10^{-6} \text{ F}}$</p> <p>$R = \frac{-25 \text{ s}}{\ln 0.1 \times 4700 \times 10^{-6} \text{ F}}$</p> <p>$R = 2300 \Omega$</p>	3
Total for question		9

Q7.

Question Number	Answer	Mark
	B	1

Q8.

Question Number	Answer	Mark
	<p>The only correct answer is B</p> <p><i>A is not correct as this shows both charge and current decreasing, which would be correct for discharging but not charging.</i></p> <p><i>C is not correct as this shows both charge and current increasing, which is not possible in the circuit shown.</i></p> <p><i>D is not correct as this shows current increasing and charge decreasing, which is not possible in the circuit shown</i></p>	(1)

Q9.

Question Number	Answer	Mark
(a)	<p>Use of $T = RC$ (1)</p> <p>$T = 0.3 \text{ s}$ (1)</p> <p><u>Example of calculation</u></p> <p>$T = RC = 1500 \Omega \times 200 \times 10^{-6} \text{ F}$</p> <p>$T = 0.3 \text{ s}$</p>	2
(b)	<p>$B5 = (6V - E4)/1.5 \text{ (k } \Omega)$</p> <p>Or $I = (E-V)/R$</p> <p>Or $I = (6.0 - 3.33)/1.5$ (1)</p> <p>Correct units or comment about mA and kΩ (1)</p> <p>(allow 1 mark for $B5 = C5/(A5-A4)$ and 1 mark for use of exponential equation)</p>	2
(c)(i)	<p>3 points plotted accurately $\pm \frac{1}{2}$ small square (1)</p> <p>Line of best fit drawn (smooth by eye) (1)</p>	2
(c)(ii)	<p>Initial tangent drawn (1)</p> <p>$t = 0.19 \text{ s} - 0.26 \text{ s}$ (1)</p> <p>Or 37% of initial current found (1)</p> <p>$t = 0.24 \text{ s} - 0.26 \text{ s}$ (1)</p> <p>Or half life determined and use of half life = $0.693RC$ (1)</p> <p>$t = 0.23 \text{ s} - 0.26 \text{ s}$ (1)</p> <p>Or uses a pair of points off the graph in exponential equation (1)</p> <p>$t = 0.24 \text{ s} - 0.26 \text{ s}$ (1)</p>	2
(c)(iii)	Reduce the time interval (1)	1
*(d)	<p>Reference to $I = I_0 e^{-t/RC}$ Or $\ln I = \ln I_0 - t/RC$ (1)</p> <p>Or states that there is exponential relationship between I and t (1)</p> <p>Plot $\ln I$ against t Or $\ln (I/I_0)$ against t (1)</p> <p>The time constant = $-1/\text{gradient}$ (1)</p>	3
Total for Question		12

Q10.

Question Number	Answer	Mark
	<p>The only correct answer is A because p.d. for each capacitor = $V/2$ energy for each capacitor = $\frac{1}{2} C (V/2)^2 = C V^2/8$ energy for pair of capacitors = $C V^2/4$</p> <p><i>B is not correct because this is the energy stored for a single capacitor with p.d. = V</i></p> <p><i>C is not correct because this is calculated without applying $V/2$</i></p> <p><i>D is not correct because this is 8 times the correct energy</i></p>	<p>1</p>