

Question Number	Answer	Mark
1(a)	Volt is a Joule coulomb ⁻¹ or $V = J C^{-1}$ or $V = W/Q$ (not rearranged) Amp is a Coulomb sec ⁻¹ or $A = C s^{-1}$ or $I = Q/t$ (not rearranged) Show units/symbols cancelling and equating to a watt. This mark can only be given if <u>both</u> the other marks scored. Method must be clear, do not allow 'let $t = 1$ '.	(1) (1) (1)
1(b)(i)	Use of energy = power × time Energy = 2.9×10^5 J <u>Example of calculation</u> $E = 700 \times 7 \times 60$ $E = 294\,000$ J	(1) (1)
1(b)(ii)	QWC - spelling of technical terms must be correct and the answer must be organised in a logical sequence See internal resistance / r Current will be less Less energy/power is lost in internal resistance OR wasted energy/power is reduced OR reduced lost volts OR it is more efficient	(1) (1) (1)
	Total for question	8

Question Number	Answer	Mark
2	<p>Attempt to use $I = Q / t$</p> <p>use of $e = 1.6 \times 10^{-19}$ 1</p> <p>$I = 2.8 \times 10^6$ A [C s⁻¹] 1</p> <p>[omit e gives answer 1.73×10^{25} scores 1]</p> <p>Example of answer</p> <p>$I = (2.6 \times 10^{26} \times 1.6 \times 10^{-19} \text{ C}) \div 15 \text{ s}$</p> <p>$I = 2.77 \times 10^6$ A</p>	<p>1</p> <p>1</p> <p>1</p>
	Total for question	3

Question Number	Answer	Mark
3	<p>The answer must be clear and organised in a logical sequence</p> <ul style="list-style-type: none"> • Different currents / current divides in parallel circuit(1) • • Same potential difference/voltage across each lamp (1) • • Use of $P = V^2 / R$ OR $P = VI$ if identified $I_A < I_B$ (1) • Leading to high resistance, smaller power (1) • • lamp B will be brighter/ lamp A dimmer (1) • • Each electron loses the same energy (1) • There are more electrons/sec in B (1) • Hence greater total energy loss /sec in B (1) 	
		Max 5
	Total for question	5

Question Number	Answer		Mark
4(a)	Diode / LED (Any type of recognised diode scores the mark but if diode is included in a list of other components the mark cannot be gained.)	(1)	
4(b)	Infinite / infinity / ∞ Or <u>Very high Or very large</u>	(1)	1
4(c)	Use of $R=V/I$ Correct value of R for their current in range 0.40 A to 0.43 A (Any valid pair of values for first mark. Use of tangent or gradient scores no marks) <u>Example of calculation</u> $R= 0.70 \text{ V} / 0.41 \text{ A}$ $R= 1.7 \Omega$	(1) (1)	2
4(d)	Any One from, e.g. To protect components / circuits Rectification Restricts current / flow (of charge) to one direction AC to DC Produce DC supply Power indicator light Light source, e.g. Christmas tree light, torch Regulate voltage (Accept any reasonable practical use for diode or LED)	(1)	1
Total for question			5

Question Number	Answer	Mark
6	<p>Indication that 500 W is 15% of incident radiation / Apply 15% efficiency to incident flux of 210 W m⁻² (i.e. find useful input) (1)</p> <p>Use of radiation flux is power per unit area (1)</p> <p>Answer = 16 m² (1)</p> <p>[2.38 m² is the answer without applying 15% → 1 mark]</p> <p><u>Example of calculation</u> Input power = (500 × 100)/15 = 3300 W Area = input power/radiation flux = 3300 W / 210 W m⁻² = 16 m²</p> <p>OR (15/100) × 210 W m⁻² = 31.5 W m⁻² Area = 500 W / 31.5 W m⁻² = 16 m²</p>	3
Total for question		3

Question Number	Answer	Mark
7(a)	<p>Use of $W = QV$ (1)</p> <p>Energy of electron = 1.6×10^{-14} (J) (1)</p> <p><u>Example of calculation</u> Energy = $1.6 \times 10^{-19} \times 100\,000$ J Energy of electron = 1.6×10^{-14} J</p>	2
7(b)	<p>Use of energy = power × time (1)</p> <p>Energy = 2.88×10^7 (J) (1)</p> <p><u>Example of calculation</u> Energy = $1000 \times 8 \times 3600$ Energy = 2.88×10^7 J</p>	2
7(c)	<p>2</p> <p>eV is very much smaller than Joule (1)</p> <p>kW h is very much bigger than Joule (1)</p> <p>in these units, answers more easily obtained from information available OR answers can be found without conversions (1)</p>	Max 2
Total for question		6

Question Number	Answer	Mark
8(a)	Current (through a conductor) is (directly) proportional to the potential difference/voltage (across it) providing the temperature of conductor remains constant OR external conditions remain constant.	1 1
(b)	Ohmic conductor; fixed resistor horizontal straight line Filament lamp; graph showing increasing resistance (straight line or curve) from a non zero resistance start (conditional on 2nd mark)	1 1 1
(c)	Filament lamps work at high temperatures OR as temp of lamp increases OR as lamp heats up. Resistance of conductor changes OR the ions vibrate more.	1 1
Total for question		7

Question Number	Answer	Mark
9(a)(i)	e.m.f./total resistance (accept $E/(R+r)$)	1
(ii)	= $D4 \cdot A4$ or p.d. = current \times <u>load</u> resistance OR ($B4 \cdot A4$)/($A4+C4$) or p.d. = e.m.f. – (internal resistance \times current) OR $F4/D4$ or p.d.=power/current	1
(iii)	9.2 (W) R and r in series	1
(b)	R and r in series Potential divider r constant so as R increases p.d. also increases OR $V = E - Ir$ E and r constant Identifies that the term Ir decreases OR $E = I(R+r)$ E and r constant As R increases I decreases	1 1 1
(c)(i)	(power) increases and then decreases Maximum power when load equals 0.8Ω	1 1
(ii)	Similar pattern of power increasing to a max and decreasing	1
	Maximum power when load resistance is 1.6Ω	1
	Total for question	10

Question Number	Answer	Mark
10(a)	A coulomb is an Amp sec or As (1) Do not credit current \times time	1
(b)	$I_1 = 10 \text{ mA}$ (1) $I_2 = 5 \text{ mA}$ (1) $I_3 = 30 \text{ mA}$ (1)	3
	Total for question	4