

Question Number	Answer	Mark
1(a)	<b>Plot of graph</b> Check points, 4 correct 2 marks, 3 correct 1 mark Line of best fit to include 0,0.6 and 0.52,0 (1)	3
(b)(i)	Use of $V = 0.43 \text{ V}$ in $P = VI$ (1) ecf values for incorrect best fit line $P = 0.17 \text{ W}$ (1)  <b>Example of calculation</b> $P = 0.4 \text{ A} \times 0.43 \text{ V}$ $P = 0.172 \text{ W}$	2
(b)(ii)	Value of e.m.f. is when the current is zero (1) No 'lost' volts OR no energy loss (1) <b>OR</b> $E = V + Ir$ $I = 0, E = V$	2
(b)(iii)	Identifies current in circuit (1) ecf values for incorrect best fit line Finds 'lost volts' (1) $r = 0.24 \Omega$ (1)  <b>Example of calculation</b> $r = (0.52 \text{ V} - 0.40 \text{ V}) \div 0.50 \text{ A}$ $r = 0.24 \Omega$	3
(c)	Graph of similar shape as in (a) but initially above the first graph (1) ecf values for incorrect best fit line  Finishing at $0.52 \text{ V}, 0.00 \text{ A}$ (1)	2
	<b>Total for question</b>	<b>12</b>

Question Number	Answer	Mark
2	Use of $V = IR$ (1) Use of lost volts = emf – terminal pd <b>Or</b> use of total resistance – $6.6\Omega$ (1) (quoting $\varepsilon = I(R + r)$ or $\varepsilon = V + Ir$ gets both marks) Internal resistance = $0.54\Omega$ (1) (rounding and different methods all give $0.5\Omega$ to 1 sig. fig .)  <u>Example of calculation</u> $V = 0.21\text{ A} \times 6.6\Omega = 1.39\text{ V}$ $Ir = 1.5\text{ V} - 1.39\text{ V} = 0.11\text{ V}$ $r = 0.11\text{ V} \div 0.21\text{ A} = 0.54\Omega$	3
<b>Total for question</b>		<b>3</b>

Question Number	Answer	Mark
3 (a)	Use of $R = V/I$ (for current) (1)  Use of sum of e.m.f. = sum of p.d.s Or use of $\mathcal{E} = V + Ir$ (1)  $r = 100\,000\Omega$ or $100\text{ k}\Omega$ or $1 \times 10^5\Omega$ (1) (Accept valid alternative methods based on potential divider)  <u>Example of calculation</u> $I = 0.018\text{ V} / 4700\Omega = 3.8 \times 10^{-6}\text{ A}$ $0.4\text{ V} = 0.018\text{ V} + (3.8 \times 10^{-6}\text{ A} \times r)$ $r = 100\,000\Omega$	3
3 (b)	Use of power = radiation flux $\times$ area (1)  Use of an electrical power equation (1)  Use of efficiency equation (1)  Efficiency = 12 % (1) (Full ecf for current from (a))  <u>Example of calculation</u> $\text{power} = 1.5 \times 10^{-3}\text{ W m}^{-2} \times 3.9 \times 10^{-4}\text{ m}^2 = 5.85 \times 10^{-7}\text{ W}$ $\text{power} = IV = 3.8 \times 10^{-6}\text{ A} \times 0.018\text{ V} = 6.84 \times 10^{-8}\text{ W}$ $\text{Efficiency} = 6.84 \times 10^{-8}\text{ W} / 5.85 \times 10^{-7}\text{ W} = 0.12$ OR 12 %	4
<b>Total for question</b>		<b>7</b>

	Answer			Mark
4(a)	Switch combination	Total resistance of circuit		(1) (1) (1) <b>3</b>
	A open. B closed.	$R$		
	A open. B open.	$2R$		
	A closed. B closed.	$R/2$ or $0.5 R$		
	A closed. B open.	$2R/3$ or $0.7 R$		
Answers must be in simplest form, e.g. not $R + R$				
4(b)	Reference to $P = V^2/R$ <b>OR</b> $P = VI$ and $V = IR$ (Accept energy equations.) (most power/energy) from the switch combination with the lowest resistance  [Ignore the table when awarding these method marks.]			(1) (1) <b>2</b>
4(c)	(Internal resistance will) reduce current <b>Or</b> reduce $V$ <b>Or</b> increase total $R$ <b>Or</b> cause lost volts <b>Or</b> energy transferred to internal resistance  less energy/power output (in all combinations)			(1) (1) <b>2</b>
<b>Total for question</b>				<b>7</b>