

Question Number	Answer	Mark
1(a)	Operable circuit with bulb and power supply variable to 12 V (ignore meters) (1) Ammeter correctly positioned (1) Voltmeter correctly positioned (1)  (voltmeter may be across ammeter as well, or whole circuit – but not across any additional resistive components such as a variable resistor)	3
1(b)(i)	The gradient of this graph is the rate of change of current with p.d. (1)  Resistance is the ratio of pd/current <b>Or</b> It is calculated using a value of pd ÷ the corresponding value of current <b>Or</b> it isn't a straight line so the gradient is not $R$ (1)  (credit $R$ not constant, so value at 6 V isn't applicable to other voltages)	2
1(b)(ii)	Use of $R = V/I$ (1) $R = 4.76 \Omega$ (1)  <u>Example of calculation</u> $R = 6.00 \text{ V} / 1.26 \text{ A}$ $R = 4.76 \Omega$	2
*1(c)	<b>(QWC – Work must be clear and organised in a logical manner using technical wording where appropriate)</b>  The resistance increases (1) (Because) the temperature increases (accept heats up) (1) Increasing the amplitude of the oscillation of the lattice ions (1) Leading to more (frequent) collisions of electrons with lattice ions (1)  Allow converse marks for an explanation explicitly based on decreasing potential difference	4
	<b>Total for question</b>	<b>11</b>

Question Number	Answer	Mark
2(a)	<u>Resistance</u> (of a fluid) to flow (1)	1
2(b)(i)	<p><u>Rate of flow</u> is inversely proportional to the viscosity  <b>Or</b> <u>rate of flow</u> decreases with increasing viscosity (and vice versa) (1)</p> <p>The time to empty the cup is proportional to the viscosity  <b>Or</b> the time to empty the cup is inversely proportional to the flow rate  <b>Or</b> the time to empty the cup decreases as viscosity decreases  <b>Or</b> the time to empty the cup decreases as the flow rate increases (1)            (Accept converse explanation in terms of time increasing for MP2)</p>	2
2(b)(ii)	<p>The temperature was greater on the first day  <b>Or</b> the temperature was lower (on the second day)  <b>Or</b> the paint/room was colder (on the second day)  <b>Or</b> the time is greater when the temperature is lower  <b>Or</b> the time is lower when the temperature is greater (1)</p>	1
2(c)	<p>Error 1 (1)            Correct outcome from error 1 (1)            Error 2 (1)            Correct outcome from error 2 (1)</p> <p>(Do not credit descriptions of changing temperature)</p> <p><u>Examples of answer</u>            Reaction time            Measured time greater than actual time</p> <p>Initial paint level in cup could be higher/lower than the level            Time would be greater /less</p> <p>Hole/opening becomes blocked            Time to drain would be greater</p> <p>Paint left in cup after pouring <b>Or</b> paint spilt            Reduces time to drain</p>	4
<b>Total for Question</b>		<b>8</b>

Question Number	Answer	Mark
3(a)	Resistivity is a constant for the material / metal OR resistivity depends on / is a property of the material / metal	(1)
	Resistance depends on (resistivity and) length / area / dimensions OR $R = \rho l/A$ with terms defined (do not credit rearranged equation)	(1)
3(b)	Correct substitution into the $R = \rho l/A$ formula $R = 0.0085 \Omega$  [ue applies. Common error is to rearrange eqn and confuse R and $\rho$ gives answer $3.4 \times 10^{-14}$ scores zero]  <u>Example of calculation</u>  $R = (1.7 \times 10^{-8} \Omega \text{ m} \times 0.5 \text{ m}) / 1 \times 10^{-6} \text{ m}^2$ $R = 0.0085 \Omega$	(1) (1)
12	Total for question	4

Question Number	Answer	Mark
4(a)	Use of $V=IR$	1
	$V = 3.0 \text{ V}$	1
(b)	pd across $30 \Omega$ resistor = $6.0 \text{ V}$ ecf their answer (a)	1
	$I_2 = 6.0/30 = 0.20 \text{ A}$	1
(c)	$I_1 = 0.60 - 0.20 = 0.40 \text{ A}$	1
	$R = 15 \Omega$ full ecf their answer for $I_2$ and their $V$ across $30 \Omega$	1
	<b>Total for question</b>	<b>6</b>

