

1 A capacitor is connected to a 6.0 V battery. The charge on the capacitor is 42 pC. What is the energy stored by the capacitor?

A 1.3×10^{-10} J

B 2.5×10^{-10} J

C 1.3×10^{-7} J

D 2.5×10^{-7} J

(Total for Question = 1 mark)

2 A capacitor with an initial charge Q_0 is discharging through a resistor. The time constant of the circuit is the time for the charge to fall to

A $0.25 Q_0$

B $0.37 Q_0$

C $0.50 Q_0$

D $0.63 Q_0$

(Total for Question = 1 mark)

3 Electrons are released from a heated metal filament.

This process is known as

A excitation.

B ionisation.

C photoelectric emission.

D thermionic emission.

(Total for Question = 1 mark)


4 A capacitor is discharging through a resistor and the time constant is 5.0 s. The time taken for the capacitor to lose half its charge is

- A 0.14 s
- B 0.81 s
- C 3.2 s
- D 3.5 s


(Total for Question 1 mark)

5 An uncharged capacitor is connected to a battery.

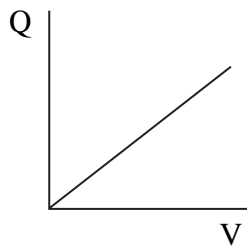
Which graph shows the variation of charge with potential difference across the capacitor?




A

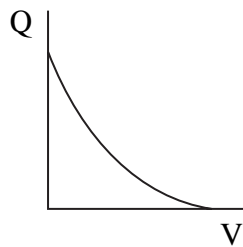

B

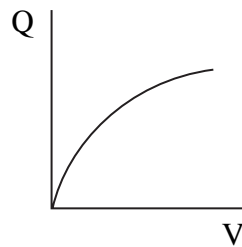

C

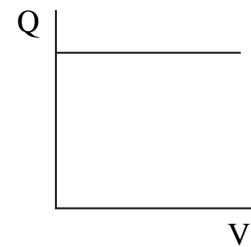


D


(Total for Question = 1 mark)

- 6 An electric motor is connected via a switch to a battery. A graph is plotted to show the variation of current I with time t . The switch is closed at time T .

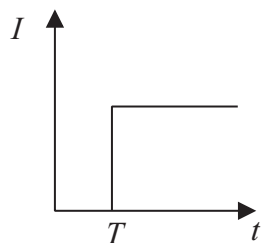
Which of the following graphs is correct?




A

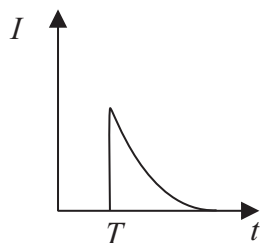

B

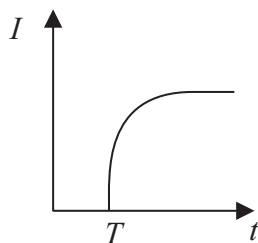

C

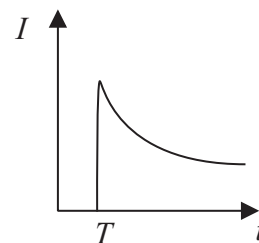

D

- A
- B
- C
- D

(Total for Question 1 mark)

- 7 The process by which electrons are released from a heated filament is known as

- A thermionic emission.
- B photoelectric emission.
- C ionisation.
- D excitation.

(Total for Question 1 mark)

8 The potential difference across a capacitor is V . The energy stored on the capacitor is X joules. The potential difference across this capacitor is increased to $3V$. The energy stored, in joules, is increased to

- A $3X$
- B $6X$
- C $9X$
- D $27X$

(Total for Question = 1 mark)


9 A capacitor of capacitance C has a potential difference V across it. The energy stored on the capacitor is Z joules. A second capacitor of capacitance $C/2$ has a potential difference $2V$ across it.

The energy stored on the second capacitor is


- A Z
- B $2Z$
- C $4Z$
- D $8Z$

(Total for Question = 1 mark)

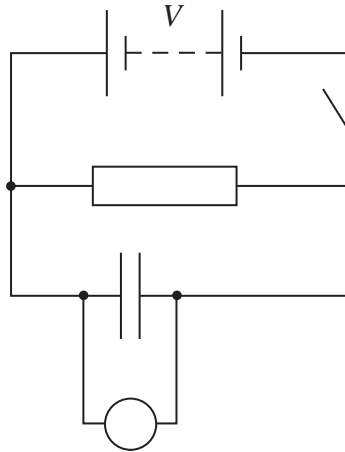- 10 The capacitor shown in the circuit below is initially charged to a potential difference (p.d.) V by closing the switch. The power supply has negligible internal resistance.



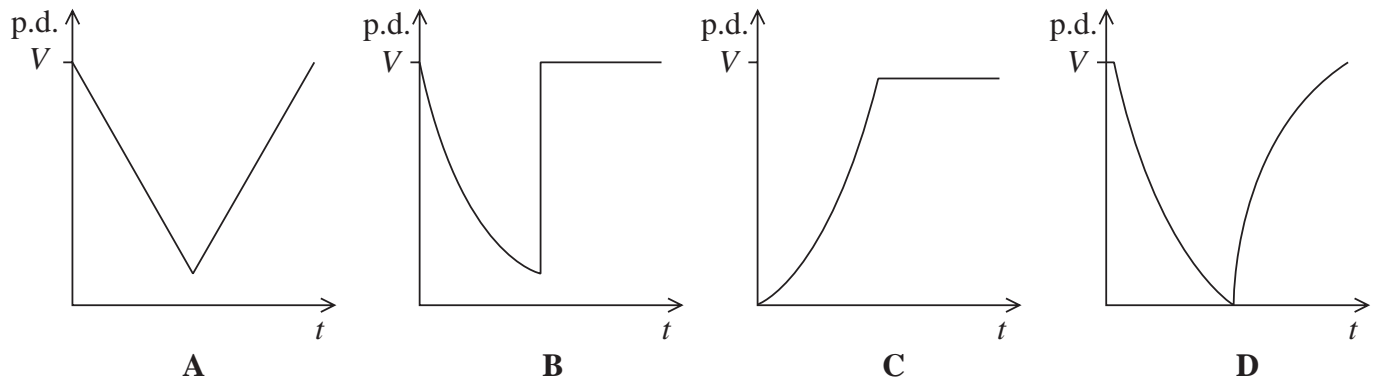The switch is opened and the p.d. across the capacitor allowed to fall. A short time later the switch is closed again. Select the graph that shows how the p.d. across the capacitor varies with time, after the switch is opened.



- A
- B
- C
- D

(Total for Question = 1 mark)