

Question Number	Answer	Mark
1(a)	<p>Increasing d will lead to a decrease in C Or see $Q/V = k/d$ (1)</p> <p>Since $C = Q/V$ (a decrease in C) means a decrease in the charge on the capacitor</p> <p>Or if V is constant (a decrease in C) means a decrease in charge on capacitor (1)</p>	2
1(b)	<p>Use of $C = k/d$ with $d = 4.2$ (mm) (1)</p> <p>use of $Q = CV$ with $V = 6$ V or cancelled later (1)</p> <p>use of $\Delta Q/Q$ or $\Delta C/C$ (1)</p> <p>% change = 17% (1)</p> <p><u>Example of calculation</u></p> $Q = \frac{6 \text{ V} \times 2.8 \times 10^{-15} \text{ F m}}{3.5 \times 10^{-3} \text{ m}} = 4.8 \times 10^{-12} \text{ C}$ $Q = \frac{6 \text{ V} \times 2.8 \times 10^{-15} \text{ F m}}{4.2 \times 10^{-3} \text{ m}} = 4.0 \times 10^{-12} \text{ C}$ $\frac{4.8 \times 10^{-12} \text{ C} - 4.0 \times 10^{-12} \text{ C}}{4.8 \times 10^{-12} \text{ C}} = 16.7\%$	4
1(c)	<p>(rapid changes in position) mean that rapid changes in Q</p> <p>Or a shorter time to charge/discharge (1)</p> <p>(small C gives) shorter <u>time constant/RC</u> (1)</p>	2
	Total for question 13	8

Question Number	Answer	Mark
2(a)	<p>Use of $C=Q/V$ (1) $V=15\text{ V}$ (1) Use of $W = QV/2$ Or $W = CV^2/2$ Or $W = Q^2/2C$ (1) $W = 2.5 \times 10^{-5}\text{ J}$ (1) (candidates who use $6.6 \times 10^{-6}\text{ C}$ can only score MP1 and MP3)</p> <p><u>Example of calculation</u> $V = Q/C = 3.3 \times 10^{-6}\text{ C} / 220 \times 10^{-9}\text{ F}$ $V = 15\text{ V}$ $W = QV/2 = (3.3 \times 10^{-6}\text{ C} \times 15\text{ V})/2$ $W = 2.5 \times 10^{-5}\text{ J}$</p>	4
2(b)	<p>$Q = 0.2 Q_0$ Or $Q = 6.6 \times 10^{-7}\text{ C}$ (1) Use of $Q = Q_0 e^{-t/RC}$ (1) $t = 7.1\text{ s}$ (1) (candidates who use $Q = 0.8 Q_0$ can only score MP2)</p> <p><u>Example of calculation</u> $Q = 0.2 Q_0$ $Q = Q_0 e^{-t/RC}$ $0.2 Q_0 = Q_0 e^{-t/RC}$ $\ln(0.2) = -t / (20 \times 10^6\ \Omega \times 220 \times 10^{-9}\text{ F})$ $t = 7.1\text{ s}$</p>	3
2(c)	<p>Either refers to $W = Q^2/2C$ Or $W \propto Q^2$ (1) If Q halves, $W \rightarrow Q^2/8C$ Or halving Q quarters W (1) (Since W becomes a quarter in the time for Q to half) it takes less time for the energy to halve than the charge to halve. (dependent mark on either MP1 or MP2) (1)</p> <p>Or Refers to $W = QV/2$ (1) Q and V both decrease over time (1) W will decrease faster so takes less time to half in value. (dependent mark on either MP1 or MP2) (1)</p>	3
2(d)	<p>Synchronous readings Or data logger records readings at exact time (1) Or voltmeter and stop watch need 2 people and data logger only one</p> <p>More readings can be taken in a shorter time Or higher sampling rate (1)</p> <p>(treat as neutral any reference to graph plotting automatically, human reaction time or accuracy)</p>	2
Total for question 15		12

Question Number	Answer		Mark
3(a)(i)	Use of $Q = CV$ $Q = 3900 \text{ (C)}$ <u>Example of answer</u> $Q = 1500 \text{ F} \times 2.6 \text{ V}$ $Q = 3900 \text{ C}$	(1) (1)	2
3(a)(ii)	Straight line through the origin Passing through 2.6 V and answer to (a)(i) or 4000 C	(1) (1)	2
3(a)(iii)	Use of $W = QV/2$ Or $W = CV^2/2$ Or use of area under graph $W = 5.1 \text{ kJ}$ (use of 4000 C gives $W = 5.2 \text{ kJ}$ (allow ecf from (a)(i)) <u>Example of answer</u> $W = 3900 \text{ C} \times 2.6 \text{ V} / 2$ $W = 5070 \text{ J}$	(1) (1)	2
3(b)(i)	Exponential decay Current decreases by equal fractions in equal time intervals	(1) (1)	2
3(b)(ii)	See attempt of I_0/e Finds time (accept 0.75-0.80s) Use of $\tau = RC$ $R = 0.0005 \Omega$ Or Finds the time for I_0 to half Uses $t_{1/2} = \tau \ln 2$ Use of $\tau = RC$ $R = 0.00050 - 0.00053 \Omega$ Or See attempt of 37% of 5400 A Finds time (accept 0.75 to 0.80 s) Use of $\tau = RC$ $R = 0.0005 - 0.00053\Omega$ Or Draws tangent at $t = 0$ to meet time axis. Records intercept of tangent with axis (accept 0.6 s - 0.9 s) Use of $\tau = RC$ $R = 0.0004 \Omega - 0.0006 \Omega$ Or reads a value off the y-axis and corresponding time Subs into formula using 5400 (A) to find RC Substitutes for C to find R $R = 0.00050 \Omega - 0.00058 \Omega$ <u>Example of calculation</u> 37% of 5400 A is 1998 A Time to fall to this value is 0.75 s $RC = 0.75 \text{ s}$ $R = 0.75 \text{ s} / 1500 \text{ F} = 0.0005 \Omega$	(1) (1) (1) (1) (1) (1) (1) (1) (1) (1) (1) (1) (1) (1) (1) (1) (1) (1) (1) (1)	4

3(c)	<p>Max 3</p> <p>Ultracapacitor used for: overtaking Or going up a hill Or starting (from rest) Or accelerating. (1) Because this requires a large <u>current/power</u>. (1) Batteries used for travelling at constant speed (1) Because this requires a small <u>current/power</u> for a longer time (1)</p>	3
Total for question 17		15

Question Number	Answer	Mark
4(a)(i)	Capacitor, resistor, supply and switch all in series (ignore voltmeter) Voltmeter directly across capacitor	(1) (1) 2
4(a)(ii)	Datalogger allows large number of readings to be taken Or graph can be plotted directly/automatically Or simultaneous reading of t and V can be taken Or idea that people can't record quickly enough, (treat as neutral accuracy, precision misreading or human reaction time)	(1) 1
4(b)	Use of $C = Q/V$ $Q = 5.0 \times 10^{-4} \text{ C}$ <u>Example of calculation</u> $Q = 100 \times 10^{-6} \text{ F} \times 5.0 \text{ V}$ $Q = 5.0 \times 10^{-4} \text{ C}$	(1) (1) 2
4(c)(i)	Use of $I = \Delta Q / \Delta t$ e.c.f their value of C from (b) $I = 0.05 \text{ A}$ (accept recalculation of Q using $V = 4.90$ or 4.95 V) <u>Example of calculation</u> $I = 5.0 \times 10^{-4} \text{ C} / 10 \times 10^{-3} \text{ s}$ $I = 0.05 \text{ A}$	(1) (1) 2
4(c)(ii)	tangent drawn at $t = 0$ $\Delta V / \Delta t = 2000 - 3300 \text{ V s}^{-1}$ Initial current = $0.22 - 0.28 \text{ A}$ (MP2 & 3 can be scored even if no tangent drawn) (No credit for exponential calculation) <u>Example of calculation</u> $\Delta V / \Delta t = 1.1 \text{ V} / 0.5 \text{ ms} = 2200 \text{ V s}^{-1}$ $I = (\Delta V / \Delta t) \times C$ $I = 2200 \text{ V s}^{-1} \times 100 \times 10^{-6} \text{ F}$ $I = 0.22 \text{ A}$	(1) (1) (1) 3
4(c)(iii)	Use of $V = IR$ using answer from (ii) correct evaluation of R (5V used with current range in (ii) gives $18 - 23 \Omega$) <u>Example of calculation</u> $5 \text{ V} = 0.22 \text{ A} \times R$ $R = 23 \Omega$	(1) (1) 2
PhysicsAndMathsTutor.com Total for question 14		12

Question Number	Answer	Mark
5(a)(i)	Use of $t=RC$ (1) Use of $T=1/f$ Or $f=1/t$ (1) Comparison of 2.2×10^{-4} (s) \ll 2.5×10^{-3} (s) Or comparison of 400 (Hz) \ll 4500 (Hz) Or reference to nRC (needed for complete discharge) where $n = 3 - 11$ Or $e^{-T/t}$ is a very small value (1)	3
5(a)(ii)	See $C = Q/V$ Or $Q = CV$ (1) See $Q = It$ (1) See $t = 1/f$ Or $f=1/t$ (1) (Answers based on $t = RC$ and $V = IR$ scores 0)	3
5(a)(iii)	sub in $C = I/fV$ (1) $C = 2.7 \mu\text{F}$ (1) <u>Example of calculation</u> $C = 5.4 \times 10^{-3} \text{ A} / (400 \text{ s}^{-1} \times 5.0 \text{ V})$ $C = 2.7 \mu\text{F}$	2
5(a)(iv)	$2.2 + 30\% = 2.9 (\mu\text{F})$ Or shows that $2.7 (\mu\text{F})$ is +22% of $2.2 (\mu\text{F})$ (1) Within tolerance / consistent (1) (2nd mark can only be awarded following an attempt at either of the above calculations) If candidates make an error in (iii) allow full ecf with a valid comment based on their values.	2
5(b)	Use of $\frac{1}{2} CV^2$ (1) $W = 3.4 \times 10^{-5} \text{ J}$ (1) (allow ecf from (iii) or use of $2.2 \mu\text{F} \rightarrow 2.75 \times 10^{-5} \text{ J}$) <u>Example of calculation</u> $W = \frac{1}{2} 2.7 \mu\text{F} \times (5.0 \text{ V})^2$ $W = 3.4 \times 10^{-5} \text{ J}$	2
Total for question 16		12

Question Number	Answer	Mark
6(a)	<p>Method marks only</p> <p>Use of $Q=CV$ with $V=16\text{ V}$ (1)</p> <p>Max value of $C = 12000\text{ }(\mu\text{F})$ (1)</p> <p>μF means 10^{-6} conversion of μF to F (1)</p> <p><u>Example of calculation</u></p> <p>$C_{\text{max}} = 1.20 \times 10000 = 12000\text{ F}$</p> <p>$C_{\text{max}} = 12000\text{ F} \times 16\text{ V}$</p> <p>$Q_{\text{max}} = 0.192\text{ C}$</p>	3
6(b)	<p>Either use of $\frac{1}{2} QV$ or $\frac{1}{2} CV^2$ (1)</p> <p>Energy = 1.5 J (1)</p> <p><u>Example of calculation</u></p> <p>$W = \frac{1}{2} 0.192\text{ C} \times 16\text{ V}$</p> <p>Energy = 1.54 J</p>	2
Total for question 13		5