
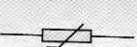


Question		Answer	M	Guidance
1				
	a	 for R ₁  for R ₂	B1 B1	
	b	i	500 Ω	B1 accept ± 20 Ω
		ii	7.0 = I x 500; I 0.014 (A)	B1 ecf b(i)
		iii	5.0 = 0.014 x R or 12 = 0.014(500 + R) R = 360 Ω	M1 A1 ecf b(i)(ii) allow R = 500 x 5/7 = 360 Ω
		iv	(at 200°C) R _{th} = 250 Ω V across thermistor = 12 x 250/(250 + 350) = 5.0 V alt 5.0 = 12 x R/(R + 350) or I = 7.0/350 = 0.02 A; V _{th} = 5.0 = 0.02 x R R = 250 Ω which occurs at 200°C	B1 B1 allow R _{th} = 250 ± 10 giving 4.8 to 5.1 V expect 350 or 360; allow 1 SF where answer is 5.0 NOT 250 x 0.02 = 5.0 V; 0.02 A must be justified allow 7.0 = 12 x 350/(350 + R)
	c	switch on 5.0 = 12 x 250/(250 + R) or 7.0 = 12 x R/(250 + R) giving R = 350 Ω which is 190°C switch off 7.0 = 12 x 250/(250 + R) or 5.0 = 12 x R/(250 + R) giving R = 180 Ω which is 210°C or Switch on, R ₂ / R ₁ = 7/5 giving R ₂ - 250 x 7/5 = 350 ohm Switch off, R ₂ / R ₁ = 5/7 giving R ₂ = 250 x 5/7 = 179 ohm	M1 A1 M1 A1	accept solution in 2 stages first calculating currents on I = 0.02 and R = 7/0.02 off I = 0.028 and R = 5/0.028 allow ± 5°C in reading from graph N.B. zero marks for correct temperatures quoted without some correct working/justification
		Total question 2	12	

Question		Answer	M	Guidance
2				
	a	i	$Q = It = 0.45 \times 4.67 \times 60 \times 60$ $= 7600$ C or As	C1 A1 B1 accept 7560 or 7570
		ii 1,2	1 positive; 2 clockwise energy must be transferred to the cell or current in opposite direction transfers energy from the cell to the circuit/AW	M1 A1 positive plus correct direction of arrow for first mark; do not penalise if arrow not labelled I. allow (conventional) current is from positive to negative ; or electron flow from – to + [but current must be clockwise in 1]
		3	$V_{XY} = 1.5 + 0.45 \times 0.90$ $V_{XY} = 1.9 \text{ (V)}$	C1 A1 accept 1.905 or 1.91
		4	$P = VI = 0.45 \times 1.5$ $P = 0.675 \text{ (J s}^{-1}\text{)}$	C1 A1 allow QV/t with ecf a(i) if necessary (11340/16800) allow 0.7 as final line if 0.675 appears above
	b		1. cell across variable resistor R ammeter in series and voltmeter in parallel across R or cell 2. Take (set of) readings of V and I for different positions/values of the variable resistor 3. plot a graph of V against I 4. (find) y-intercept = E 5. (find) the gradient of the V against I graph which equals the internal resistance in magnitude or 4 or 5 take one pair of values of V,I and substitute into equation $E = V + Ir$ to find r or E	B1 B1 B1 B1 B1 B1 QWC last marking point needed for full marks allow use (digital) voltmeter across <u>unloaded</u> cell to find E; add R and find one value of V and I; then use equation to find r (points 2 to 5) ignore sign of gradient in determining r allow for no graph plot, using 2 pairs of values of V and I substituted into equation allows r and E to be found.(points 2 to 5)
	c	i	4 x 1.5 V cells gives 6.0 V with r of 3.6 Ω so current is $6.0 / (3.6 + 18) = 0.28 \text{ A}$ requires (2 W/6 V =) 0.33 A to light normally or power delivered = $(0.28^2 \times 18 \text{ or } 5.0 \times 0.28) = 1.4 \text{ W}$ alt: use 0.33 A & 6 V to show need emf of 7.2 V (1.8 V per cell)	B1 B1 B1 allow AW such as: 6 V but total R now 21.6 Ω ; 6 V across 21.6 Ω gives 5 V across 18 Ω ; requires 6 V to light normally allow $P = 1.(6)7 \text{ W}$ for 2 marks; only give the third mark if P labelled as power delivered by cell
		ii	$1.5 n = 0.33 (18 + 0.9 n) \text{ or } 1.5n = 6 + 0.3n$ so $3.6 n = 18 \text{ or } 1.2n = 6$ giving $n = 5$	M1 A1 alt: lamp needs $V = 6\text{V}$ and $I = 0.33 \text{ A}$ terminal p.d per cell is $1.5 = V + 0.9 \times 0.33$ giving $V = 1.2 \text{ V}$ so $n = 6/1.2 = 5$ allow trial and error method but working must be shown to score any marks
		Total question 3	19	

Question		Answer	Marks	Guidance
3	a	emf – J C ⁻¹ , resistance – V A ⁻¹ , energy – V C, charge – A s	B1 B1	4 correct 2 marks; 2 correct 1 mark
	b	i	B1 B1	NOT coulomb allow any other form e.g. heat, light, etc
		ii	B1	allow any description which uses $E = V + Ir$ but not just the formula alone, e.g. 'lost volts' per unit current is just acceptable
		iii	B1 B1 A0	allow R in X branch is half that in YZ branch/AW
		iv	C1 A1	
		v	B1 B1 A0	p.d./voltage across 3 Ω and 6 Ω are equal with justification
		vi	C1 C1 C1 A1	or $V = 0.24 \times 4$ or $= 0.08 \times 12$ or 0.16×6 or (iv) $\times 2$ alt: R in parallel gives 4.0 Ω; total R = $1.2/0.24 = 5.0 \Omega$ $r = 5.0 - 4.0 = 1.0 (\Omega)$ allow 1SF
			Total	15