

Question		Answer	Marks	Guidance
2	(a)	R's in parallel have same V/AW so $4.0 \times 0.30 = 6.0 \times 0.20$	M1 A1	allow I splits in inverse ratio to R or AW; hence I in 6 ohm = $4 / 6 \times 0.3 = 0.2$ A
	(b) (i)	sum of/total current into a junction equals the sum of/total current out or total algebraic sum of currents is zero	B1	allow Kirchoff's first law
	(ii)	0.50 (A)	A1	accept 0.5 (A) (no SF error)
	(c)	correct formula for R_p and substitution $R_p = 2.4 \Omega$ $R_s = 8.0 (\Omega)$	C1 C1 A1	apply ecf to R_p for second mark accept 8 (Ω) (no SF error)
	(d) (i)	energy transferred from source/changed from some form to electrical energy; <u>per</u> unit charge (to drive charge round a complete circuit)	M1 A1	allow form as e.g. light/chemical/heat allow energy <u>divided by</u> charge
	(ii)	$V = IR = 0.50 \times 8.0 = 4.0$ (V)	A1	ecf b(ii),c i.e. answer = b(ii) x c accept 4 (V) (no SF error)
	(iii)	$E - V = Ir$ giving $5.0 - 4.0 = 0.50 r$ $r = 2.0 (\Omega)$	C1 A1	ecf b(ii) accept 2 (Ω) (no SF error); give max of 1 mark for $r = 3.3 \Omega$, i.e. using $I = 0.3$ A
		Total	12	

Question	Expected Answers	M	Additional Guidance
4			
a	resistance decreases with increase in light intensity	B1	ora
b	i 3.0 (V)	B1	accept 3 V, no SF error
	ii $3.0 = 1.1.2 \times 10^3$ giving $I = 2.5 \times 10^{-3}$ A $6.0 / 2.5 \times 10^{-3} = R = 2400 \Omega$ 2.4 k Ω	C1 C1 A1	accept $6 = (R / R + 1.2 \text{ k}).9$ $2R + 2.4 \text{ k} = 3R$ or similar $R = 2.4 \text{ k}$; give 2 with POT error accept ratio of resistors $6/3 \times 1.2$ good candidates can do this by inspection with no working – full marks allow 2400 written on answer line rather than 2.4 if 2400 Ω within body of text
	iii 49 or 50 (W m^{-2})	B1	ecf (b)(ii) if on R within graph range
c	i 2.2 (k Ω)	B1	allow any value from 2.1 to 2.2
	ii large(r) <u>changes in</u> R at low light intensities relating change in R to change in V	B1 B1	allow greater sensitivity of LDR at low light or steeper gradient/AW e.g. bigger change in I so in V or use of $V = R / (R + 1200) V_s$ or bigger change in V ratio across Rs
d	V across 1.2 k Ω falls so V across LDR rises because ratio of Rs changes in favour of LDR/ potential divider argument or total V is constant	B1 B1 B1	alternative I increases because <u>total</u> R is less so V across LDR rises do not award B marks where there is CON e.g. V across 1.2 k rises so V across LDR rises
e	continuous record for very long time scale of observation can record very short time scale signals (at intervals) automatic recording/remote sensing data can be fed directly to computer (for analysis)	B1 B1	allow any two sensible suggestions which fall within the 4 categories listed for 2 marks
	Total question 4	14	