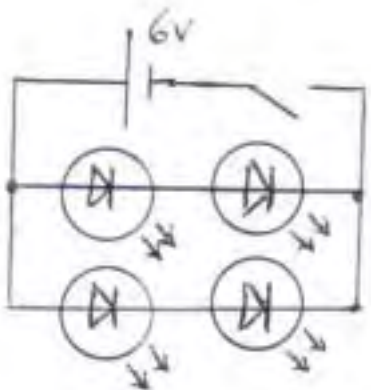


Question		Answer	Marks	Guidance
1	(a)	Work done/energy <u>transfer</u> (red) per unit time	B1	accept per second or rate of energy transfer / rate of doing work or energy transfer / time taken
	(b) (i)	using $P = VI$ $I = 40/230 = 0.17(4)$ (A)	C1 A1	accept 4/23
	(b) (ii)	$R = 230/0.17 = 1400$ (Ω)	B1	possible ecf b(i); expect and accept 1322 or 1353 Ω accept $40 = 230^2/R$ giving $R = 52900/40 = 1322 \Omega$
	(c)	$l = RA/\rho$ $l = 1.3 \times 10^3 \times 3.0 \times 10^{-8} / 7.0 \times 10^{-5}$ $l = 0.56$ (m)	C1 C1 A1	Choosing $R = \rho l/A$ substitution; ecf b(ii) evaluation; allow 0.57 m (using $R = 1322 \Omega$) and 0.58 m (using 1353 Ω) and 0.6 m (using 1400 Ω)
A A A	(d)	larger power needs larger I so smaller R (for same V) smaller R (but same length) so larger A / thicker	B1 B1 B1	accept $P = V^2/R$ or calculation $I = 0.26$ A giving $R = 880$ or 890Ω NB if R calculated correctly here, give first 2 marks hence smaller R (but same length) so larger A / thicker
	(e) (i)	$Q = It = 0.17 \times 8 \times 60 \times 60$ $Q = 4900$ (C)	C1 A1	ecf b(i) allow 4896; or 5000 or 5011 if using $I = 0.174$ A give 1 mark for 1.36 or 81.6
	(ii)1	(a unit of) <u>energy</u> equal to 3.6 MJ or 1 kW for 1 h/AW	B1	eg 1000 W for 3600 s or similar
	(ii)2	$40 \times 8 = 320$ Wh / 0.32 kWh $0.32 \times 22 = 7.0(4)$ p	C1 A1	accept 7 p (no SF error); allow 7000p (7040) for 1 mark
		Total	15	

Question			Answer	Marks	Guidance
2	(a)	(i)1	infinity	B1	accept symbol
	(a)	(i)2	$R = 1.8/10 \times 10^{-3}$ $R = 180 \Omega$	C1 A1	0.18 Ω scores 1 mark
A A A	(a)	(ii)	resistance decreases because I increases more than V therefore since $R = V/I$ value decreases/AW	B1 B1 B1	accept calculation at second value, e.g. at 2.0 $R = 53 \Omega$, <u>with comparison</u> OR at two other values QWC mark for second marking point
A A A	(b)		correct <u>symbol</u> and <u>direction</u> for LED R in series with LED across XY ammeter in series voltmeter in parallel with LED only	B1 B1 B1 B1	circle not essential, internal line optional no variable resistor
	(c)		torch; car brake/rear light/ traffic light, etc. torch: draws a lower current / light lasts longer before battery discharged/AW or LEDs (much) more efficient (at converting electrical energy into light)/AW or if one LED fails remainder still lit/AW	M1 A1	suitable example accept any one sensible statement, include longer life, more durable contradictory statements score zero
Total				12	

Question		Expected Answers	M	Additional Guidance
3				
	a	i read off value of current (at $V = 6.0 \text{ V}$) calculate R using V/I	B1 B1	any reference to using gradient scores 0/2 accept $I = 0.25 \text{ (A)}$ or 250 (mA) accept $R = 24 \Omega$
		ii V is not proportional to I	B1	accept not a straight line; R is not constant
	b	i $Q = It = 0.25 \times 1 = 0.25 \text{ C}$ ii $E = VIt$ or $QV = 6 \times 0.25 = 1.5 \text{ J}$ iii $E = VIt = 1.5 \times 4 \times 60 \times 60$ $= 2.16 \times 10^4 \text{ J}$	B1 B1 C1 A1	ecf(b)(i) ecf b(ii) accept $2.2 \times 10^4 \text{ J}$; allow 360 J for 1 mark only
	c	i energy transfer per unit charge from electrical to other forms ii 30 mA iii Use of $P = VI$ suitable method (may be expressed purely in numerical form) $= 0.36 \text{ W}$	B1 B1 A1 M1 A1 A0	or energy transfer/charge; work done /charge or across LED $3 \times 0.030 = 0.090 \text{ W}$ per LED so 0.090×4 or 30 mA in two branches at 6 V or total current is 60 mA from 6 V battery
		iv 	B1 B1 B1	symbol for LED correct orientation of LED correct circuit
	d	draws a lower current/ light lasts longer (before battery discharged)/AW or LEDs more efficient (at converting electrical energy into light) or if one LED fails there are still two lit or more robust/longer working life	B1	allow lower power consumption/AW
		Total question 1	16	