

Question			Answer	Marks	Guidance
1	(a)	(i)	potential difference (across a component)/current (in it)	B1	allow symbols if symbols defined; voltage or p.d.; allow per not over
		(ii)	read 10 V from graph ($R = V/I = 10/0.04$ $= 250 \text{ } (\Omega)$)	C1 M1 A0	allow 9.8 or 9.9 ecf reading from graph
	(b)		$R = \rho l/A$ or $\rho = RA/l$ $\rho = 250 \times 1.2 \times 10^{-3}$ $\rho = 0.30 \text{ } (\Omega \text{ m})$	C1 C1 A1	select formula mark ecf(a)(ii) ; a correct substitution correct answer allow 0.3
A A A	(c)		(graph curves so) R changes qualification: I increases faster than V increased temperature is caused by (larger) <u>current</u> in slice qualification: $P = I^2R$ as R decreases ρ decreases	B1 B1 B1 B1 B1	allow R increases or decreases allow : by calculating two values of R do not allow either of the first two marking points if reference made linking gradient and R value QWC mark ; allow heating effect is caused by.... allow 'R decreases' already stated earlier in answer max 3 out of 4 + QWC mark
			Total	10	

Question			Answer	Marks	Guidance
2	(a)	(i)	energy transfer per unit charge from chemical/other to electrical form	B1 B1	allow energy per unit charge
		(ii)	$(Q = It =) 200 \times 4 \times 60 \times 60$ $= 2.9 \times 10^6$ (C)	M1 A1	accept 200 x 14400 accept 2.88×10^6
		(iii)	$E = QV = 2.88 \times 10^6 \times 24$ $= 6.9 \times 10^7$ (J)	C1 A1	accept 72 MJ if using 3 MC or 69.6 or 70 if using 2.9 MC
	(b)	(correct symbol and polarity connected to X and Y	B1	allow one cell or more or two cells with dotted lines between
A		(ii)	$V = 30 - 24 = 6$ V $R = V/I = 6/120$ $= 0.05$ (Ω)	M1 M1 A0	evidence of the V subtraction needed do not allow use of $E = V + Ir$; it must be IR
		(iii)	$P = VI = 6 \times 120$ $= 720$ ($J s^{-1}$)	C1 A1	or $I^2R = 120^2 \times 0.05$ or $V^2/R = 6^2 / 0.05$
		(iv)	$(3600 - 720)/3600 = 2880/3600$ $= 0.8$ $= 80$ (%)	C1 C1 A1	ecf b(iii) ; using 2880 instead of 3600 gives 75%; scores zero allow $(30 - 6)I/30I = 24/30 = 0.8 = 80$ (%)
	(c)	($t = Q/I = 2.88 \times 10^6/120$ or $E/VI = 69 \times 10^6/(24 \times 120)$ $t = 2.4 \times 10^4/3600 = 6.7$ h	M1 A1	ecf (a)(iii) ; accept 3×10^6 giving 2.5×10^4 s and 6.9 h allow ora using 7.0 h giving $E = 72.5$ MJ
		(ii)	power supplied = $30 \times 120/1000 = 3.6$ kW cost = $3.6 \times 7 \times 26 = 655$ (p)	A1	ecf c(i) accept any consistent answer do not allow 2.88 kW giving 524 p unless repeated error from b(iv)
			Total	17	