

Question		Expected Answers	M	Additional Guidance
1				
	a	i	$12/2.0 = 6.0 \text{ } (\Omega)$	B1 allow 6; do not apply the SF penalty (N.B. applied only once per paper) for any answer where the second SF is 0
		ii	attempt to <u>use</u> resistors in parallel formula $1/R = 8/6$ $R = 0.75 \text{ } (\Omega)$	C1 C1 A1 no mark for just quoting formula ecf (a)(i) allow $\frac{3}{4} \text{ } (\Omega)$
		iii	$P = V^2/R = 12^2/0.75$ or $8VI = 8 \times 12 \times 2$ or $I^2R = 16^2 \times 0.75$ $= 192 \text{ W}$	C1 A1 ecf (a)(ii)
	b		$\rho = RA/l$ $= 6.0 \times 0.24 \times 2.0 \times 10^{-6}/0.9$ $= 3.2 \times 10^{-6}$ $\Omega \text{ m}$	C1 C1 A1 B1 correct rearrangement of formula ecf (a)(i) ; substitution into a correct formula 2/3 marks for one or more POT errors accept $3.2 \text{ } \Omega \text{ } \mu\text{m}$; 4×10^{-7} scores 2/3
	c	i	(As V is the same) then R must be the same to give <u>same P</u>	B1 accept alternative wording producing same argument, e.g. same I, same V so same R
		ii	$0.75/8 = 0.094 \text{ } (\Omega)$	B1 ecf (a)(ii)/8 ; accept 3/32 but NOT 0.09
		iii	for parallel circuit with break in one wire rest still work or series strips very wide (if use material of same resistivity as such low resistance/ giving poor visibility))	B1 any sensible statement
	d	i	14 V	B1
		ii	e.g. $V = 12 \text{ V}$; $I = 20$ substitution into $E = V + Ir$, e.g. $14 = 12 + 20 r$ $r = 0.1 \text{ } \Omega$	C1 C1 A1 or any suitable pair of readings from graph ecf(d)(i) ; accept $r = \text{gradient}$; $= (14 - 12)/20$ or similar ; $= 0.1 \text{ } \Omega$
Total question 2			17	

Question		Expected Answers	M	Additional Guidance
2				
	a	energy per unit area per unit time	B1	accept power per unit area; allow second for unit time
	b	Small <u>changes</u> in R for high light intensities/daylight conditions Large <u>changes</u> in R for low light intensities/dim light/night time conditions to change circuit state need a significant change in R to be useful/reliable	B1 B1 B1	accept low R by day, high R by night for 1 mark NOT comparison e.g. R by day smaller than R at night max 2 marks from 3 marking points
	c	i 2.5 (k Ω) ii 5.0 = I x 2.5 k Ω giving I = 2.0 x 10 ⁻³ A iii 4.0 = 2.0 x 10 ⁻³ x R or potential divider argument giving R = 2.0 x 10 ³ Ω	A1 C1 A1 M1 A0	allow 2.4 to 2.6 ecf (c)(i) accept 2.0 mA ecf (c)(ii) or ecf (c)(i) accept 2.0 k Ω
	d	R (of LDR) = 1(.0 k Ω) potential divider of 1.0 k Ω and 2.0 k Ω giving 3.0 V across LDR	B1 C1 A1	accept I = 3.0 (mA) so V = 3.0 (mA) x 1.0 (k Ω) = 3.0 V
	e	light shining on the LDR will cause it to switch the illumination off causing an ON/OFF oscillation/AW	B1 B1	two suitable qualifying statements for the 2 marks
Total question 3			12	

Question		Expected Answers	M	Additional Guidance
3				
	a	i		
		ii		
		iii		
		iv1		
		iv2		
	b			
	c	i		
		ii		
		Total question 2	15	