

Question		Answer	Marks	Guidance
1	(a)	resistivity = resistance x area (of cross-section)/length	B1	accept equation with <i>resistance</i> as subject allow <i>over</i> for divide by; do NOT allow formula with a word for each symbol
	(b) ($R = \rho l/A = 1.7 \times 10^{-8} / 6.4 \times 10^{-3}$ $= 2.7 \times 10^{-6} (\Omega)$	C1 A1	accept $2.66 \times 10^{-6} (\Omega)$
	(ii)	$P = I^2 R$ $= 8000^2 \times 2.7 \times 10^{-6}$ $= 170 \text{ W}$	C1 C1 A1	select formula; can use $P = VI$ & $V = IR$ ecf b(i) 173 (2.7), 170 (2.66)
	(iii)	$170 \times 9.0 = 1530 \text{ W}$ or $170 \times 24 = 4080 \text{ W}$ $1.5 \times 24 = 36 \text{ (kW h)}$ $4.08 \times 9 = 36.7 \text{ (kWh)}$	B1 B1	ecf b(ii) ; 1 mark for X 9 or 1 mark for X 24
	(iv)	$36 \times 15 = 540 \text{ p}$	B1	ecf b(iii) 551(36.7), 555 (37)
	(c)	$I = nAev$ $8000 = 8.4 \times 10^{28} \times 6.4 \times 10^{-3} \times 1.6 \times 10^{-19} v$ $v = 9.3 \times 10^{-5} \text{ (m s}^{-1}\text{)}$	C1 C1 A1	select formula correct substitution
		Total	12	

Question		Answer	Marks	Guidance
2	(a) (energy transferred from source/changed from some form to electrical energy; per unit charge (to drive charge round a complete circuit)	M1 A1	allow energy <u>divided by</u> charge
	(ii)	any source has an <u>internal resistance</u> where energy is transferred into thermal energy /lost as heat	B1 B1	there will be 'lost' volts (across the cell when a current is drawn) or $V = E - Ir$ explained
	(b) ($V = IR$ $1.2 = 0.2 R$ $R = 6.0 \Omega$	C1 A1	substitution needed to score mark allow 6Ω
	(ii)	$1.6 - 1.2 = 0.4 = 0.2 r$ $r = 2.0 \Omega$	C1 A1	allow 2Ω
	(c) (i)	$Q = It = 0.20 \times 3600 \times 1.5$ $= 1100$ correct unit,	C1 A1 B1	substitution needed to score mark 1080 allow 1 mark max for 0.3 or 18 allow C, kC, A s exception 0.3 A h or 18 A min scores 3 marks
	(i)	energy = $QV = 1100 \times 1.2$ or $I^2Rt = 0.2^2 \times 6 \times 5400$ $= 1320$ (J)	C1 A1	ecf (c)(i)1 substitution needed to score mark 1296(1080) allow 1 mark for 1728 (using 1.6)
	(ii)	I is constant for about 9 to 10 hours because <u>internal</u> resistance remains constant/cell operates at constant <u>emf</u> I falls <u>rapidly/towards zero</u> over last hour or so because <u>cell's/chemical energy</u> is used up (so E falls)	B1 B1 B1 B1	QWC must have link between observation and reason to score full marks accept r of cell increases causing fall in V or I
		Total	17	

Question		Expected Answers	M	Additional Guidance
3	a	use of $R = \rho l/A$ $= 2.4 \times 12 \times 10^{-3}/9.0 \times 10^{-6}$ $= 3.2 \times 10^3 (\Omega)$	C1 M1 A0	
	b	$V^2 = PR$ $= 0.125 \times 3.2 \times 10^3$ $V = 20(V)$	C1 M1 A0	allow $V = \sqrt{(0.125 \times 3.2 \times 10^3)}$ allow substituting $V = 20$ to prove $P = 0.125 \text{ W}$
	c	i	B1 B1	do not allow any reference to values of V or P , etc in answer
		ii	B1 B1	accept $P = 40^2/3.2 \text{ k} = 0.50 \text{ W}$ so P per resistor = $0.50/4 = 0.125 \text{ W}$ do not accept $P_{\text{total}} = 0.50 \text{ W}$ without proof – scores zero
	d	i	M1 A1	accept figures $24 \times 10^{-3} \text{ m}$ and $36 \times 10^{-6} \text{ m}^2$ to give $1.6 \times 10^3 \Omega$
		ii	B1 M1 A1	allow $P = V^2/R$; $V_X = 2V_Y$ etc. allow 1 mark only for using $P = V^2/R$ or IV and V is larger across X (i.e. not quantitative) so X has larger P
Total question 1			13	