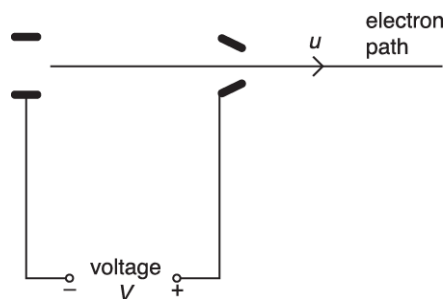


# Energy, Power and Resistance EMF and PD

1. An electron gun is used to accelerate electrons from rest through a voltage  $V$ . The electrons emerge with a speed  $u$ .



The voltage in the gun is halved to  $\frac{V}{2}$ . At what speed do the electrons emerge?

- A  $\frac{u}{4}$
- B  $\frac{u}{2}$
- C  $\frac{u}{\sqrt{2}}$
- D  $u\sqrt{2}$

Your answer

[1]

2. One million electrons travel between two points in a circuit. The **total** energy gained by the electrons is  $1.6 \times 10^{-10}$  J.

What is the potential difference between the two points?

- A  $1.6 \times 10^{-16}$  V
- B  $1.6 \times 10^{-4}$  V
- C  $1.0 \times 10^3$  V
- D  $1.0 \times 10^9$  V

Your answer

[1]


3. Which definition is correct and uses only quantities rather than units?

- A Acceleration is the change in velocity per second.
- B Resistance is potential difference per ampere.
- C Intensity is energy per unit cross-sectional area.
- D Electromotive force is energy transferred per unit charge.

Your answer

[1]

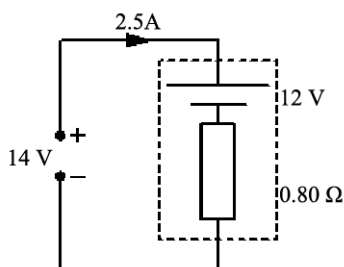4. A 14 V d.c. supply is used to charge a 12 V car battery of internal resistance  $0.80 \Omega$  for 6.0 hours. The current in the circuit is 2.5 A.



How much electrical energy is provided by the charging supply?

- A. 13 kJ
- B. 110 kJ
- C. 650 kJ
- D. 760 kJ

Your answer

[1]

5. In a particle-accelerator electrons are accelerated through a potential difference of 120 kV. The electron beam current is  $8.0 \mu\text{A}$ .

What is the total energy transferred to the electrons in a time of 2.0 hours?

- A 0.96 J
- B 120 J
- C 1900 J
- D 6900 J

Your answer

[1]

6. A small heater is connected to a power supply. The power supply is switched on for 100 s. The current in the heater is 3.0 A and it dissipates 1200 J of thermal energy.

What is the potential difference across the heater?

- A 0.25V
- B 4.0V
- C 12V
- D 300V

Your answer

[1]


7. Which of the following is **not** a source of electromotive force (e.m.f.)?

- A chemical cell
- B light-dependent resistor
- C power supply
- D solar cell

Your answer

[1]

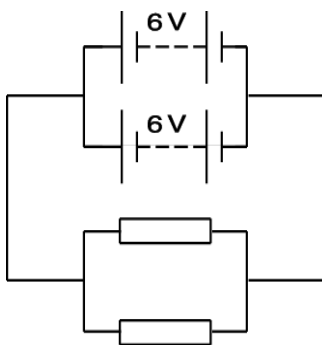8. Two batteries, each of e.m.f 6.0 V and negligible internal resistance, are joined in parallel. The cells are connected to two identical resistors, joined in parallel.



What is the voltage across each resistor?

- A. 1.5 V
- B. 3.0 V
- C. 6.0 V
- D. 12.0 V

Your answer

[1]

9. Stationary waves are produced in a flute when it is played. When all finger-holes are covered up, the flute can be treated as a pipe open at both ends. A flute is played so that it sounds the next harmonic above the fundamental frequency.


Which diagram correctly shows the node N and antinode A positions for the displacement of air for this harmonic?

- A**    A        N        A
- 
- B**    N        A        N
- 
- C**    A    N    A    N    A
- 
- D**    N    A    N    A    N

Your answer

[1]

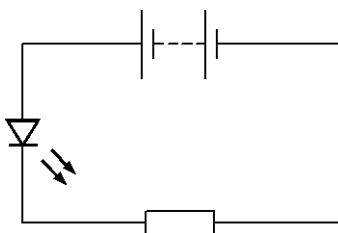10. A light-emitting diode (LED) and a resistor are connected in series to a battery of negligible internal resistance.



The e.m.f. of the battery is 8.0 V. A charge of 10 C passing through the resistor transfers 60 J of energy. What is the potential difference across the LED?

- A. 2.0 V
- B. 6.0 V
- C. 8.0 V
- D. 14.0 V

Your answer

[1]

11. The p.d. across a resistor is 12 V. The power dissipated is 6.0 W.

Which statement is correct?

- A. The charge passing through the resistor in one second is 2.0 coulomb.
- B. The resistor transfers 6.0 joule for each coulomb passing through the resistor.
- C. The resistor transfers 12 joule in 2.0 second.
- D. The resistor dissipates 6.0 joule when the current is 2.0 ampere.

Your answer

[1]

12. A battery of e.m.f. of 8.0 V and internal resistance 2.5  $\Omega$  is connected to an external resistor. The current in the resistor is 350 mA.

What is the power dissipated in the external resistor?


- A. 1.9 W
- B. 2.5 W
- C. 2.8 W
- D. 3.1 W

Your answer

[1]

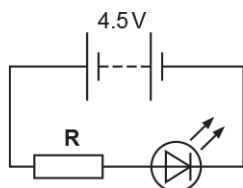13. A light-emitting diode (LED) emits red light when it is positively biased and has a potential difference (p.d.) greater than about 1.8 V.

An LED is connected into a circuit, as shown below.



The battery has electromotive force (e.m.f.) 4.5 V and negligible internal resistance.

The resistor **R** has resistance 150  $\Omega$ .

Assume the p.d. across the LED is 1.8 V.

Calculate the ratio  $\frac{\text{power dissipated by LED}}{\text{power dissipated by resistor}}$ .

ratio = ..... [2]

14. A filament lamp is described as being 120 V, 60 W. The lamp is connected to a supply so that it lights normally.

Which statement is correct?

- A. The charge passing through the filament in one second is 2.0 coulomb.
- B. The lamp transfers 60 joule for each coulomb passing through the filament.
- C. The lamp transfers 120 joule in 2.0 second.
- D. The supply provides 60 joule to the lamp when the current is 2.0 ampere.

Your answer

[1]

**15.** The unit of potential difference is the volt.

Use the equation  $W = VQ$  to show that the volt may be written in base units as  $\text{kg m}^2 \text{A}^{-1} \text{s}^{-3}$ .

**[3]**

**16(a).** Electron diffraction provides evidence for the wave-like behaviour of particles. Electrons are diffracted by a thin slice of graphite.

In one experiment, electrons are accelerated from rest through a potential difference of 300 V.


Show that the final speed  $v$  of the electrons is  $1.0 \times 10^7 \text{ m s}^{-1}$ .

**[3]**

**(b).** Determine the de Broglie wavelength  $\lambda$  of the electrons.

$\lambda = \dots\dots\dots \text{ m}$  **[2]**

17. Electrons in a beam are accelerated from rest by a potential difference  $V$  between two vertical plates before entering a uniform electric field of electric field strength  $E$  between two horizontal parallel plates, a distance  $2d$  apart.

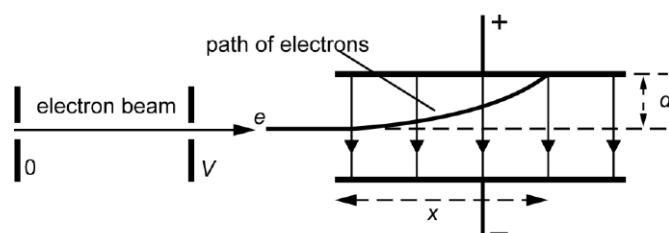

**Fig. 2.1**

The path of the electrons is shown in Fig. 2.1. The electron beam travels a horizontal distance  $x$  parallel to the plates before hitting the top plate. The beam has been deflected through a vertical distance  $d$ .

Show that  $x$  is related to  $V$  by the equation

$$x^2 = \frac{4dV}{E}$$

18 (a). The circuit diagram shows a battery of e.m.f.  $E$  and internal resistance  $r$  connected to a variable resistor  $R$ .

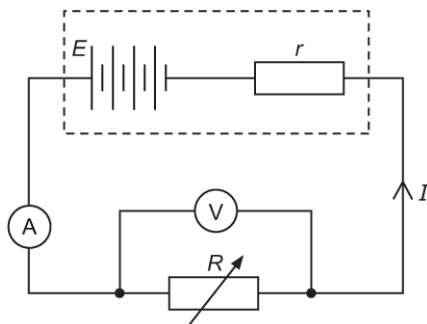


Fig. 5.1

The current  $I$  in the variable resistor is measured using an ammeter and the potential difference  $V$  across the variable resistor is measured using a voltmeter.

The resistance  $R$  of the variable resistor is varied.  $I$  and  $V$  are recorded for each value of  $R$ . A graph of  $V$  ( $y$ -axis) against  $I$  ( $x$ -axis) is plotted.

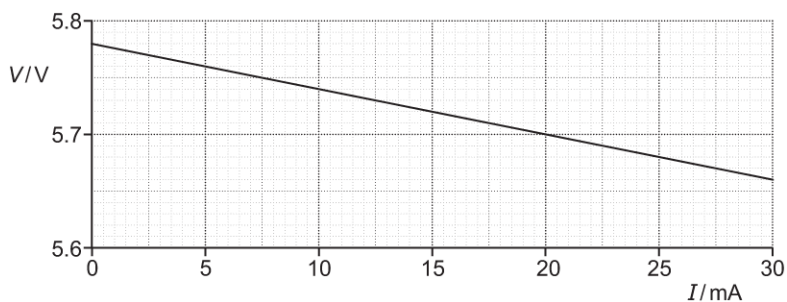


Fig. 5.2

Explain how values for  $E$  and  $r$  may be determined from the graph. No calculations are required.

.....

.....

.....

[2]

(b). The resistance of the variable resistor is now fixed. The current is 25 mA.

- i. Use the graph to determine the resistance  $R$  of the variable resistor.

$R = \dots\dots\dots \Omega$  [1]



- ii. Calculate the energy  $W$  dissipated in the variable resistor in 5.0 minutes.

$$W = \dots\dots\dots \text{ J [2]}$$

- iii. Calculate the charge  $Q$  passing through the variable resistor in 5.0 minutes. Include an appropriate unit.

$$Q = \dots\dots\dots \text{ unit } \dots\dots\dots \text{ [2]}$$

19. A chemical cell is connected across a resistor.

- i. The terms electromotive force (e.m.f.) and potential difference (p.d.) are terms associated with the circuit.

State **one** similarity and **one** difference between e.m.f. and p.d.

similarity:

-----  
-----

difference:


-----  
-----

[2]

- ii. The resistor is cylindrical in shape. It has cross-sectional area  $1.2 \times 10^{-6} \text{ m}^2$  and length  $6.0 \times 10^{-3} \text{ m}$ . In this resistor there are  $9.6 \times 10^{16}$  free electrons. Calculate the mean drift velocity  $v$  of the electrons when the current in the resistor is 3.0 mA.

$$v = \dots\dots\dots \text{ m s}^{-1} \text{ [3]}$$

20. **Fig. 26.1** shows part of the apparatus for an experiment in which electrons pass through a thin slice of graphite (carbon atoms) and emerge to produce concentric rings on a fluorescent screen.

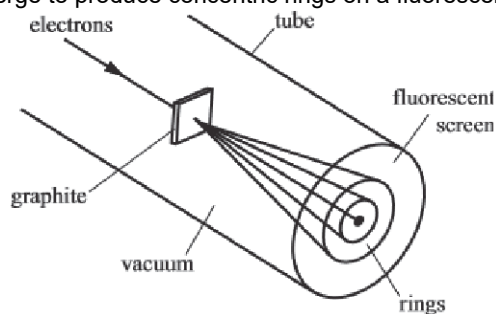

**Fig. 26.1**

- i. Explain how this experiment demonstrates the wave-nature of electrons.

---



---



---



---



---

[3]

- ii. The beam of electrons in the apparatus shown in **Fig. 26.1** is produced by accelerating electrons through a potential difference of 1200 V.

Show that the de Broglie wavelength of the electrons is  $3.5 \times 10^{-11}$  m.

[2]

- iii. When de Broglie first put forward his idea it was new to the scientific community. Describe one way in which they could validate his ideas.

---



---

[1]

21. A student monitors the temperature in a room by using a potential divider circuit containing a negative temperature coefficient (NTC) thermistor. The student sets up the circuit shown in Fig. 4.2.

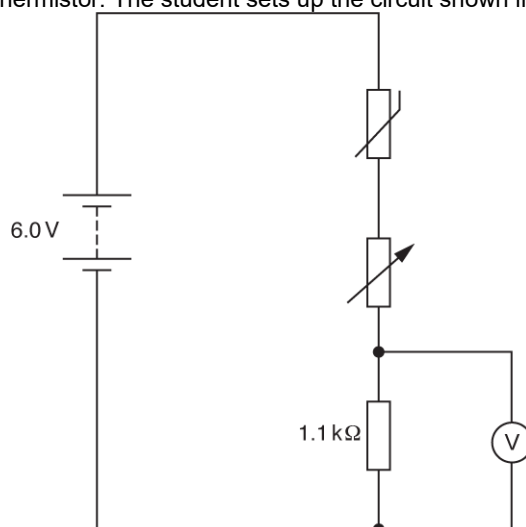


Fig. 4.2

The battery has an e.m.f. of 6.0 V and negligible internal resistance.

- i. When the temperature of the thermistor is 12 °C the thermistor has a resistance of 6.8 kΩ. The resistance of the variable resistor is set to a value of 1.4 kΩ. Calculate the reading  $V$  on the voltmeter.

$V = \dots\dots\dots V$  [2]

- ii. Explain how the reading on the voltmeter will change when the temperature of the thermistor increases.

.....

.....

.....

.....

.....

.....

.....


.....

.....

.....

[4]

**22 (a).** Fig. 4 shows a circuit with five identical  $60\ \Omega$  resistors. The battery has electromotive force (e.m.f.)  $9.0\ \text{V}$  and negligible internal resistance.

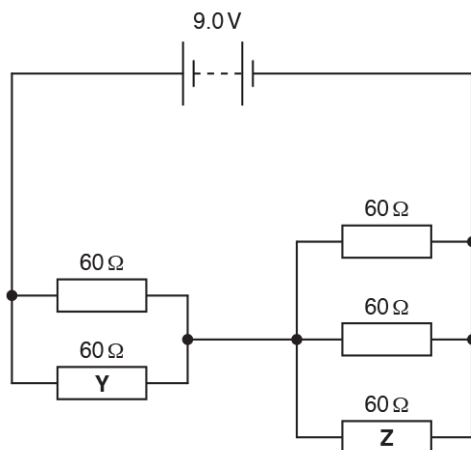

**Fig. 4**

- i. Show that the total resistance in the circuit is  $50\ \Omega$ .  
Make your reasoning clear.

[2]

- ii. Calculate the potential difference  $V$  across resistor **Y**.

$$V = \dots\dots\dots \text{V} \quad [2]$$

- iii. Calculate the charge  $Q$  passing through resistor **Y** in two minutes (include an appropriate unit).

$$Q = \dots\dots\dots \text{unit: } \dots\dots\dots [3]$$

- iv. Calculate the energy  $W$  dissipated in resistor **Y** in two minutes.

$$W = \dots\dots\dots \text{J} \quad [1]$$

(b). Explain how the mean drift velocity of electrons in resistor **Y** compares with the mean drift velocity of electrons in resistor **Z**.

---



---



---



---



---

[3]

23. A researcher is investigating the de Broglie wavelength of charged particles.


The charged particles are accelerated through a potential difference  $V$ . The de Broglie wavelength  $\lambda$  of these particles is then determined by the researcher.

Each particle has mass  $m$  and charge  $q$ .

- i. Show that the de Broglie wavelength  $\lambda$  is given by the expression  $\lambda^2 = \frac{h^2}{2mq} \times \frac{1}{V}$ .

[2]

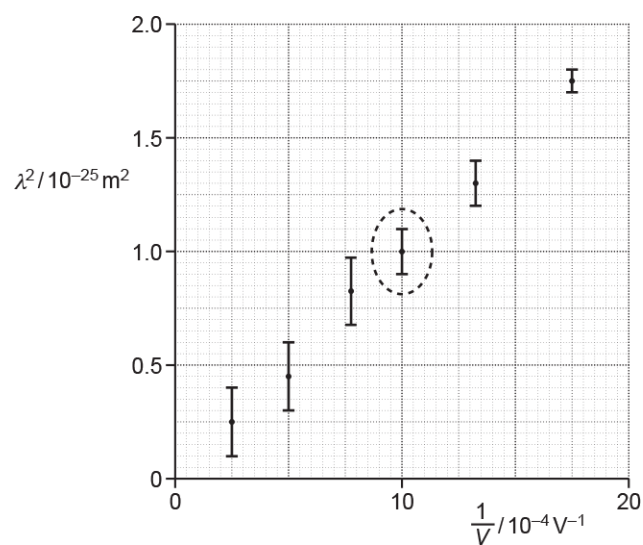- ii. The researcher plots data points on a  $\lambda^2$  against  $\frac{1}{V}$  grid, as shown below.



- 1 Calculate the percentage uncertainty in  $\lambda$  for the data point circled on the grid.

percentage uncertainty = ..... % **[2]**

- 2 Draw a straight line of best fit through the data points. **[1]**

- 3 The charge  $q$  on the particle is  $2e$ , where  $e$  is the elementary charge.

Use your best fit straight line to show that the mass  $m$  of the particle is about  $10^{-26}$  kg.

**[4]**

**END OF QUESTION PAPER**