

Question			Answer	Marks	Guidance
1	(a)	(i)	Correct shape of (exponential) decay curve (labelled L)	B1	Note: The curve must show a gradient of decreasing magnitude as time increases and appear to have a finite value of V at $t = 0$ Ignore any levelling of the curve or $V = 0$ towards the end
		(ii)	Correct shape of curve (labelled H)	B1	Note: As (i) and this curve must show a smaller time constant than (i); the initial V can be different Note: One of the curves must be labelled
		(iii)	Correct explanation in terms of constant-ratio for V values for <u>fixed</u> intervals of t	B1	Allow V is halved every half-life; V decreases to 0.37 (of its initial value) after every time constant Note: This can be scored on a suitably labelled sketch graph in either (iii) or Fig. 4.1
	(b)	(i)	(time constant = $6.9 \times 10^{-6} \times 240$) time constant = 1.7×10^{-3} (s)	B1	Note: Answer to 3 sf 1.66×10^{-3} (s)
		(ii)	charge = $6.9 \times 10^{-6} \times 1.4$ (= 9.66×10^{-6} C) ($\Delta t = 1/120 = 0.0083$ s) current = $\frac{6.9 \times 10^{-6} \times 1.4}{0.0083}$ current = 1.2×10^{-3} (A)	C1 C1 A1	Possible ecf from (b)(i) for value of total capacitance Note: Answer to 3 sf 1.16×10^{-3} (A) Allow: 2 marks for $9.66 \times 10^{-6} \times 60 = 5.8 \times 10^{-4}$ (A); $\Delta t = 1/60$ s used Allow: 2 marks for $9.66 \times 10^{-6} \times 240 = 2.3 \times 10^{-3}$ (A); $\Delta t = 1/240$ s used
		(iii)	The capacitors do not fully discharge (AW) Any <u>one</u> from: <ul style="list-style-type: none"> • Period (of switching) is (halved to) 4.2×10^{-3} (s) (and this time is comparable to the time constant) • The time constant (of the circuit) and period of mechanical switch are comparable / similar 	B1 B1	
Total				9	

Question		Answers	Marks	Guidance
2	(a)	The time taken for the p.d / current / charge to decrease to 1/e of its (initial) value.	B1	Allow 37% instead of 1/e. Not time constant = CR on its own.
	(b)	Any suitable values with units, eg: 5 MΩ and 1 μF.	B1	
	(c) (i)	$R = \frac{4.9 \times 10^{-7} \times 5.0}{\pi \times (0.06 \times 10^{-3})^2}$ or $R = 217 \text{ (}\Omega\text{)}$ time constant = 0.010×217 time constant = 2.2 (s)	C1 C1 A1	Note: An incorrect equation here for A prevents this and any subsequent marks. Allow 2 marks for 0.54 (s) – diameter of 0.12 mm used instead of radius 0.06 mm.
	(ii)	Electrons are removed from X or electrons are deposited on Y . X becomes positive or Y becomes negative (The size of charge is the same because) an equal number of electrons are removed and deposited (on the plates).	B1 B1 B1	Allow electrons move anticlockwise (in the circuit). There is no ecf from the previous B1 mark.
	(iii)	$E = \frac{1}{2} \times 0.010 \times 12^2$ or $E = 0.72 \text{ (J)}$ $m = 8900 \times [\pi \times (0.06 \times 10^{-3})^2 \times 5.0]$ or $5.0(3) \times 10^{-4} \text{ (kg)}$ $5.03 \times 10^{-4} \times 420 \times \Delta\theta = 0.72$ increase in temperature = 3.4 (°C)	C1 C1 C1 A1	Note: An incorrect equation here for m or V prevents this and any subsequent marks. Correct substitution into $mc\Delta\theta = 0.72$; allow any subject. Note: Do not penalise using diameter here again if already penalised in (c)(i).
	(iv)	Energy or V^2 increases by a factor of 4. The (change in temperature) increases by a factor of 4 (because $\Delta\theta \propto E$).	B1 B1	Allow the label E or W for energy. Allow $\Delta\theta = 13.6 \text{ (}^\circ\text{C)}$ for this B1 mark - possible ecf from (iii).
Total			14	

Question		Answer	Marks	Guidance
3	(a)	Series branch: Using $(100^{-1} + 300^{-1})^{-1}$ and $C = 75 \text{ } (\mu\text{F})$ capacitance = 500 + 75 capacitance = 575 (μF)	C1 A1	Possible ecf, if capacitance of series branch is incorrect
	(b) (i)	Time constant method: 37% of 6.0 V is 2.2 V. The time taken to reach 2.2 V is equal to the time constant time constant = 60 (s) / $CR = 60 \text{ (s)}$ $500 \times 10^{-6} \times R = 60$ $R = \frac{60}{500 \times 10^{-6}}$ resistance = $1.2 \times 10^5 \text{ } (\Omega)$ Substitution method: Correct values for p.ds and t substituted into $V = V_0 e^{-\frac{t}{CR}}$ Correct values substituted into $\ln(V/V_0) = -\frac{t}{CR}$ resistance = $1.2 \times 10^5 \text{ } (\Omega)$	C1 C1 A1 C1 C1 A1	Note: Allow full credit for other correct methods Allow: time constant in the range 58 s to 62 s Deduct 1 mark for misreading graph followed by ecf Note: If C value from (a) is used, then deduct 1 mark followed by ecf Eg: $2.2 = 6.0e^{-\frac{60}{CR}}$ - values read $t \pm 1$ small square Eg: $\ln(2.2/6.0) = -\frac{60}{500 \times 10^{-6} \times R}$ Note: If C value from (a) is used, then deduct 1 mark followed by ecf. Using 575 (μF) gives $1.04 \times 10^5 \text{ } (\Omega)$
	(ii)	Correct p.ds from graph: 6 (V) and 3.6 (V) $\frac{1}{2} \times 500 \times 10^{-6} \times 6.0^2$ or $\frac{1}{2} \times 500 \times 10^{-6} \times 3.6^2$ energy is $9.00 \times 10^{-3} \text{ (J)}$ and $3.24 \times 10^{-3} \text{ (J)}$ energy lost = $5.76 \times 10^{-3} \text{ (J)}$ or $5.8 \times 10^{-3} \text{ (J)}$	C1 C1 A1	Allow V value to be in the range 3.5 V to 3.7 at 30s Note: Do not penalise 10^n error from (b)(ii) again here Allow 1 mark for: $\frac{1}{2} \times 500 \times 10^{-6} \times (6.0 - 3.6)^2 = 1.44 \times 10^{-3} \text{ (J)}$ Note: Do not penalise use of 575 μF again. This gives a value of $6.62 \times 10^{-3} \text{ (J)}$
Total			8	

Question		Answer	Marks	Guidance
4	(a)	(farad = 1) coulomb per (unit) volt	B1	Allow: C V ⁻¹
	(b)	(i)	B1	Allow: 'inverse of C'
		(ii)	B1	
	(c)	<p>Diagram: All 3 capacitors connected in series</p> $\frac{1}{C} = \frac{1}{100} + \frac{1}{200} + \frac{1}{500} \quad / \quad \frac{1}{C} = 1.7 \times 10^{-2}$ <p>capacitance = 59 (μF)</p>	B1 C1 A1	<p>Note: Correct symbol must be used for capacitor and at least one of the capacitance values (without the unit) must be shown</p> <p>Allow: Answer to 1 sf Note: Answer to 3sf is 58.8 (μF) Allow: 1.7 × 10⁻² (μF) scores 1 mark from the C1A1</p>
	(d)	(i)	C1 A1	Allow: 1 mark for 2.4 × 10 ⁿ , n ≠ 0 (POT error)
		(ii)	C1 A1	<p>Possible ecf from (d)(i)</p> <p>Note: Answer to 3 sf is 28.8 (J) Allow full credit for correct use of ½ VQ or ½ V²C; the final p.d is 24 (V)</p>
			Total	10

Question		Expected Answers	Marks	Additional guidance
5	(a)	capacitance = charge / potential difference	B1	Allow: p.d. and voltage Not: charge per volt or coulombs per p.d
	(b) (i)	$V = Q/C$ and $Q = \text{constant}$ in series circuit $V = \frac{450}{450 + 150} \times 6.0$ potential difference = 4.5 (V)	C1 A1	Allow: 1 mark for an answer of 1.5 (V) Note: Using (b)(ii), alternative marking scheme $V = 6.75 \times 10^{-4} / 150 \times 10^{-6}$ C1 $V = 4.5$ V A1
	(ii)	charge = $150 \times 10^{-6} \times 4.5$ charge = 6.75×10^{-4} (C)	B1	Possible e.c.f. Note: Using (b)(iii) ... $Q = 6.0 \times 1.125 \times 10^{-4} = 6.75 \times 10^{-4}$ (C)
	(iii)	$\frac{1}{C} = \frac{1}{150} + \frac{1}{450}$ (working in μF) capacitance $C_T = 1.125 \times 10^{-4}$ (F) or 113 μF	B1	Possible alternative: capacitance = $6.75 \times 10^{-4} / 6.0$ capacitance = 1.125×10^{-4} (F) or 113 μF Possible e.c.f. from (ii)
	(c) (i)	time constant = CR time constant = $1.125 \times 10^{-4} \times 45 \times 10^3$ time constant = 5.06 (s)	M1 A0	Note: The mark is for multiplying correct C and R values Possible e.c.f. from (b)(iii)
	(ii)	Graph starting from 6.0 (V) Correct shaped curve Approximately correct value of V at CR	B1 B1 B1	Note: The (exponential decay) curve must not touch or cut the time axis Note: V is 2 to 2.5 (V) at $t \approx 5$ s

Question		Expected Answers	Marks	Additional guidance
	(iii)	$\frac{1}{2} \times 4.5^2 \times 150 \times 10^{-6}$ <u>and</u> $\frac{1}{2} \times 1.5^2 \times 450 \times 10^{-6}$ ratio = $\frac{0.5 \times 4.5^2 \times 150 \times 10^{-6}}{0.5 \times 1.5^2 \times 450 \times 10^{-6}}$ ratio = 3 <p style="text-align: center;">Or</p> $\frac{1}{2} Q^2 / C_{150}$ and $\frac{1}{2} Q^2 / C_{450}$ ratio = C_{450} / C_{150} ratio = 3	C1 A1 C1 A1	Allow: with or without the 10^{-6} Possible e.c.f. from (b)(i) and (b)(ii) Allow: full credit for correct use of either $\frac{1}{2} QV$ or $\frac{1}{2} Q^2 / C$
	(iv)	The ratio remains constant The charge / Q is the same for both capacitors	B1 B1	
Total			13	